

# ECE 113- Basic Electronics

Lecture week 10: Continuation of AC response in circuits (under steady state condition)

---

Dr. Ram Krishna Ghosh, Assistant Professor  
Office: B601, Research and Development Block


Email: [rkghosh@iiitd.ac.in](mailto:rkghosh@iiitd.ac.in)



INDRAPRASTHA INSTITUTE *of*  
INFORMATION TECHNOLOGY  
DELHI


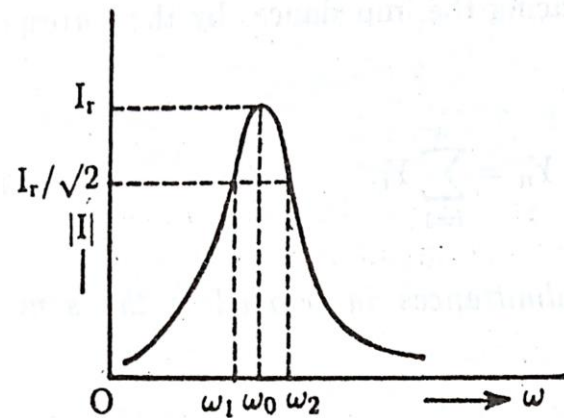
## Bandwidth frequencies of a series RLC circuit



Current response in series RLC circuit

Let  $\omega_x$  is the angular frequency at which current is  $I = I_r/\sqrt{2}$

$$\frac{I_r}{\sqrt{2}} = \frac{V}{\sqrt{2}R} = \frac{V}{\left[ R^2 + \left( \omega_x L - \frac{1}{\omega_x C} \right)^2 \right]^{1/2}}$$

$$\text{or, } 2R^2 = R^2 + \left( \omega_x L - \frac{1}{\omega_x C} \right)^2$$

$$\text{or, } \omega_x L - \frac{1}{\omega_x C} = \pm R$$

$$\text{or, } \omega_x^2 LC \mp \omega_x RC - 1 = 0.$$

Only positive roots of this eq. are acceptable

The roots are

$$\omega_1 = \frac{\sqrt{R^2 C^2 + 4LC} - RC}{2LC}$$

$$\text{and } \omega_2 = \frac{\sqrt{R^2 C^2 + 4LC} + RC}{2LC}$$

$$\omega_2 - \omega_1 = \frac{R}{L} = \frac{\omega_0 R}{\omega_0 L} = \frac{\omega_0}{Q}$$

$$\text{or, } Q = \frac{\omega_0}{\omega_2 - \omega_1}. \quad \text{This eq. relates the Q factor with bandwidth} \\ \rightarrow \text{Higher the Q, smaller the bandwidth}$$

At frequencies  $\omega_1$  and  $\omega_2$  the power dissipation is  $(I_r/\sqrt{2})^2 R \rightarrow$  half the power dissipated at resonance. **So  $\omega_1$  and  $\omega_2$  are called half power frequencies**

## Capacitor voltage in series RLC circuit




The voltage across capacitor C is  $V_C = -\frac{j}{\omega C} \frac{V}{R + j(\omega L - \frac{1}{\omega C})}$  where V is the applied voltage

The magnitude of  $V_C$  is

$$|V_C| = \frac{V}{\omega C \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} = \frac{V}{[\omega^2 R^2 C^2 + (\omega^2 LC - 1)^2]^{1/2}} \quad (a)$$

$|V_C|$  is maximum at  $\omega = \omega_c$  when the denominator on the r.h.s. of the eq. (a) is minimum. Therefore, for maximum  $|V_C|$ , we have

$$\begin{aligned} \frac{d}{d\omega} [\omega^2 R^2 C^2 + (\omega^2 LC - 1)^2] &= 0 \\ \text{or, } 2\omega R^2 C^2 + 4\omega LC(\omega^2 LC - 1) &= 0 \\ \text{or, } 2LC(\omega^2 LC - 1) + R^2 C^2 &= 0 \\ \text{or, } \omega = \omega_c &= \left[ \frac{1}{LC} \left( 1 - \frac{R^2 C}{2L} \right) \right]^{1/2} \\ \text{or, } \omega_c &= \omega_0 \left[ 1 - \frac{1}{2Q^2} \right]^{1/2} \quad (b) \end{aligned}$$

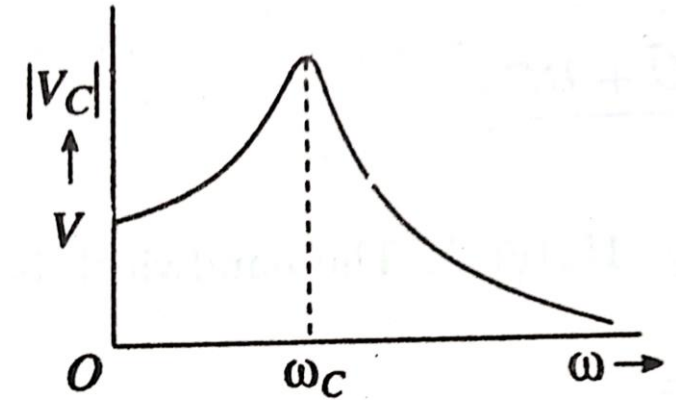

**Fig.15.17A.** Variation of  $|V_C|$  with  $\omega$

From eq. (b),  $\omega_c < \omega_0$  where  $\omega_0$  is the resonant frequency.

→ This is expected, as current peaks at  $\omega_0$  and the capacitor voltage is a product of current and  $1/\omega C$  which increases with decreasing frequency.

**When Q is large  $\omega_c \simeq \omega_0$**

→  $\omega_c$  is sometimes called capacitor charge resonance or voltage resonance, but current resonance is true resonance as current and voltage in the circuit is in phase.

## Sinusoidal voltage applied to a parallel RLC circuit

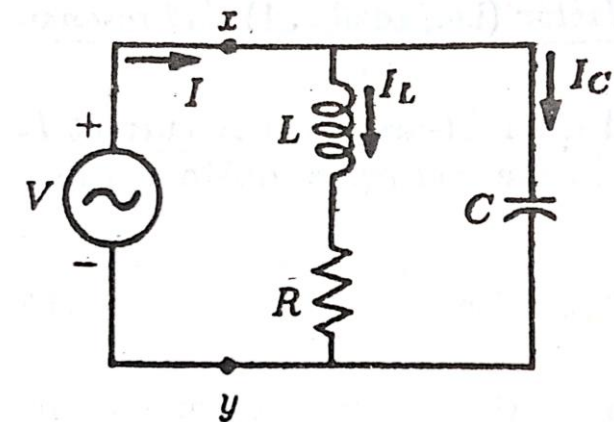


Fig.15.19. A parallel resonant circuit

Let  $I_L$  and  $I_C$  are phasors for current through the inductor and the capacitor, respectively, and  $I$  is the current from the source.

→  $I_L$  and  $I_C$  are almost  $180^\circ$  out of phase.  $I_C$  leads source voltage  $V$  by  $90^\circ$  while  $I_L$  lags source voltage  $V$  by  $90^\circ$ .

By KCL, the source current  $I$  is a phasor sum of  $I_C$  and  $I_L$ , and in resonance  $V$  and  $I$  are in phase.

We have, 
$$I = I_C + I_L \quad (1)$$

But,  $I = V/Z$ ; where  $Z$  is the impedance offered by the circuit at the terminal  $x, y$  in the circuit.

Also, 
$$I_L = \frac{V}{R + j\omega L} \quad \text{and} \quad I_C = \frac{V}{1/(j\omega C)} = j\omega CV. \quad (2)$$

Therefore, from (1) and (2),

$$\begin{aligned} \frac{V}{Z} &= \frac{V}{R + j\omega L} + j\omega CV \\ \text{or, } \frac{1}{Z} &= \frac{1}{R + j\omega L} + j\omega C \end{aligned} \quad \begin{aligned} \frac{1}{Z} &= \frac{R - j\omega L}{R^2 + \omega^2 L^2} + j\omega C \\ \text{or, } Y = \frac{1}{Z} &= \frac{R + j(\omega CR^2 + \omega^3 L^2 C - \omega L)}{R^2 + \omega^2 L^2} \end{aligned} \quad \begin{aligned} & \text{[Y is the admittance]} \\ & (3) \end{aligned}$$

In resonance,  $I$  and  $V$  will be in phase when the imaginary part of  $Y$  is zero, i.e.,

$$\omega CR^2 + \omega^3 L^2 C - \omega L = 0$$

$$\text{or, } \omega^2 L^2 C = L - CR^2$$

$$\text{or, } \omega = \omega_p = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$\omega_p \rightarrow$  parallel resonance angular frequency

The impedance of the circuit is purely resistive at resonance

Corresponding parallel resonance frequency,  $f_p = \frac{\omega_p}{2\pi} = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$

Admittance in resonance  $\rightarrow Y_p = \frac{R}{R^2 + \omega_p^2 L^2} = \frac{R}{L/C} = \frac{CR}{L}$

If  $R$  is small  $\rightarrow Z_p$  is large.

For  $R \rightarrow 0, Z_p \rightarrow \infty$

Also when  $R \rightarrow 0; \omega_p \rightarrow \frac{1}{\sqrt{LC}}$  the series resonance angular frequency

and the impedance in resonance  $\rightarrow Z_p = \frac{1}{Y_p} = \frac{L}{CR}$