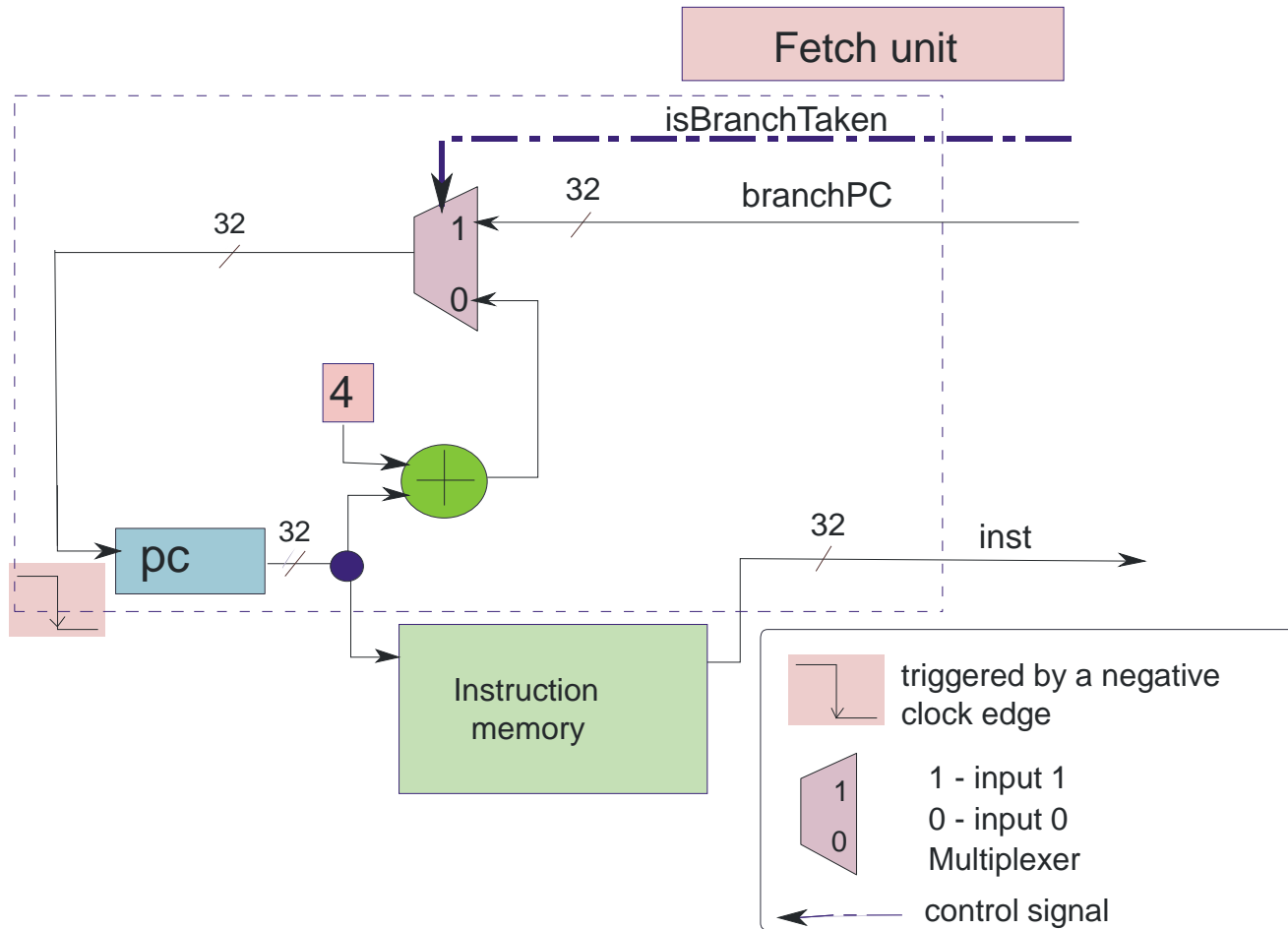


Instruction Fetch (IF) Stage



isBranchTaken

- * isBranchTaken is a **control** signal
 - * It is generated by the EX unit
- * Conditions on isBranchTaken

Instruction	Value of <i>isBranchTaken</i>
non-branch instruction	0
<i>call</i>	1
<i>ret</i>	1
<i>b</i>	1
<i>beq</i>	branch taken – 1 branch not taken – 0
<i>bgt</i>	branch taken – 1 branch not taken – 0

Operand Fetch Unit

Inst.	Code	Format	Inst.	Code	Format
add	00000	add rd, rs1, (rs2/imm)	lsl	01010	lsl rd, rs1, (rs2/imm)
sub	00001	sub rd, rs1, (rs2/imm)	lsr	01011	lsr rd, rs1, (rs2/imm)
mul	00010	mul rd, rs1, (rs2/imm)	asr	01100	asr rd, rs1, (rs2/imm)
div	00011	div rd, rs1, (rs2/imm)	nop	01101	nop
mod	00100	mod rd, rs1, (rs2/imm)	ld	01110	ld rd, imm[rs1]
cmp	00101	cmprs1, (rs2/imm)	st	01111	st rd, imm[rs1]
and	00110	and rd, rs1, (rs2/imm)	beq	10000	beq offset
or	00111	or rd, rs1, (rs2/imm)	bgt	10001	bgt offset
not	01000	not rd, (rs2/imm)	b	10010	b offset
mov	01001	mov rd, (rs2/imm)	call	10011	call offset
			ret	10100	ret


Instruction Formats

Format	Definition					
<i>branch</i>	<i>op</i> (28-32)	<i>offset</i> (1-27)				
<i>register</i>	<i>op</i> (28-32)	<i>I</i> (27)	<i>rd</i> (23-26)	<i>rs1</i> (19-22)	<i>rs2</i> (15-18)	
<i>immediate</i>	<i>op</i> (28-32)	<i>I</i> (27)	<i>rd</i> (23-26)	<i>rs1</i> (19-22)	<i>imm</i> (1-18)	
<i>op</i> → opcode, <i>offset</i> → branch offset, <i>I</i> → immediate bit, <i>rd</i> → destination register						
<i>rs1</i> → source register 1, <i>rs2</i> → source register 2, <i>imm</i> → immediate operand						

- * Each format needs to be **handled** separately.


St *r1*, 20[*r2*]

Register File Read

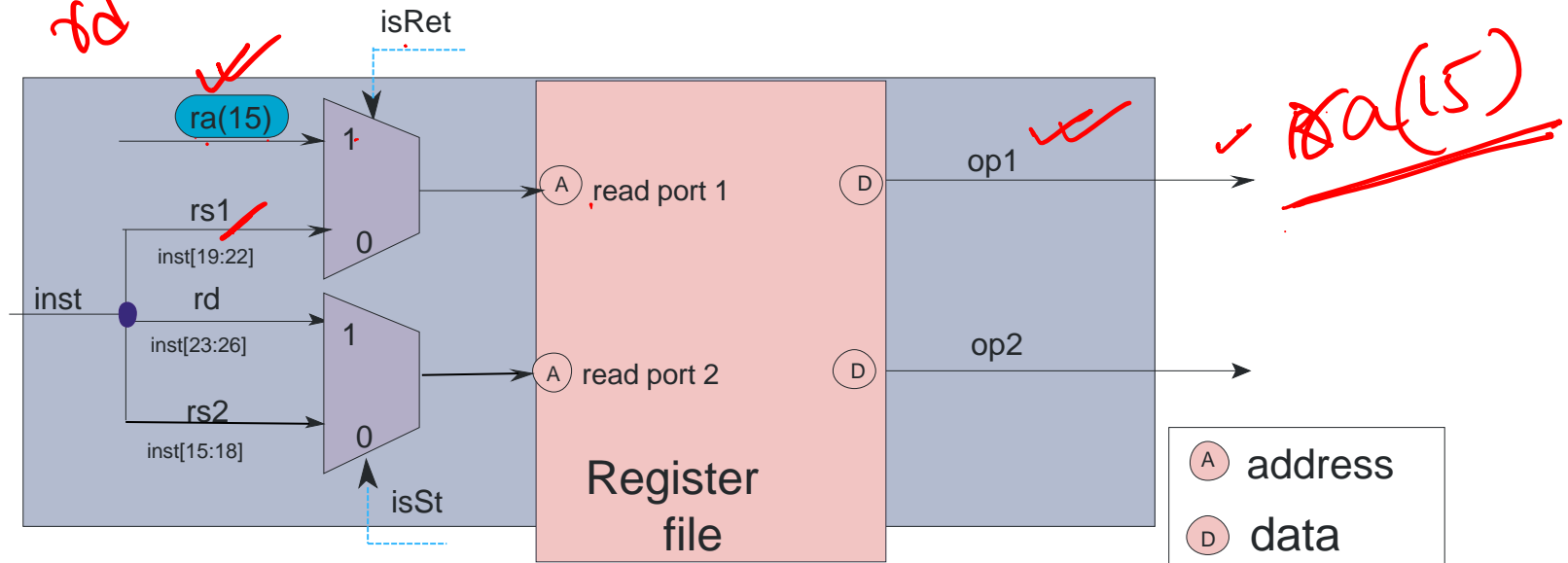


- * **First input** → *rs1* or *ra(15)* (ret instruction)
- * **Second input** → *rs2* or *rd* (store instruction)

Immediate and Branch Unit

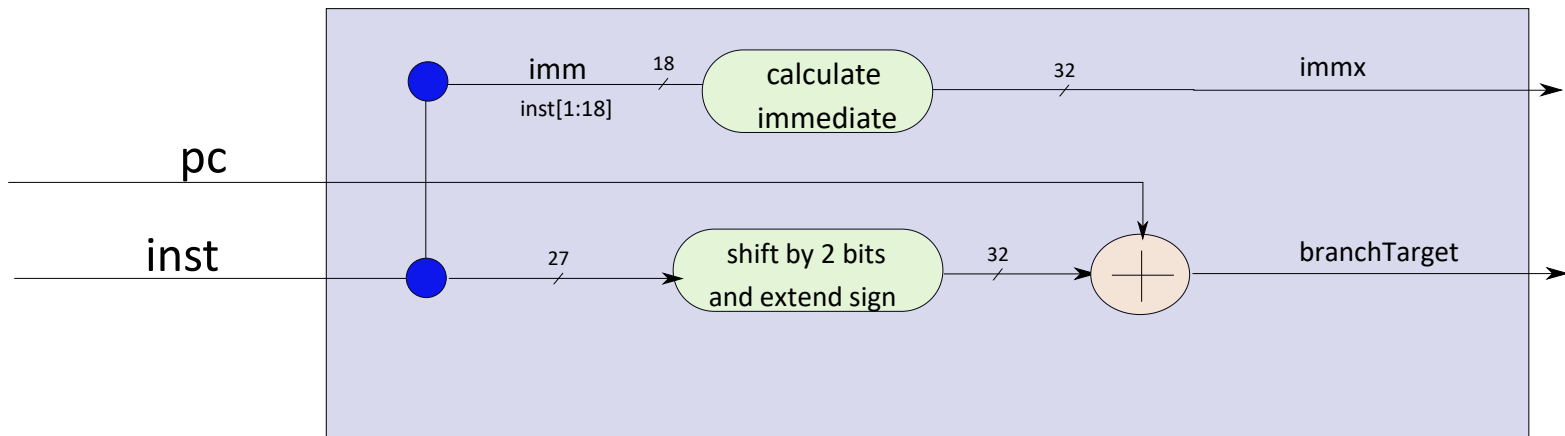


- * Compute **immx** (extended immediate), **branchTarget**, irrespective of the **instruction format**.
- * For the **branchTarget** we need to choose between the embedded target and op1 (ret)

OF Unit

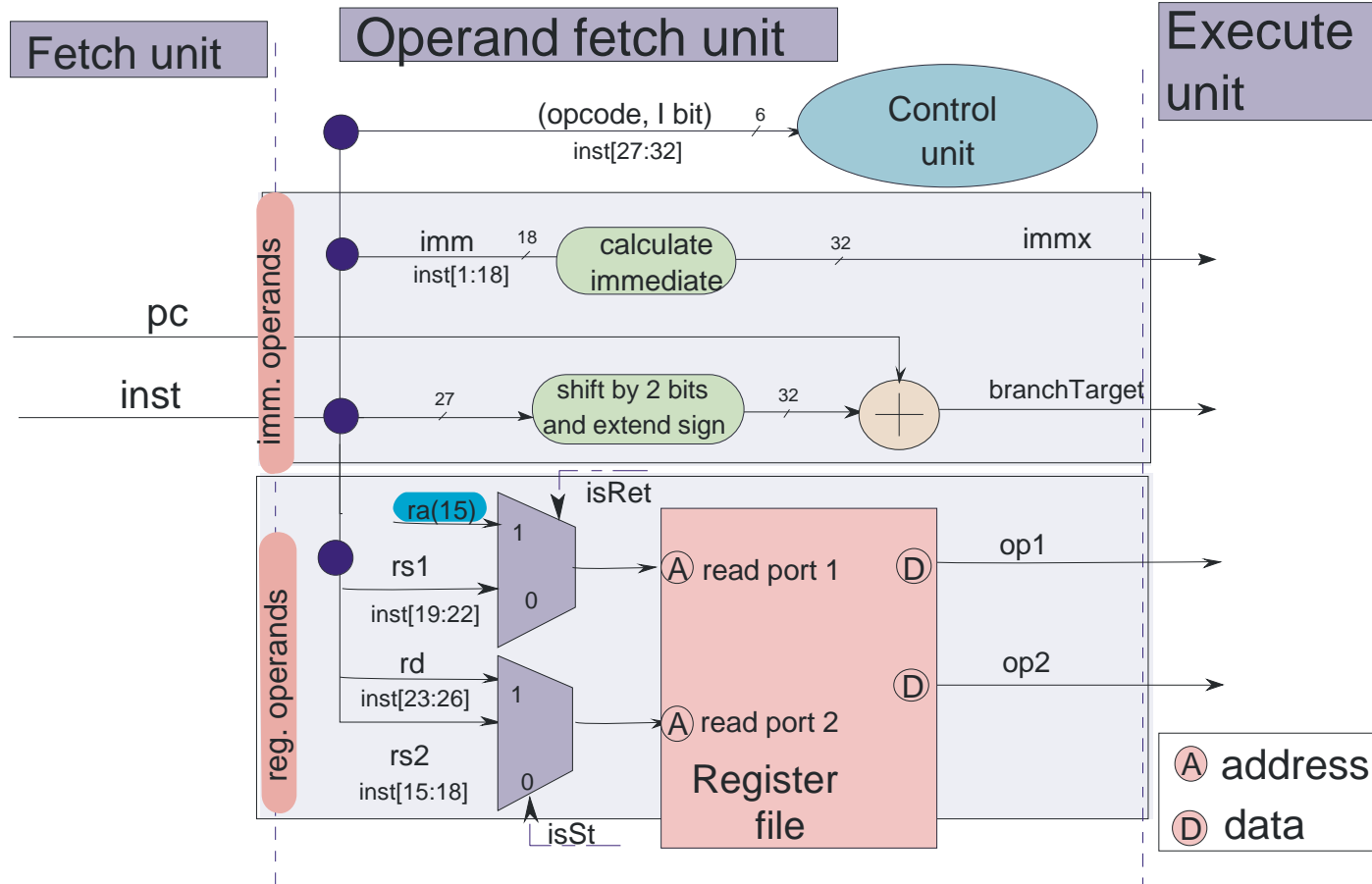


EX Stage – Branch Unit

 


Generates the isBranchTaken Signal

ALU

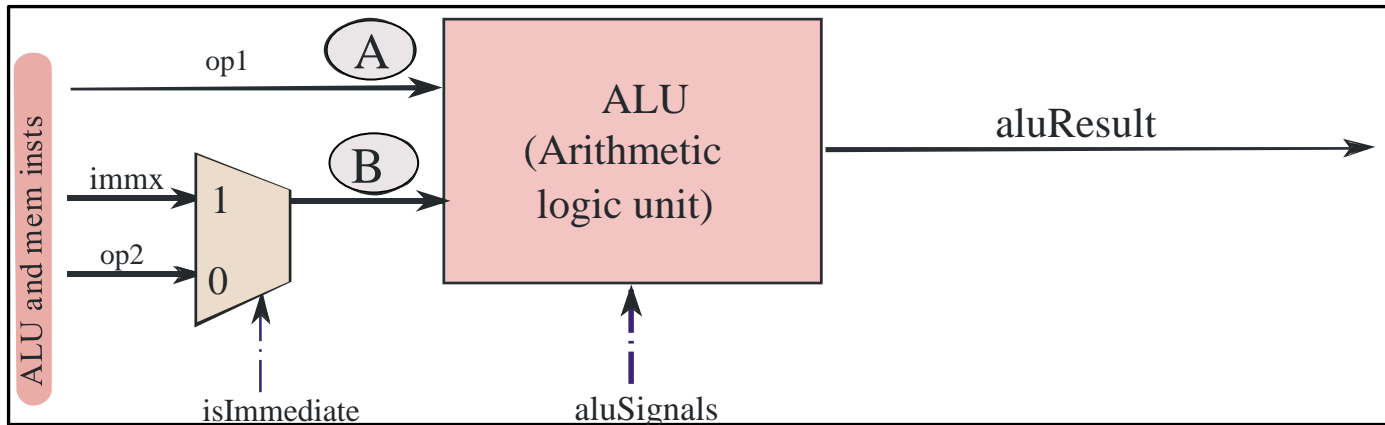


Choose between immx and op2 based on the value of the I bit


Inside the ALU

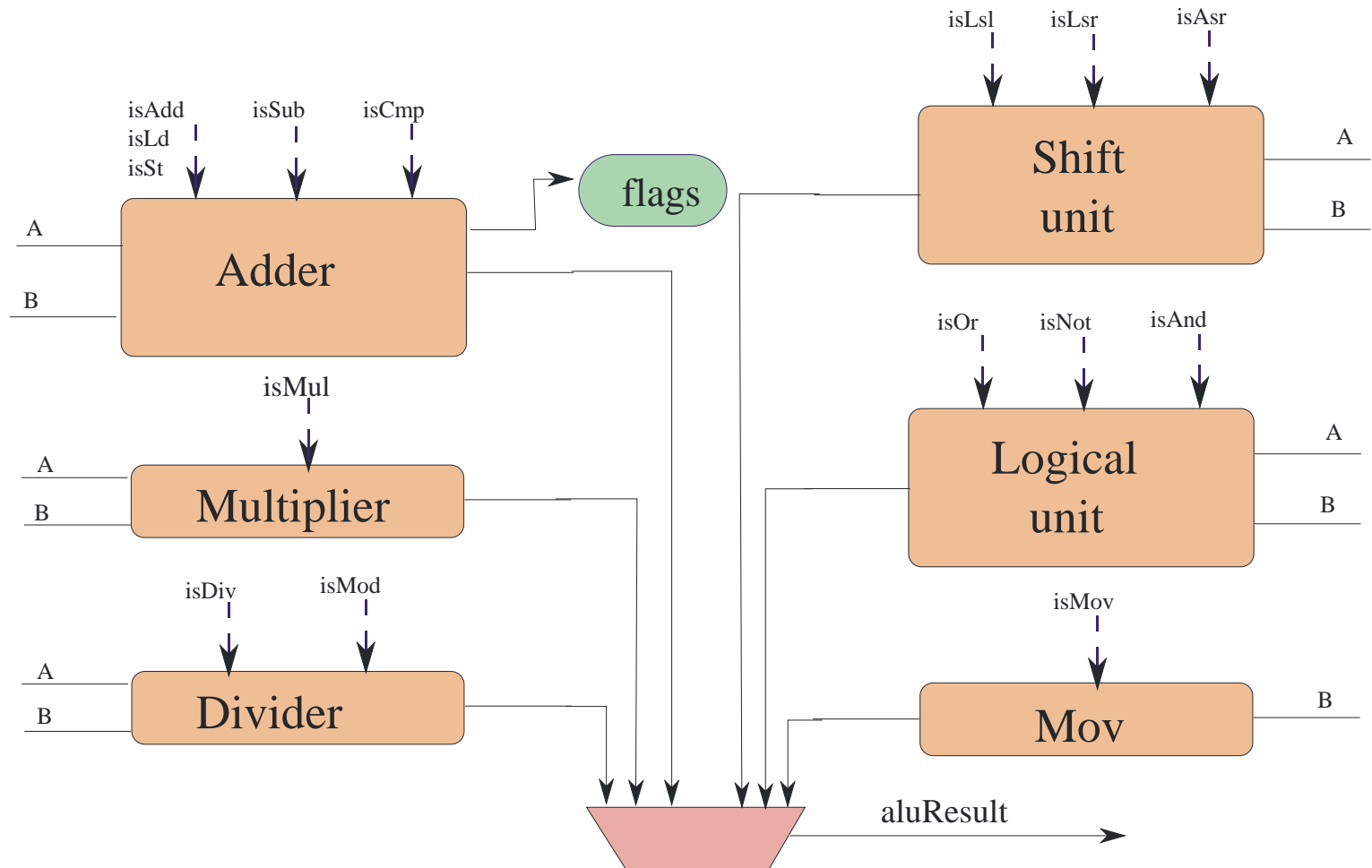


EX Unit

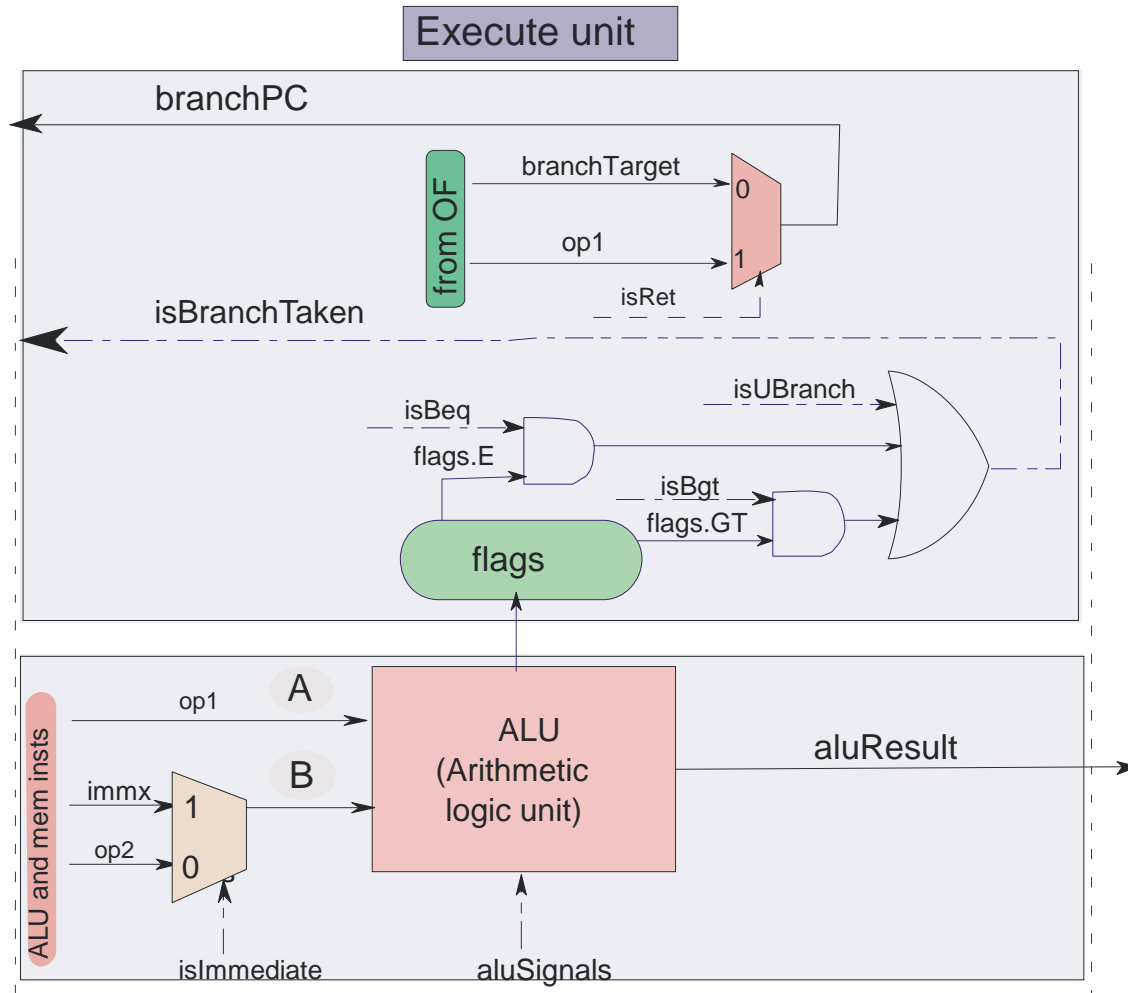


MA Unit

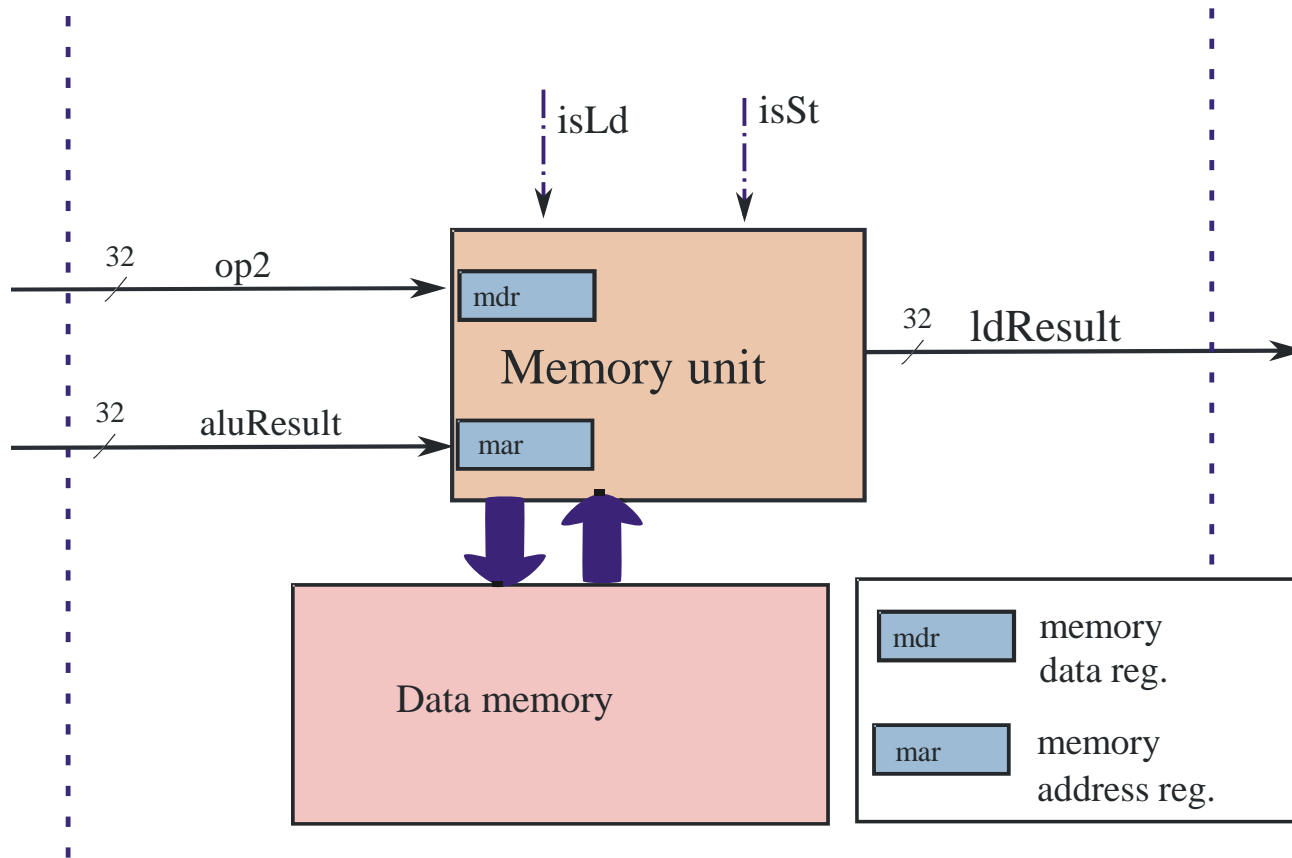


RW Unit

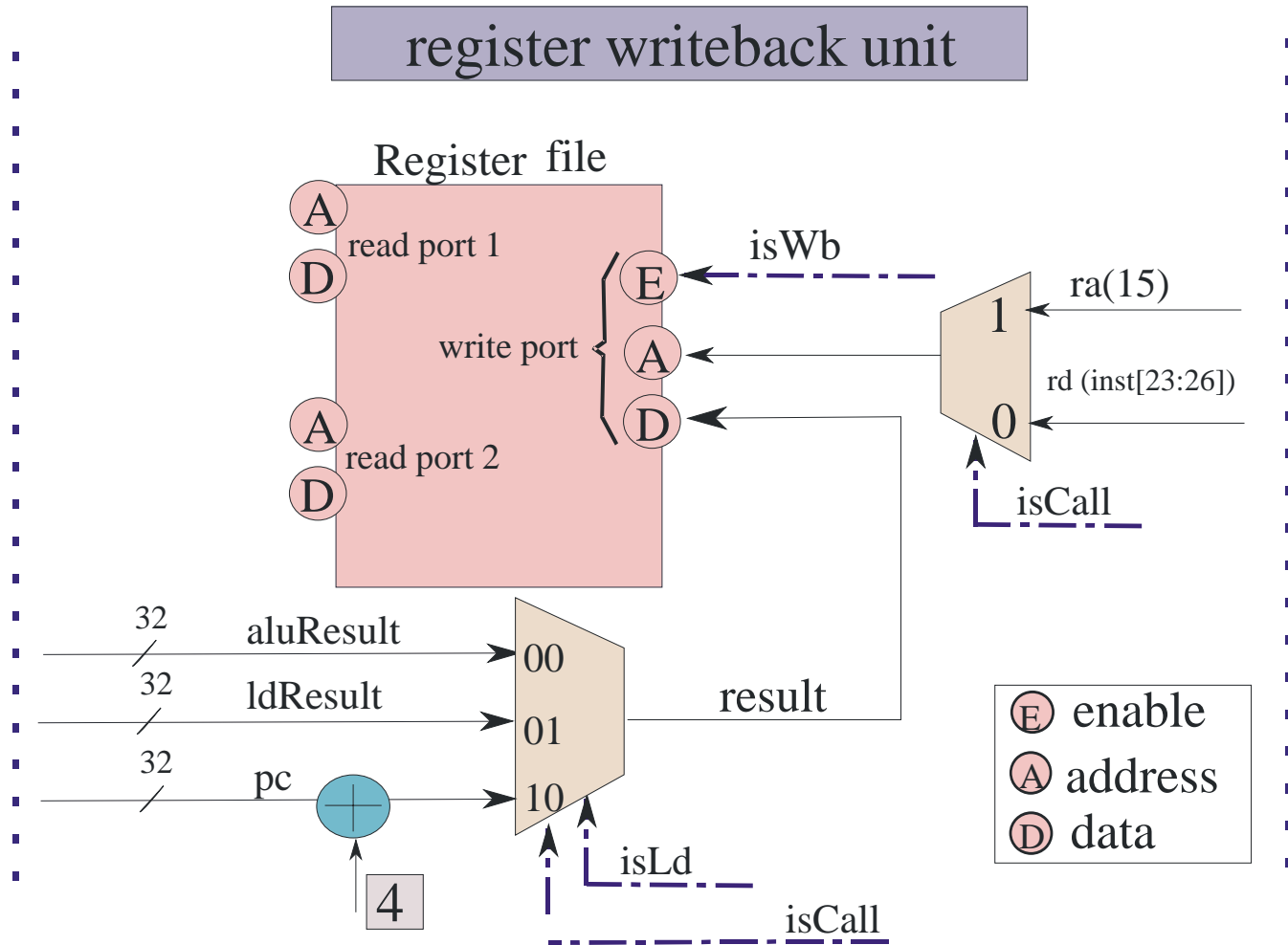

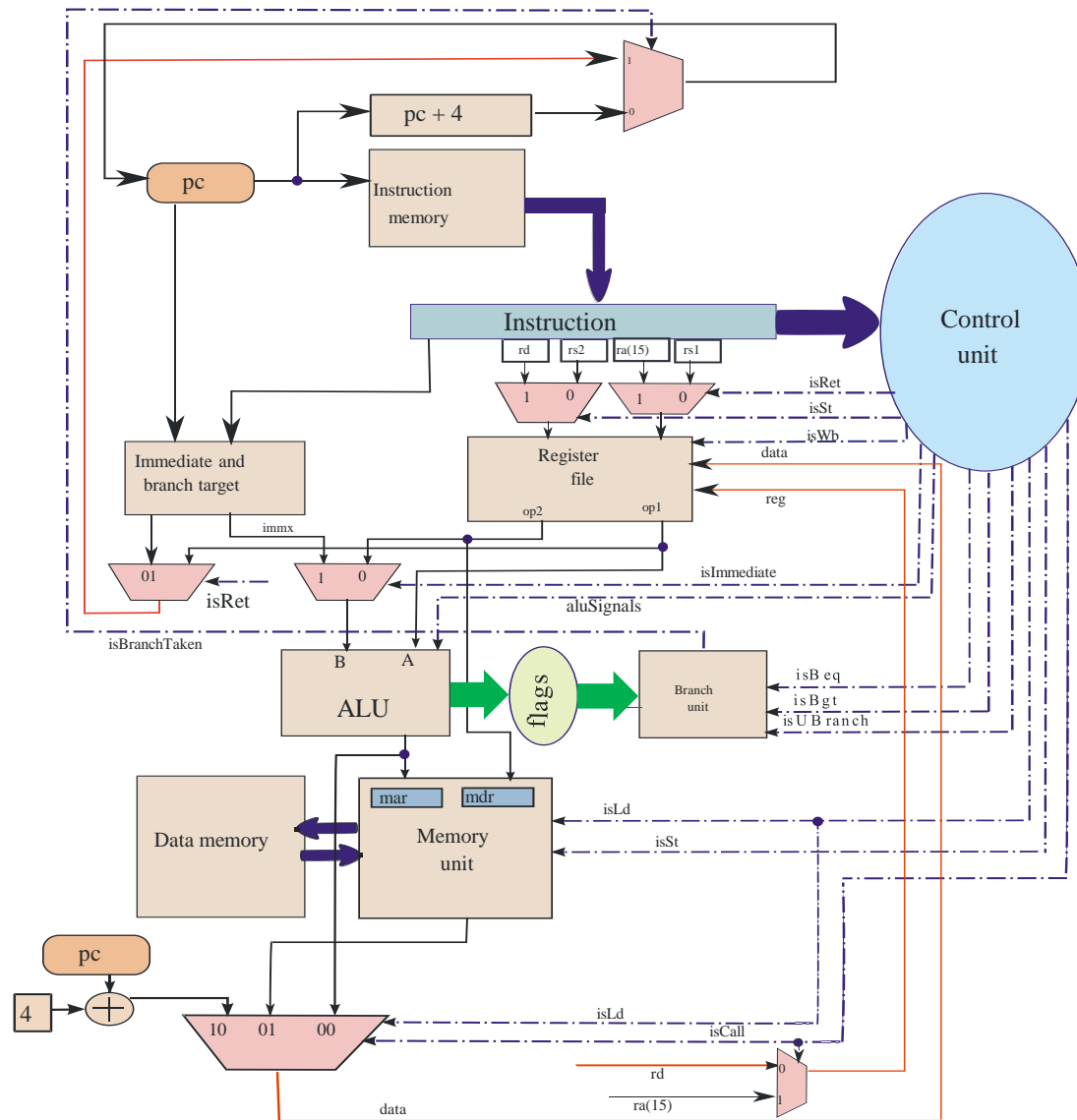

The Hardwired Control Unit

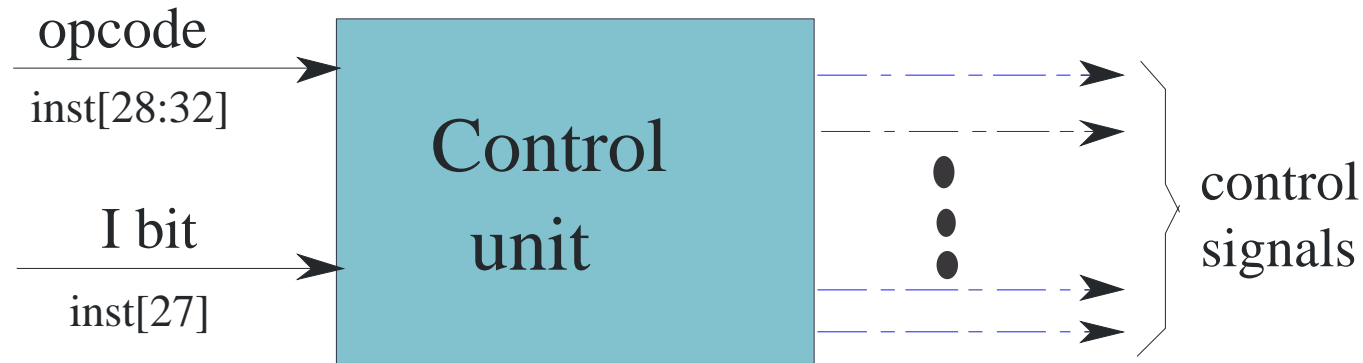

- * Given the **opcode** and the **immediate** bit
 - * It generates all the **control signals**


Control Signals

SerialNo.	Signal	Condition
1	<i>isSt</i>	Instruction: <i>st</i>
2	<i>isLd</i>	Instruction: <i>ld</i>
3	<i>isBeq</i>	Instruction: <i>beq</i>
4	<i>isBgt</i>	Instruction: <i>bgt</i>
5	<i>isRet</i>	Instruction: <i>ret</i>
6	<i>isImmediate</i>	<i>I</i> bit set to 1
7	<i>isWb</i>	Instructions: <i>add, sub, mul, div, mod, and, or, not, mov, ld, lsl, lsr, asr, call</i>
8	<i>isUBranch</i>	Instructions: <i>b, call, ret</i>
9	<i>isCall</i>	Instructions: <i>call</i>

Control Signals – II

<i>aluSignal</i>		
10	<i>isAdd</i>	Instructions: <i>add, ld, st</i>
11	<i>isSub</i>	Instruction: <i>sub</i>
12	<i>isCmp</i>	Instruction: <i>cmp</i>
13	<i>isMul</i>	Instruction: <i>mul</i>
14	<i>isDiv</i>	Instruction: <i>div</i>
15	<i>isMod</i>	Instruction: <i>mod</i>
16	<i>isLsl</i>	Instruction: <i>lsl</i>
17	<i>isLsr</i>	Instruction: <i>lsr</i>
18	<i>isAsr</i>	Instruction: <i>asr</i>
19	<i>isOr</i>	Instruction: <i>or</i>
20	<i>isAnd</i>	Instruction: <i>and</i>
21	<i>isNot</i>	Instruction: <i>not</i>
22	<i>isMov</i>	Instruction: <i>mov</i>

Control signal Logic

 

Serial No.	Signal	Condition
1	<i>isSt</i>	$\overline{op_5} \cdot \overline{op_4} \cdot \overline{op_3} \cdot \overline{op_2} \cdot \overline{op_1}$
2	<i>isLd</i>	$\overline{op_5} \cdot \overline{op_4} \cdot \overline{op_3} \cdot \overline{op_2} \cdot \overline{op_1}$
3	<i>isBeq</i>	$op_5 \cdot \overline{op_4} \cdot \overline{op_3} \cdot \overline{op_2} \cdot \overline{op_1}$
4	<i>isBgt</i>	$op_5 \cdot \overline{op_4} \cdot \overline{op_3} \cdot \overline{op_2} \cdot op_1$
5	<i>isRet</i>	$op_5 \cdot \overline{op_4} \cdot op_3 \cdot \overline{op_2} \cdot \overline{op_1}$
6	<i>isImmediate</i>	<i>I</i>
7	<i>isWb</i>	$\sim(op_5 + \overline{op_5} \cdot op_3 \cdot op_1 \cdot (op_4 + \overline{op_2})) + op_5 \cdot \overline{op_4} \cdot \overline{op_3} \cdot \overline{op_2} \cdot op_1$
8	<i>isUbranch</i>	$op_5 \cdot \overline{op_4} \cdot (\overline{op_3} \cdot op_2 + op_3 \cdot \overline{op_2} \cdot \overline{op_1})$
9	<i>isCall</i>	$op_5 \cdot \overline{op_4} \cdot \overline{op_3} \cdot op_2 \cdot op_1$

Control Signal Logic - II

<i>aluSignals</i>		
10	<i>isAdd</i>	$\overline{op5}.\overline{op4}.\overline{op3}.\overline{op2}.\overline{op1} + \overline{op5}.op4.op3.op2$
11	<i>isSub</i>	$\overline{op5}.\overline{op4}.\overline{op3}.\overline{op2}.op1$
12	<i>isCmp</i>	$\overline{op5}.\overline{op4}.op3.\overline{op2}.op1$
13	<i>isMul</i>	$\overline{op5}.\overline{op4}.\overline{op3}.op2.\overline{op1}$
14	<i>isDiv</i>	$\overline{op5}.\overline{op4}.\overline{op3}.op2.op1$
15	<i>isMod</i>	$\overline{op5}.\overline{op4}.op3.\overline{op2}.\overline{op1}$
16	<i>isLsl</i>	$\overline{op5}.op4.\overline{op3}.op2.\overline{op1}$
17	<i>isLsr</i>	$\overline{op5}.op4.\overline{op3}.op2.op1$
18	<i>isAsr</i>	$\overline{op5}.op4.op3.\overline{op2}.\overline{op1}$
19	<i>isOr</i>	$\overline{op5}.\overline{op4}.op3.op2.op1$
20	<i>isAnd</i>	$\overline{op5}.op4.\overline{op3}.op2.\overline{op1}$
21	<i>isNot</i>	$\overline{op5}.op4.\overline{op3}.\overline{op2}.\overline{op1}$
22	<i>isMov</i>	$\overline{op5}.op4.\overline{op3}.\overline{op2}.op1$