

- AND ---- For AND operation on two variables, say  $X$  and  $Y$ , the operation results in 1 if and only if both the variables are 1 and the result is denoted by  $F = X \cdot Y$ , where  $F$  is the result of the operation. If there are more than two variables, then the operation results in 1 iff all the variables are 1, else it will be 0.

true

false

intersection

even numbers  
divisible by 3

- OR ---- For OR operation on two variables, say  $X$  and  $Y$ , the operation results in 1 if and only if both the variables are 0 and the result is denoted by  $F = X + Y$ , where  $F$  is the result of the operation. If there are more than two variables, then the operation results in 0 iff all the variables are 0, else it will be 1.

- NOT ---- For operation on one variable only, say  $X$ . This operation results in 0 if the variable is 1 and results in 1 if the variable is 0 and the result is denoted by  $F = \bar{X}$  or  $F = X'$ , where  $F$  is the result of the operation. This is also called complementing and  $F$  is called the logical complement of  $X$ .


0 → 1

1 → 0


- We can combine gates into fancier combinational circuits such as the multiplexer. This device allows us to steer **any one of a number of inputs to a single output.**

universal  
gates  
Basic  
gates


# Logic Function (through examples)

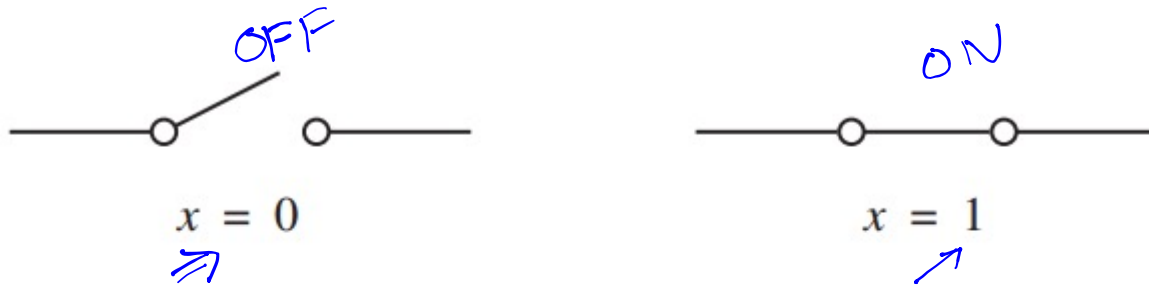


Two states of a switch

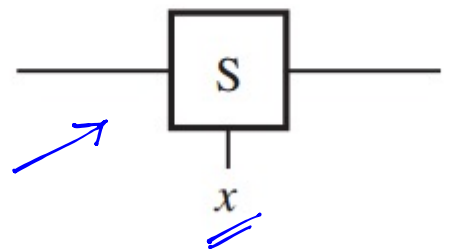

Symbol for a switch

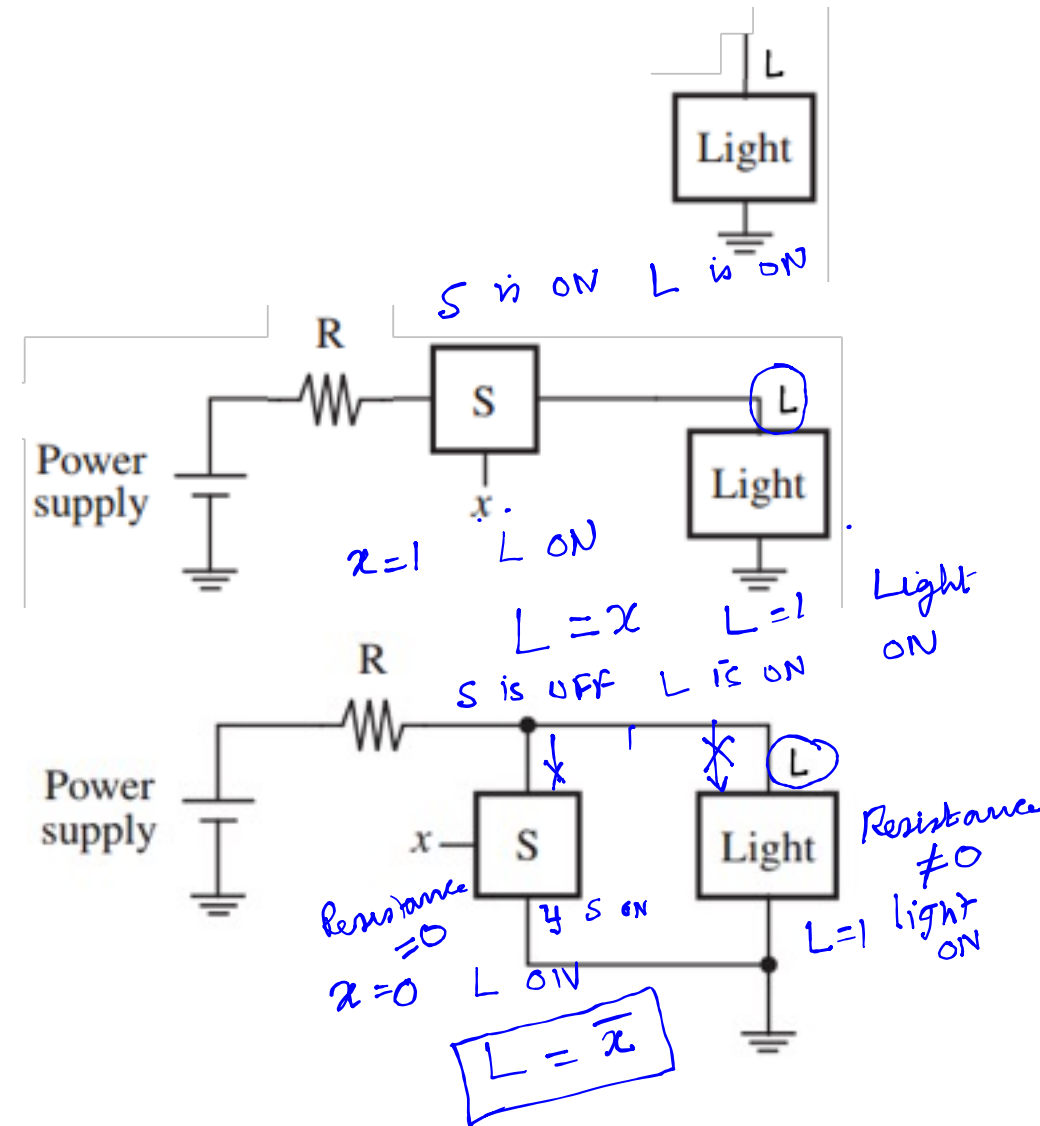


# Boolean Expression

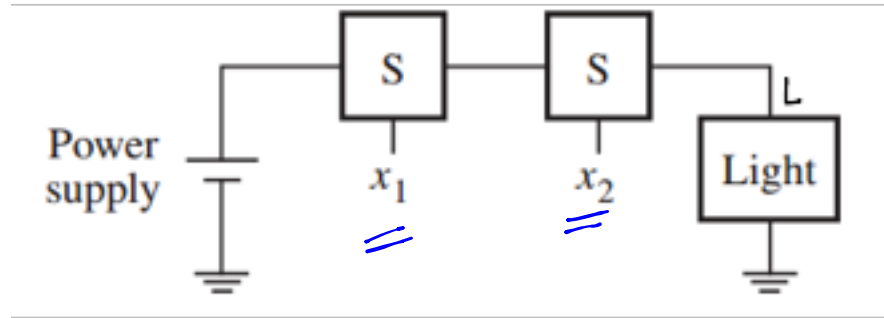

Intersection ( $\cap$ )  $L = x_1 \cdot x_2$

AND ( $\cdot$ )


*logical function*

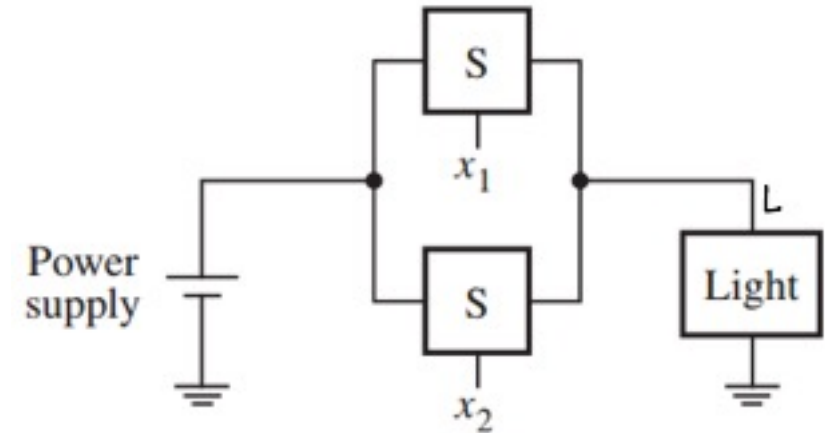

Union ( $\cup$ )  $L = x_1 + x_2$


OR ( $+$ )

$$(x_1 + x_2) \cdot x_3 = L$$

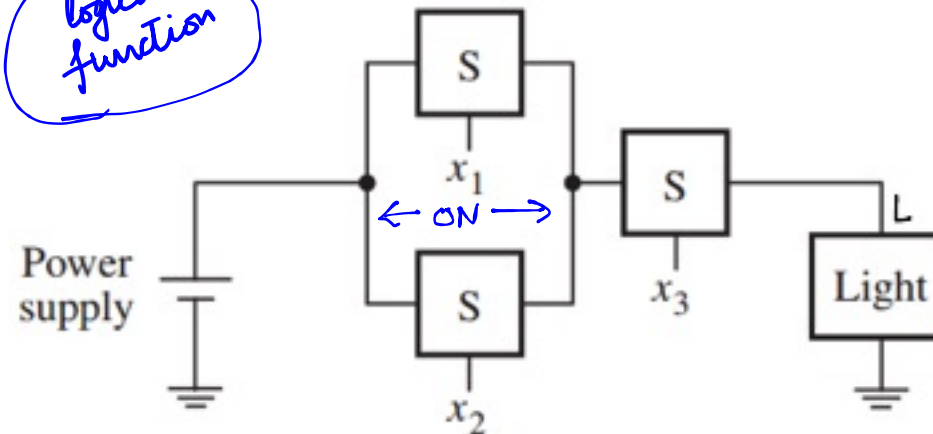


Combination of AND and OR

# Boolean Expression

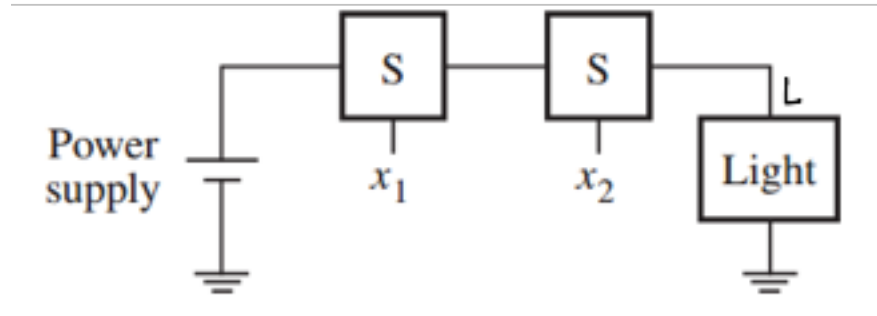

$$L = x_1 \cdot x_2$$

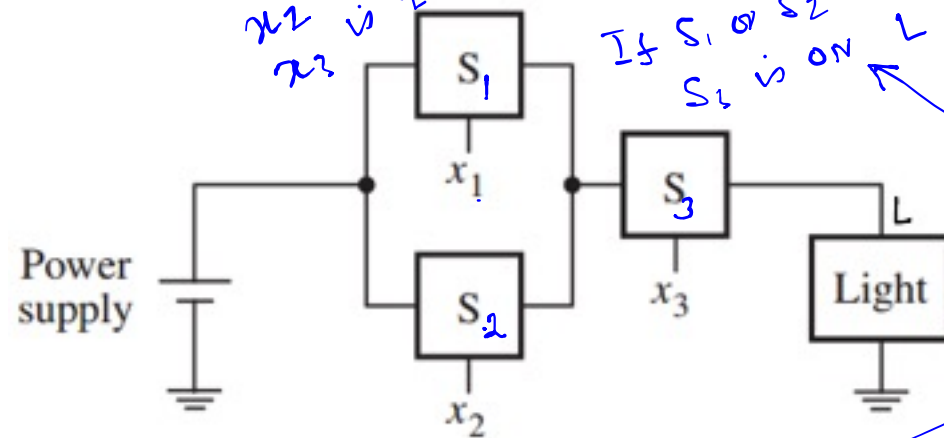*x<sub>1</sub> is 1 S<sub>1</sub> is ON  
x<sub>2</sub> is 1 S<sub>2</sub> is ON  
x<sub>3</sub> is 1 S<sub>3</sub> is ON*



*If S<sub>1</sub> or S<sub>2</sub> is ON and S<sub>3</sub> is ON L will be ON*

$$L = x_1 + x_2$$

*"If x<sub>1</sub> or x<sub>2</sub> is 1 and x<sub>3</sub> is 1 Light will be on!"*

$$L = (x_1 + x_2) \cdot x_3$$

*in logic form*

- AND ---- For AND operation on two variables, say  $X$  and  $Y$ , the operation results in 1 if and only if both the variables are 1 and the result is denoted by  $F = X \cdot Y$ , where  $F$  is the result of the operation. If there are more than two variables, then the operation results in 1 iff all the variables are 1, else it will be 0.
- OR ---- For OR operation on two variables, say  $X$  and  $Y$ , the operation results in 0 if and only if both the variables are 0 and the result is denoted by  $F = X + Y$ , where  $F$  is the result of the operation. If there are more than two variables, then the operation results in 0 iff all the variables are 0, else it will be 1.
- NOT ---- For operation on one variable only, say  $X$ . This operation results in 0 if the variable is 1 and results in 1 if the variable is 0 and the result is denoted by  $F = \bar{X}$  or  $F = X'$ , where  $F$  is the result of the operation. This is also called complementing and  $F$  is called the logical complement of  $X$ .
- We can combine gates into fancier combinational circuits such as the multiplexer. This device allows us to steer **any one of a number of inputs to a single output.**

# Basic Logic Gates


Institute of  
Electrical &  
Electronics Engineering  
for  
Information  
Recommended

Name	Symbol	IEEE	Logical Function	Truth Table															
NOT			$Z = \overline{x_1}$	<table><tr><td><math>x_1</math></td><td><math>Z</math></td></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table> <p>for Inverter</p>	$x_1$	$Z$	0	1	1	0									
$x_1$	$Z$																		
0	1																		
1	0																		
AND			$Z = x_1 \cdot x_2$	<table><tr><td><math>x_1</math></td><td><math>x_2</math></td><td><math>Z</math></td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table> <p>Truth Table for AND</p>	$x_1$	$x_2$	$Z$	0	0	0	0	1	0	1	0	0	1	1	1
$x_1$	$x_2$	$Z$																	
0	0	0																	
0	1	0																	
1	0	0																	
1	1	1																	
OR			$Z = x_1 + x_2$	<table><tr><td><math>x_1</math></td><td><math>x_2</math></td><td><math>Z</math></td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table> <p>for OR</p>	$x_1$	$x_2$	$Z$	0	0	0	0	1	1	1	0	1	1	1	1
$x_1$	$x_2$	$Z$																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	1																	

# Truth Table: Positive Logic Function vs. Negative Logic Function


TT

$x_1$	$x_2$	$z$
0	0	0 $\rightarrow 1$
0	1	0 $\rightarrow 1$
1	0	0 $\rightarrow 1$
1	1	1 $\rightarrow 0$

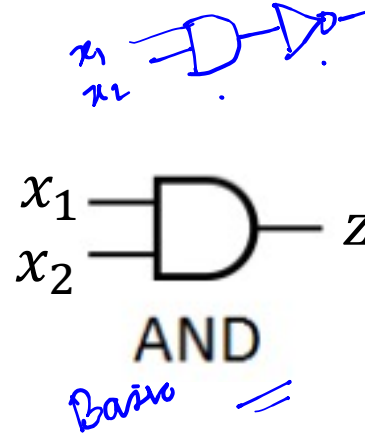


AND followed by NOT

$x_1$	$x_2$	$z$
0	0	1
0	1	1
1	0	1
1	1	0

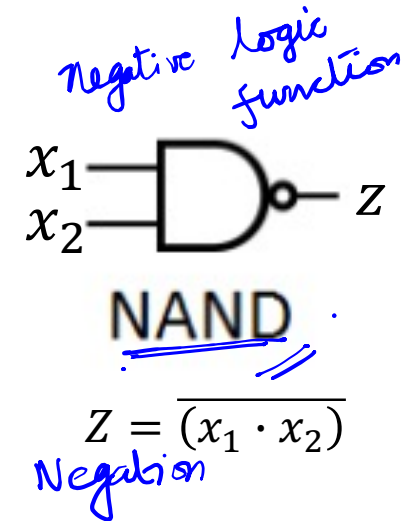


$x_1$	$x_2$	$z$
0	0	0
0	1	1
1	0	1
1	1	1

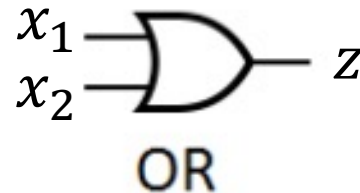

OR followed by NOT

$x_1$	$x_2$	$z$
0	0	1
0	1	0
1	0	0
1	1	0

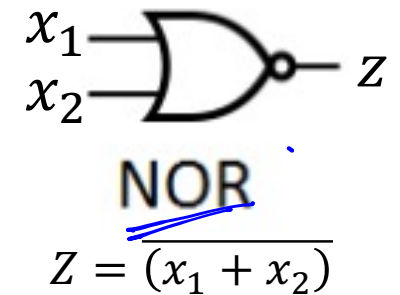



# Positive and Negative Logic Symbol:

**Positive Logic**

AND

$x_1$	$x_2$	$Z$
0	0	0
0	1	0
1	0	0
1	1	1

**Negative Logic**

AND

$x_1$	$x_2$	$Z$
0	0	0
0	1	0
1	0	0
1	1	1

**Logic Function Equivalences:**

- $x_1 \cdot x_2 = \overline{\overline{x_1} + \overline{x_2}}$  (De Morgan's Law)
- $\overline{x_1 \cdot x_2} = \overline{x_1} + \overline{x_2}$  (NAND is OR with inverted inputs)
- $\overline{\overline{x_1} + \overline{x_2}} = x_1 \cdot x_2$  (NOR is AND with inverted inputs)

**Handwritten Notes:**

- Symbol** → +ve & -ve
- Logic function** → +ve & -ve
- gate merged** → +ve & -ve
- older**