

H. W. --- Will discuss in the next class if you are not able to solve it.

A student staying in a hostel has to make up his mind about his dinner. If he has enough money (M) and at least three of his friends (F) also agree to go out for dinner, and it is not raining (R), he will have dinner with his friends in a restaurant outside the campus. If he is not able to go out, but at least three of his friends agree to join him (J), if the kind of food he wanted is available on home delivery (K) he will order home delivery of food from outside. **But if the general feeling is that the food in the hostel mess is good on that day (G),** he will have his dinner in the hostel mess.

Let his decision be denoted by a 2-bit output D_1D_0 :

$D_1D_0 = 00 \Rightarrow$ He eats in the hostel mess, $D_1=1$ home delivery, $D_0=0$ go out

$D_1D_0 = 01 \Rightarrow$ He goes out to have dinner in a restaurant, and

$D_1D_0 = 10 \Rightarrow$ He orders food through home delivery.

$D_0 = \overline{M} \cdot \overline{F} \cdot \overline{R} \cdot \overline{G}$ $D_1 = (\overline{M} + \overline{F} + \overline{R}) \cdot J \cdot K \cdot \overline{G}$

$R=1$ not raining

$D_0 = D_1 = 1$
never happens

practice problems
not there in mpsu.
statement to logic

Binary Addition:

$$X = x_4 x_3 x_2 x_1 x_0 = 01111$$

$$Y = y_4 y_3 y_2 y_1 y_0 = 01010$$

Find:

$$\text{Sum } S = \overset{1}{s_4} \overset{1}{s_3} \overset{0}{s_2} \overset{1}{s_1} \overset{1}{s_0} \text{ and}$$

$$\text{Carry } C = c_5, c_4, c_3, c_2 \text{ and } c_1$$

$\begin{matrix} 0 & 1 & 1 & 1 & & 0 \end{matrix}$

in hardware

C	$c_5 \leftarrow c_4$	carry forward
X	$c_5 \leftarrow 0$	$z_0 + y_0$
Y	01111	↓
S	+01010	c_i
11001		
$s_4 \ s_3 \ s_2 \ s_1 \ s_0$		

$$\begin{aligned}
 &1 \times 2^0 + 1 \times 2^0 \\
 &= 2 \times 2^0 \\
 &\rightarrow = 2^1 \\
 &1 \times 2^1 + 0 \times 2^0
 \end{aligned}$$


HA (single bit) and FA (multi-bit)

$$c \oplus (x \oplus y) = (c \oplus x) \oplus y = c \oplus x \oplus y$$

2 variables

x	y	Carry c	Sum s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

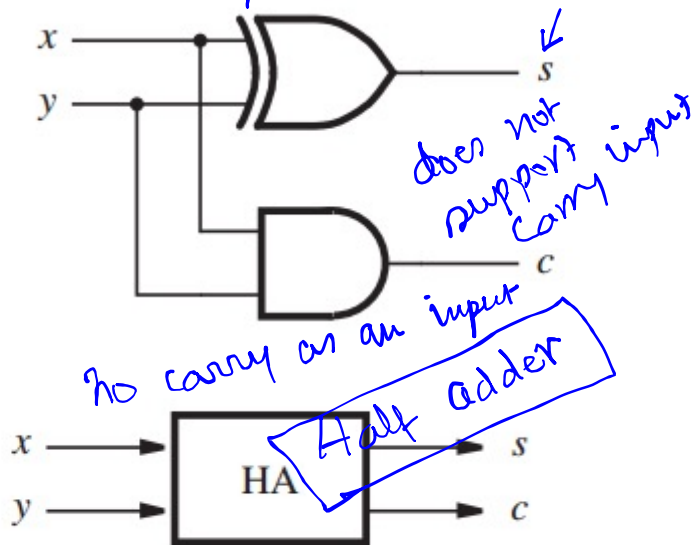Handwritten notes:
 c_4, c_3, c_2, c_1, c_0
 x_4, x_3, x_2, x_1, x_0
 y_4, y_3, y_2, y_1, y_0
 $x \oplus y$




Generated carries $\rightarrow 1110$

$$\begin{array}{r} X = x_4x_3x_2x_1x_0 \\ + Y = y_4y_3y_2y_1y_0 \\ \hline S = s_4s_3s_2s_1s_0 \end{array}$$

...	c_{i+1}	c_i	...
...	...	x_i	...
...	...	y_i	...
...	...	s_i	...



c_i	x_i	y_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

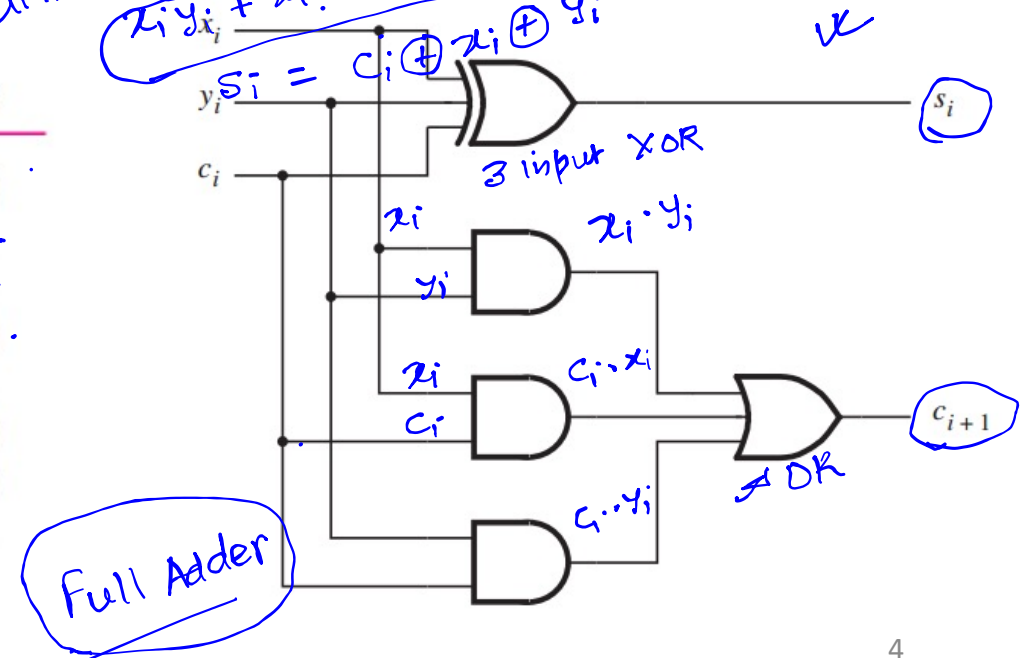Handwritten notes:
 minimised SOP
 $x_i y_i + x_i c_i + y_i c_i = c_{i+1}$
 $s_i = c_i \oplus x_i \oplus y_i$



HA (single bit) and FA (multi-bit):

x	y	Carry c	Sum s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

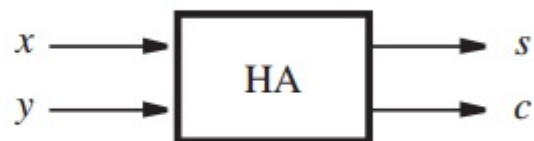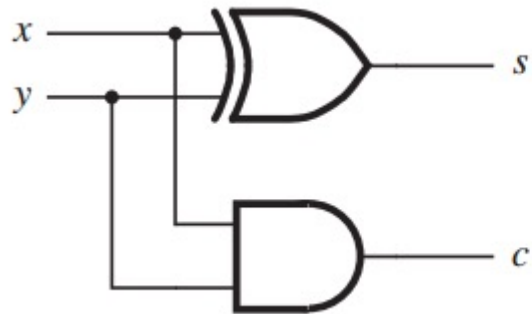

$$c_{i+1} = \bar{c}_i \cdot x_i \cdot y_i + c_i \cdot \bar{x}_i \cdot y_i + c_i \cdot x_i \cdot \bar{y}_i + c_i \cdot x_i \cdot y_i \rightarrow \text{CSOP}$$


Handwritten notes: Blue arrows point from the first three terms to the final simplified equation. A blue arrow points from the last term to the text 'less power faster'.

$$c_{i+1} = x_i \cdot y_i + c_i \cdot (\bar{x}_i \cdot y_i + x_i \cdot \bar{y}_i)$$

Handwritten notes: Blue underlines are under $x_i \cdot y_i$ and $(\bar{x}_i \cdot y_i + x_i \cdot \bar{y}_i)$.


$$c_{i+1} = x_i \cdot y_i + c_i \cdot (x_i \oplus y_i)$$

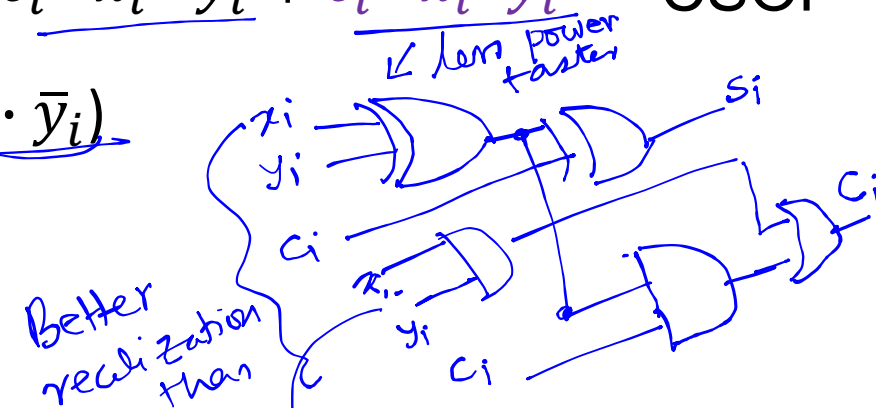Handwritten notes: Blue underlines are under $x_i \cdot y_i$ and $(x_i \oplus y_i)$.



c_i	x_i	y_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

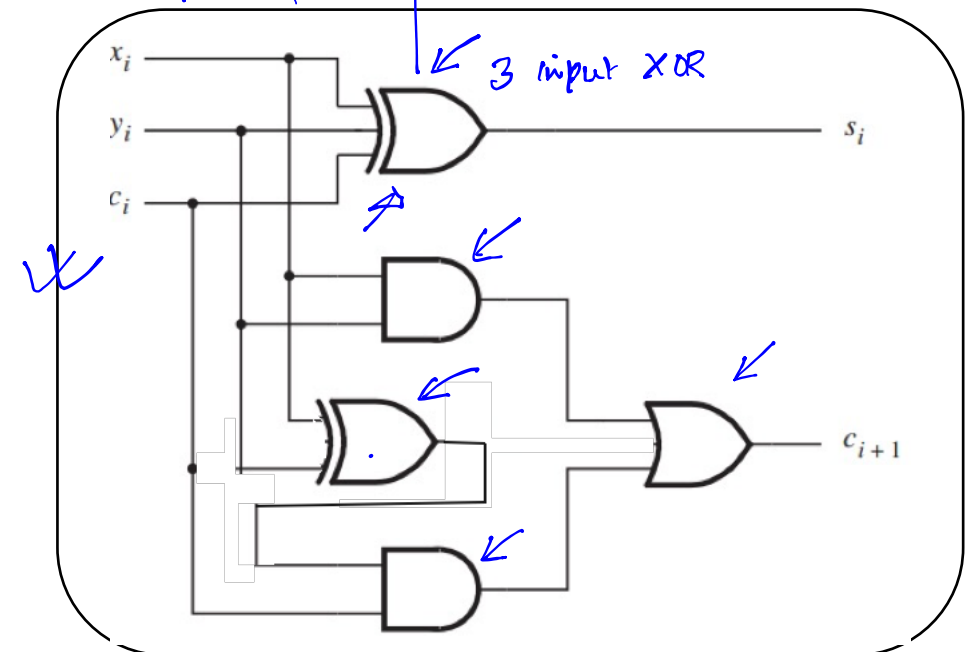
Handwritten notes: Blue arrows point to the rows where $c_i = 0$ and $c_i = 1$.



HA (single bit) and FA (multi-bit)


$$s_i = (x_i \oplus y_i \oplus c_i)$$
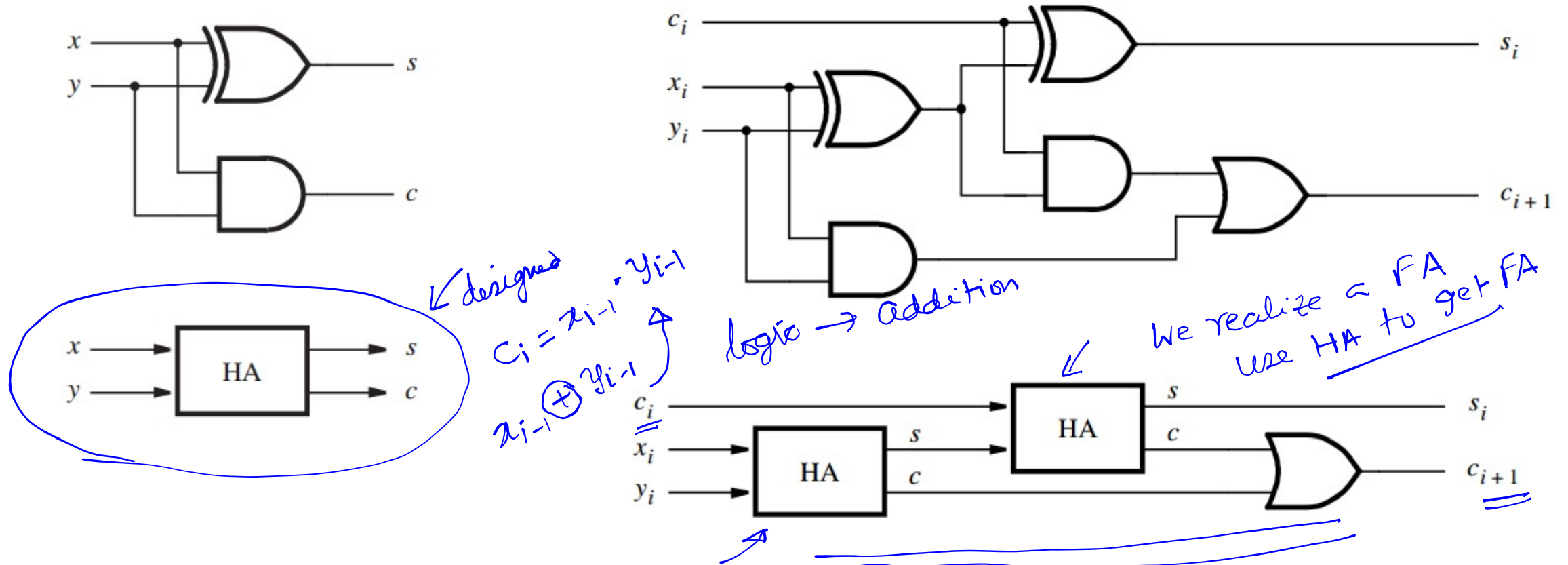
$$c_{i+1} = x_i \cdot y_i + c_i \cdot (x_i \oplus y_i)$$



This approach minimizes the number of ICs needed to implement the circuit, and it reduces the wiring complexity substantially.


4-bit FA Block diagram

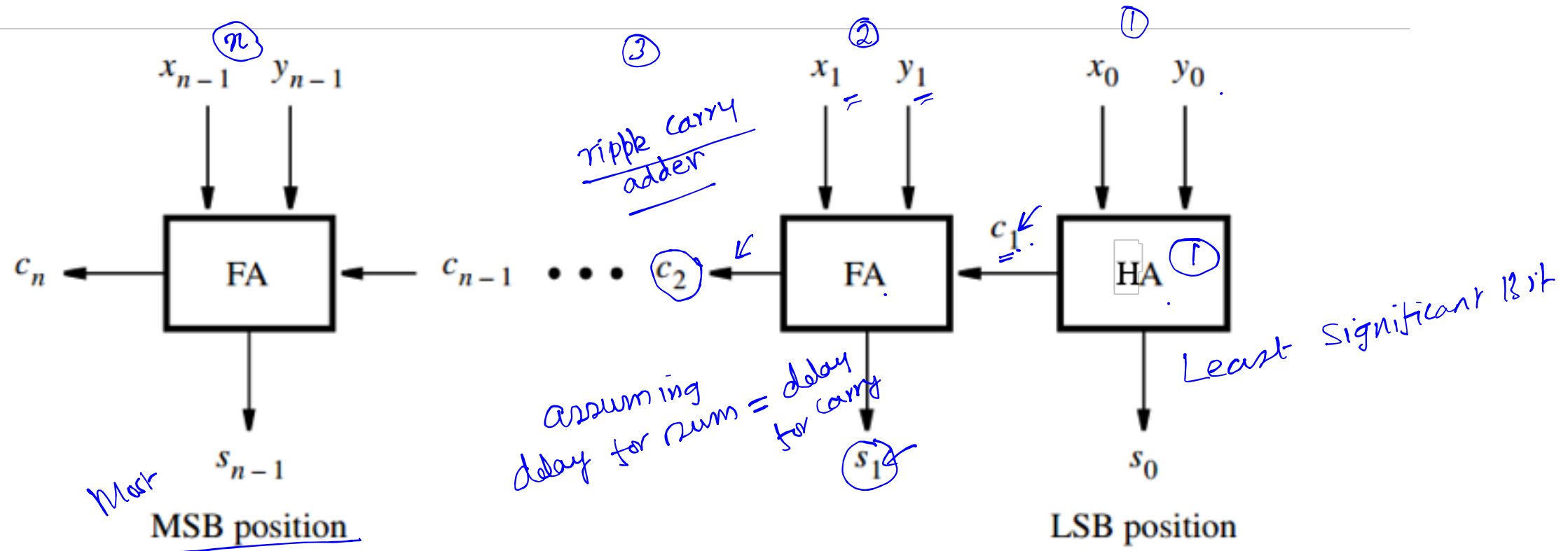

This is called a Ripple Carry Adder. There are other architectures available for an adder and will be a topic in your Computer Organization course next sem.

H.W. Draw a timing diagram for a 3-bit full adder.

unable to draw

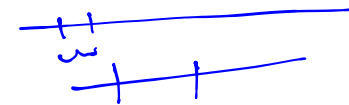

We will look at it in the next class, after you try it. If you try and find it difficult, we will discuss it, else we will spend a little time over what does the timing diagram tell us. If you are not keen on doing the H.W. we will not bother about it at all.

4 bit adder
 $x_3 x_2 x_1 x_0$
 $y_3 y_2 y_1 y_0$

3 bit adder
 $x_2 x_1 x_0$
 $y_2 y_1 y_0$


addition of 4 numbers
 $w_1 w_0$
 $x_1 x_0$
 $y_1 y_0$
 $z_1 z_0$

display solution in the next class in the "length"

1 MHz \rightarrow 1 nsec fast
 \nearrow 1 μ sec \nwarrow
1 GHz. slow
 \nearrow 1 nsec.

Unsigned Numbers (Issues)

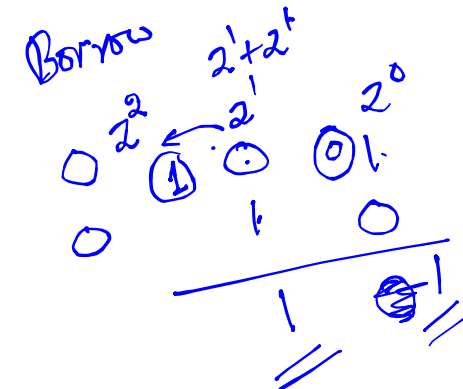- Negative Numbers
- Subtraction when the result is negative
- Separate Circuits for addition and subtraction



$y - x$
 $y + (-x)$

diff. bet. y and x

x	y	D_{yx}	B_{yx}
0	0	0	0
0	1	1	0
1	0	1	1
1	1	0	0

Borrow

$$D_{yx} = x \oplus y; B_{yx} = x \cdot \bar{y}$$

Logic used

Half Subtractor

Sign

$$x - y = x + (-y)$$

same clk. but adjust input

diff. x and y

x	y	D_{xy}	B_{xy}
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Borrow

$$D_{xy} = x \oplus y; B_{xy} = \bar{x} \cdot y$$

B Sign
 4 bit \rightarrow 1 sign bit
 + 3 bit number
 + for sign number
 signed numbers
 01000 \rightarrow 5 bits
 4 bits.
 32 bit
 31
 0 \rightarrow 7
 4 bit

$+4$ familiar -4 negative
representation better

- bit
 - positive
 - negative

not preferred.


exists.

Computer
Organization
13423700
Compare

3425 800
Compare
① store accuracy
sign bits

① Compare magnitude

∴ ② subtract ③ Re insert sign bit

the
-- A 
6 (2 bit)
4 range

$(2^8)^4$
 $(256)^4$
approximation

1. If both the numbers have the same sign, drop the sign bit, add the two numbers and reinsert the sign bit.
256 bit → 64 bit Comp. (2^3)
2. If one is positive and the other is negative, remove the sign bit, *check smaller magnitude* subtract the larger number from the smaller number and then reintroduce the sign of the number with larger magnitude. ---- A very laborious process, hence not preferred.

10