

ECE 113: Basic Electronics

Lecture 2: Voltage and current sources, resistor, Kirchhoff's laws

Dr. Ram Krishna Ghosh, Assistant Professor
Office: B601, Research and Development Block

Email: rkghosh@iiitd.ac.in




INDRAPRASTHA INSTITUTE *of*
INFORMATION TECHNOLOGY
DELHI



Independent and dependent source




Independent source

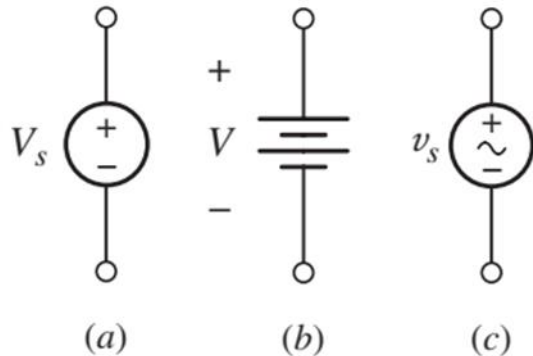


■ **FIGURE 2.16** (a) DC voltage source symbol; (b) battery symbol; (c) ac voltage source symbol.

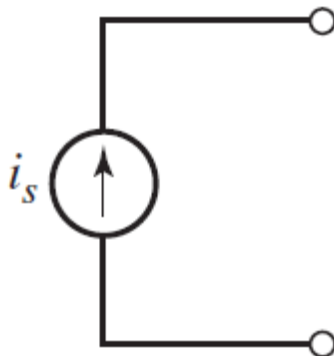Terminal voltage is completely independent of the current



Current is completely independent of the terminal voltage

Dependent source

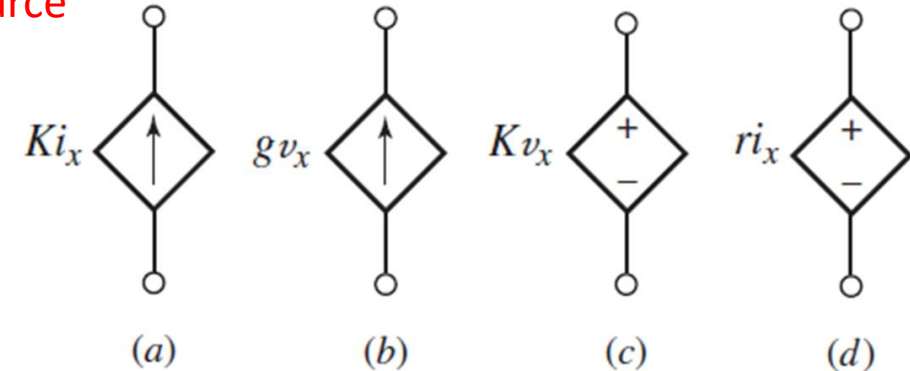

■ **FIGURE 2.18** The four different types of dependent sources: (a) current-controlled current source; (b) voltage-controlled current source; (c) voltage-controlled voltage source; (d) current-controlled voltage source.

K is a dimensionless scaling const. g is a scaling factor with units of A/V and r is a scaling factor with units of V/A

- These are also ideal sources
- Dependent on current or voltage at some other area of the circuit
- Again independent of terminal voltage/current

Networks and Circuits




Circuit: A circuit may be defined as a complete path for electric current flow.

Branch: A group of circuit elements, usually in series, and having two terminals is called a branch of a circuit.

Network: A network is a combination of circuit elements or branches interconnected in some ways.

Mesh or Loop: A loop is any closed path formed by a number of branches in a network. A mesh is the simplest possible closed path.

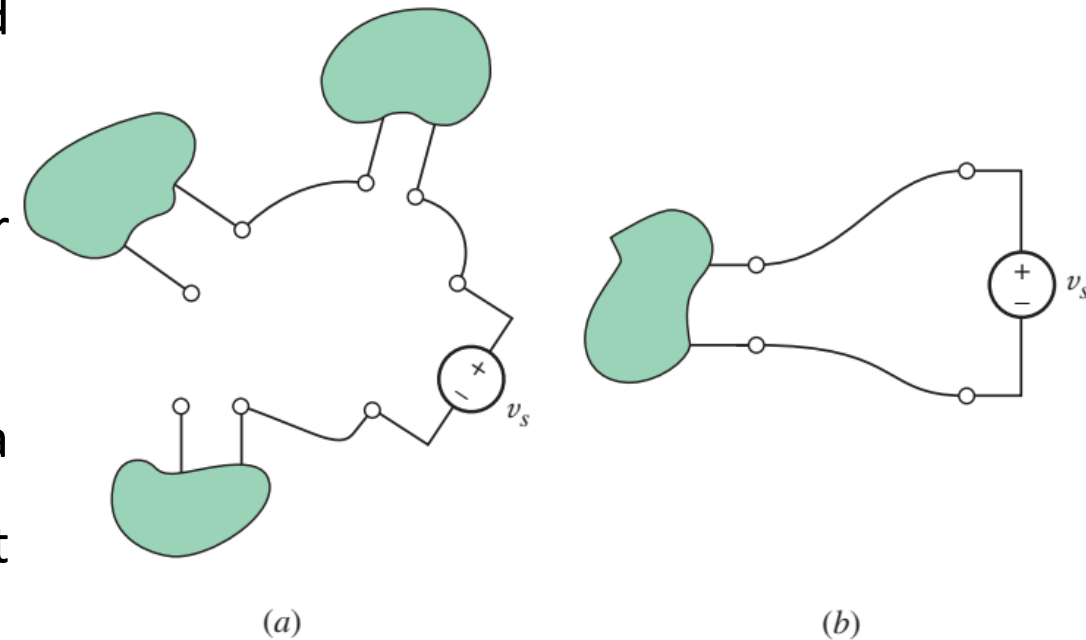Node or junction: A node or junction is simply a common point where two or more circuit components meet.




■ **FIGURE 2.21** (a) A network that is not a circuit. (b) A network that is a circuit.


Networks and Circuits



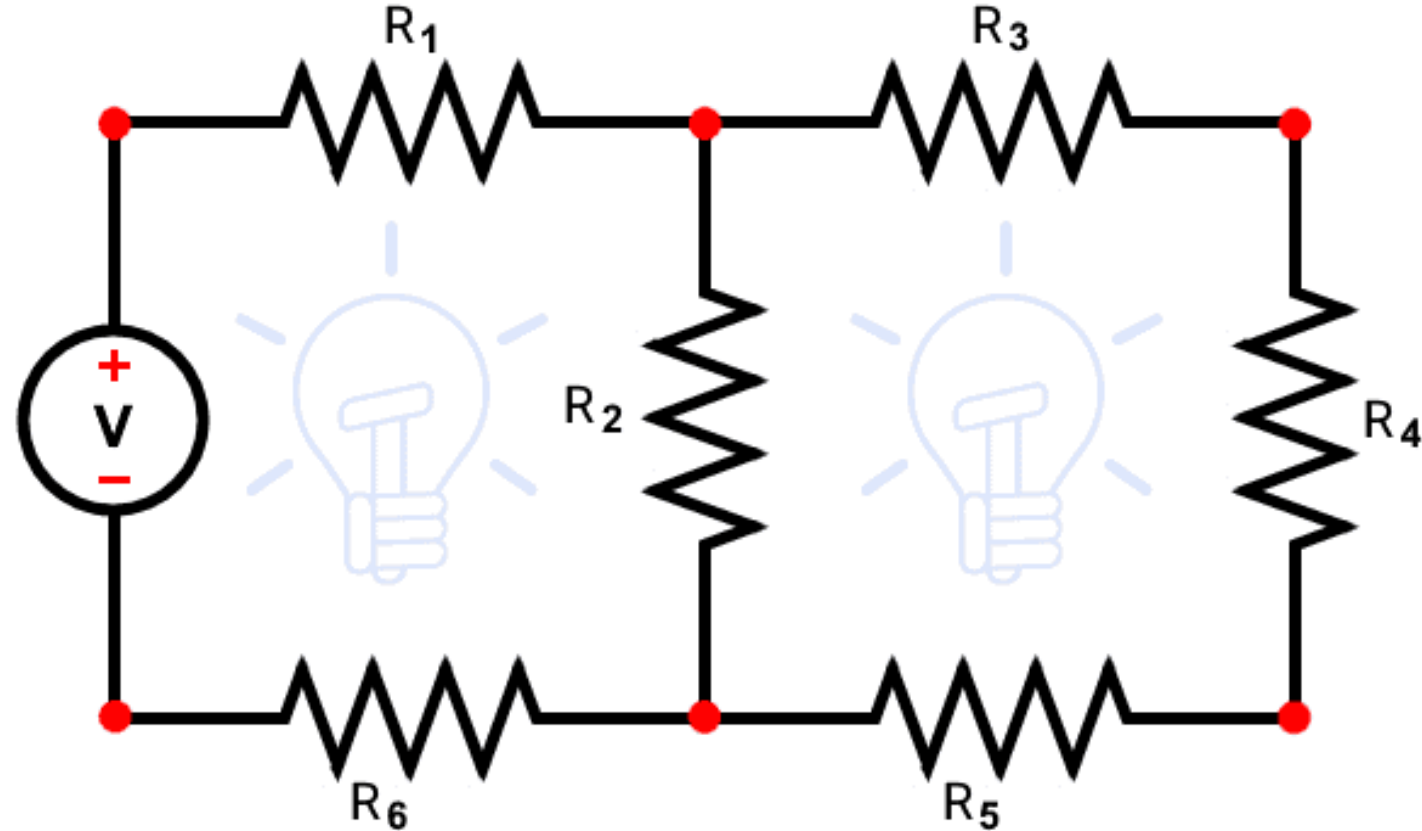
**How to Find the Number of Nodes,
Loops, Branches & Meshes in a Circuit?**




Finding Nodes in a Circuit

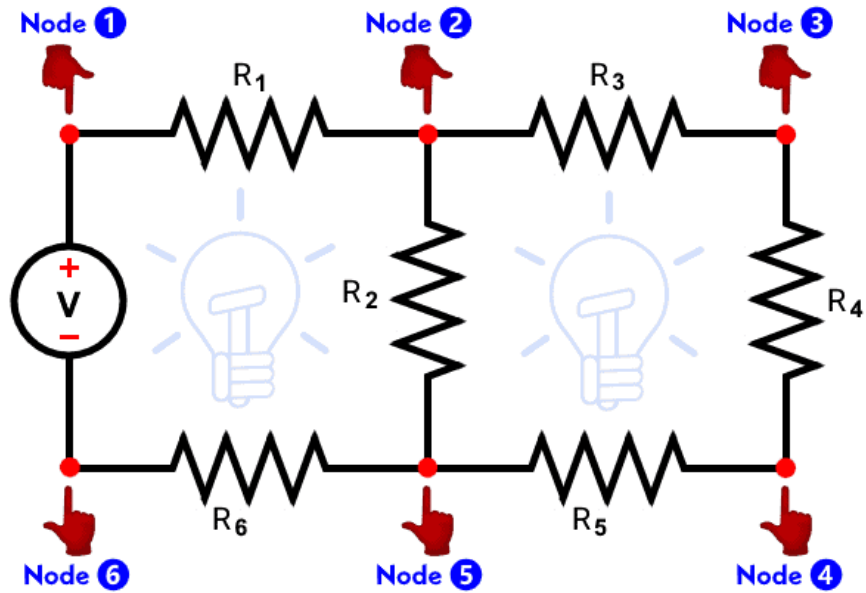


Finding Loops in a Circuit

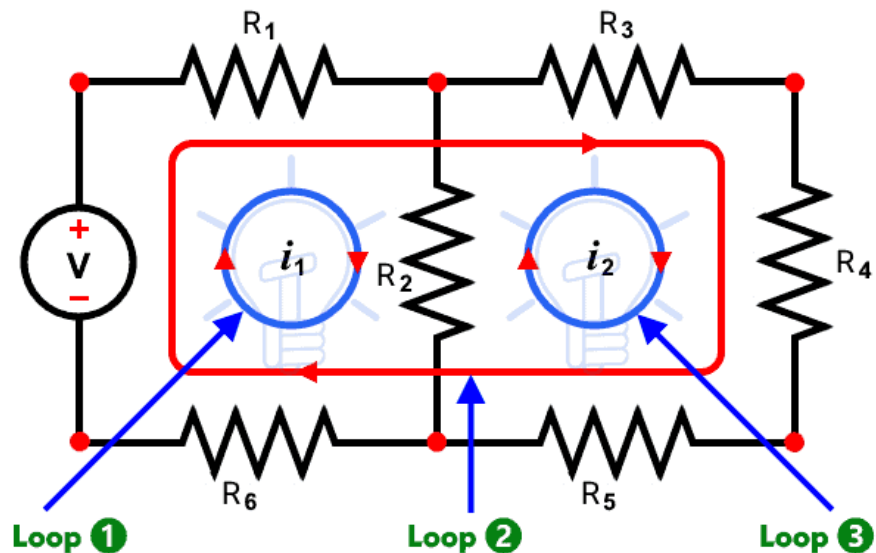


Finding Branches in a Circuit

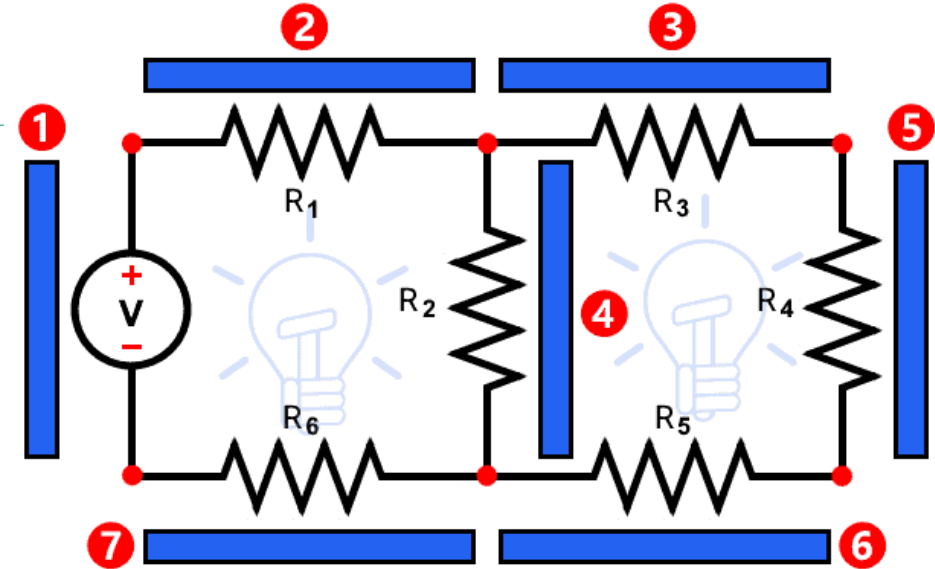

Finding Meshes in a Circuit

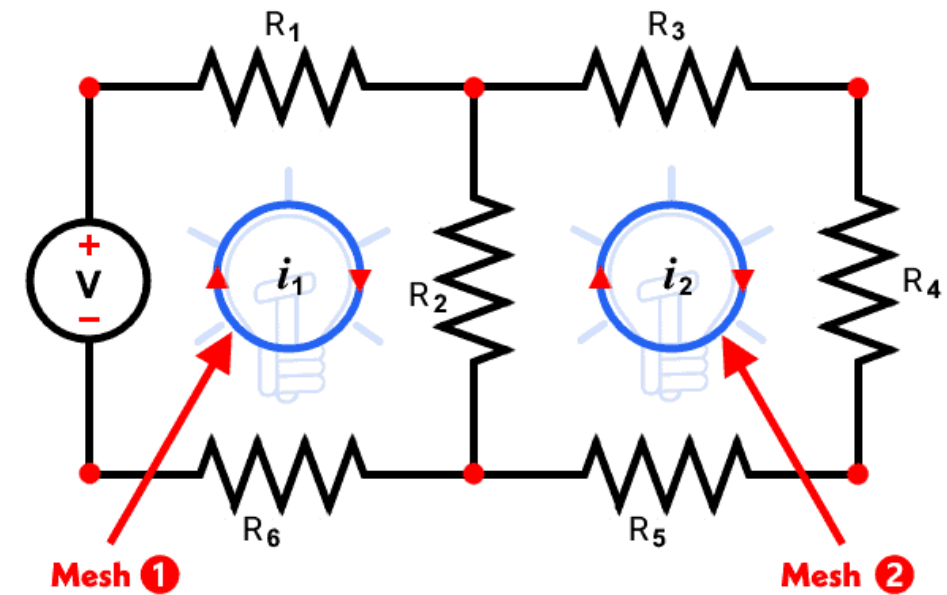


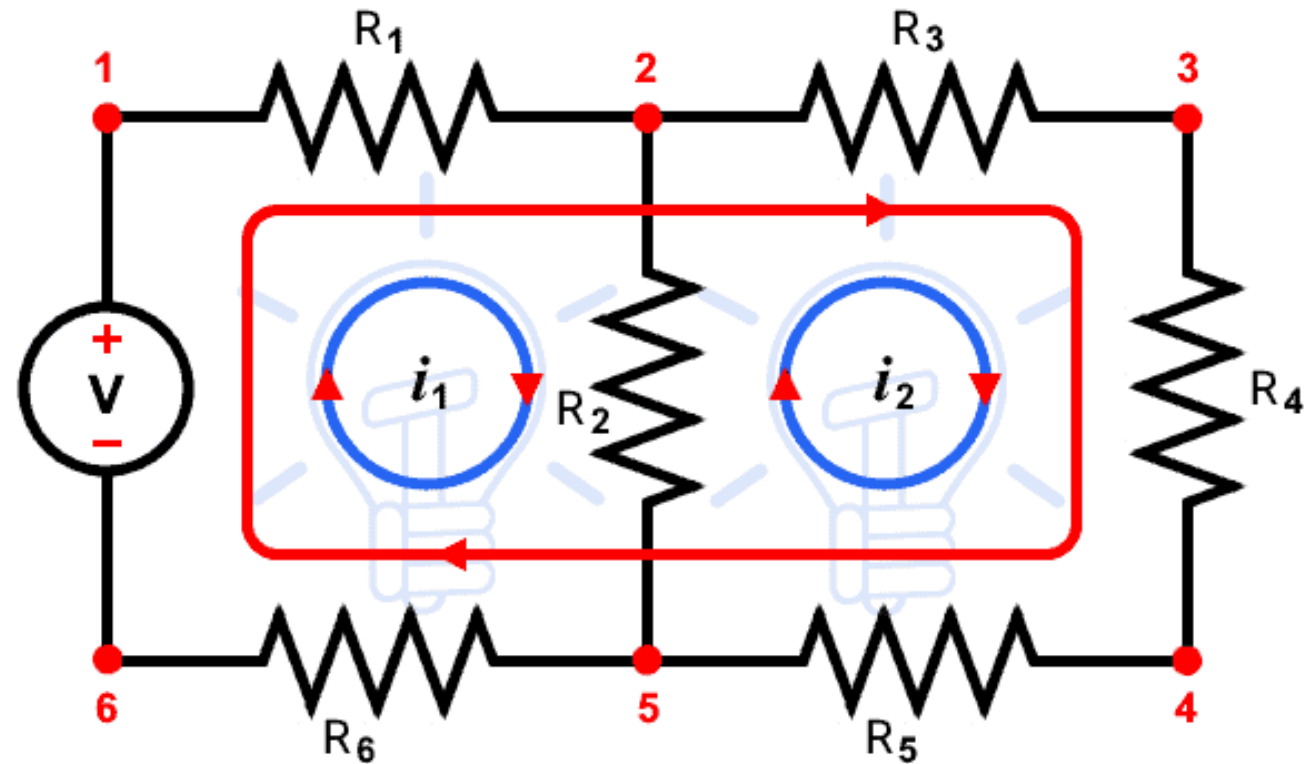How to Determine the Number of Nodes, Loops, Branches and Meshes in a Circuit ?




⑥ Nodes, ⑦ Branches, ③ Loops & ② Meshes

Networks and Circuits

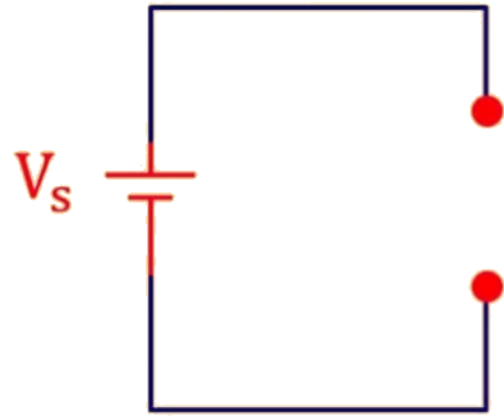

Open Circuit

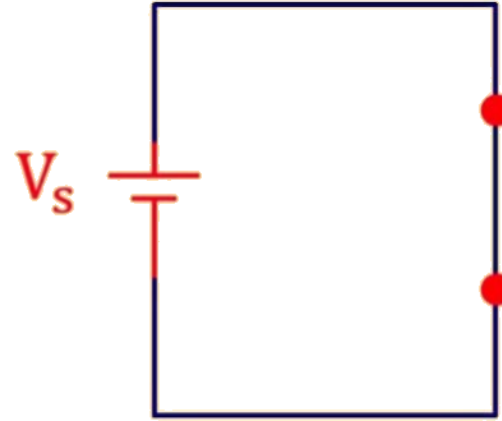

Short Circuit


Open circuit: If the load connected between any two terminals of any network is made infinite, i.e., the conducting path between the terminals is made open then the terminals are said to be open circuited.

Short circuit: If any two terminals of a network are connected by a wire of almost zero resistance then the terminals are said to be short circuited

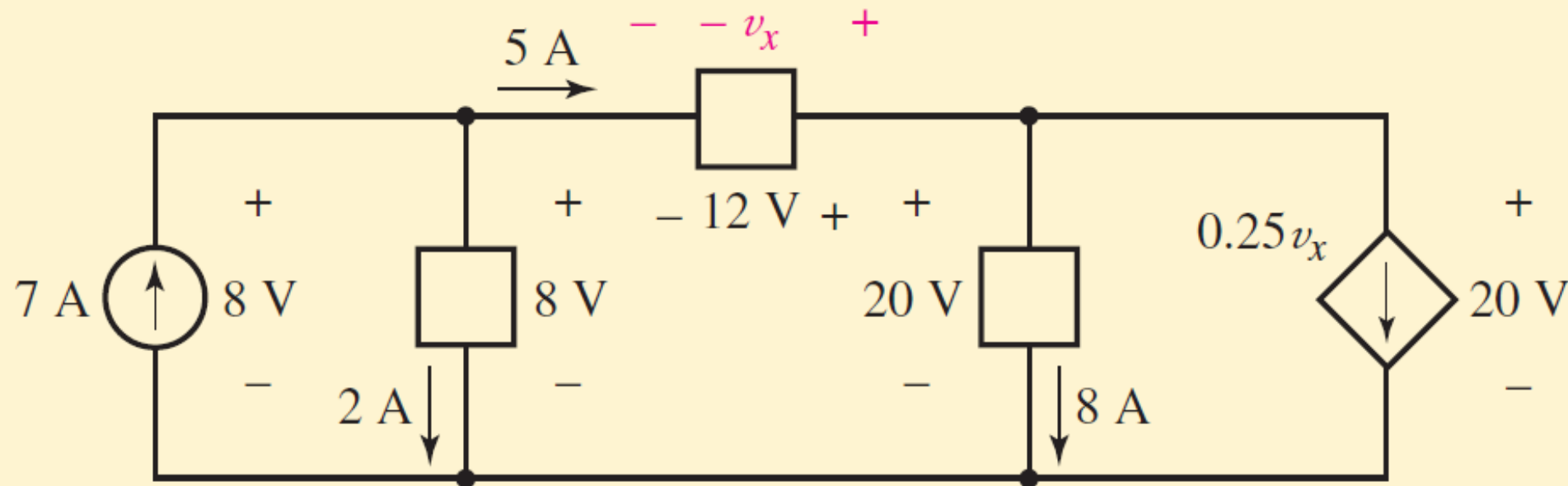Example problem



Find the power *absorbed* by each element in the circuit in Fig



Ans: (left to right) -56 W ; 16 W ; -60 W ; 160 W ; -60 W .

Ohm's law





- Ohm's law states that the current, I flowing in a circuit, is directly proportional to the applied voltage V at constant temperature.

$$I \propto V$$


$$I = \frac{V}{R}$$
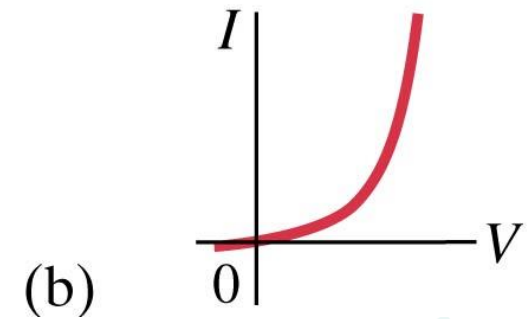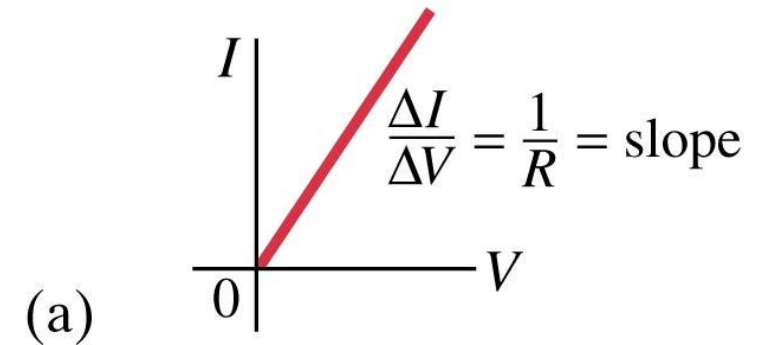
$$\text{or } V = I.R \quad \text{or } R = \frac{V}{I}$$



In many conductors, the resistance is independent of the voltage; this relationship is called Ohm's law. Materials that do not follow Ohm's law are called nonohmic.

Resistivity

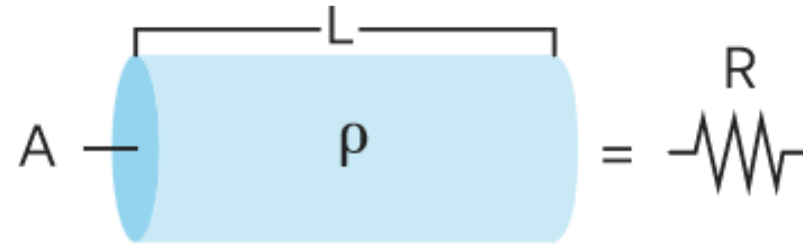


L = length
A = area
 ρ = resistivity

$$R = \rho \frac{L}{A}$$

Resistance

Vs


Resistivity

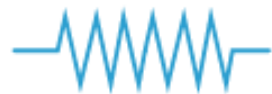

Area

Length

Resistivity

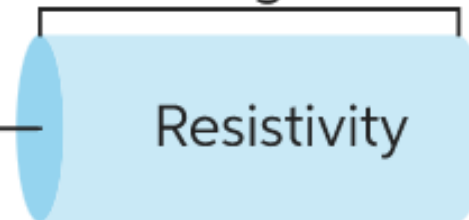

Drude model (a classical approach of classical conductivity)




The basic assumptions of the Drude model

1. between collisions the interaction of a given electron

independent electron approximation
free electron approximation

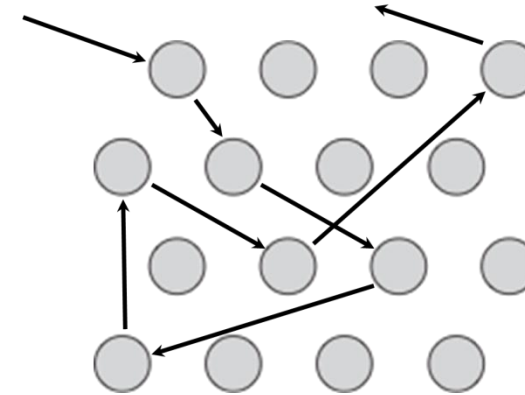2. collisions are instantaneous events

Drude considered electron scattering off
the impenetrable ion cores



the specific mechanism of the electron scattering is not considered below

3. an electron experiences a collision with a probability per unit time $1/\tau$

dt/τ – probability to undergo a collision within small time dt

randomly picked electron travels for a time τ before the next collision

τ is known as the relaxation time, the collision time, or the mean free time

τ is independent of an electron position and velocity

4. after each collision an electron emerges with a velocity that is randomly directed and with a speed appropriate to the local temperature

Drude theory: electrical conductivity



If we apply an electric field, the equation of motion is


$$m_e \frac{d\mathbf{v}}{dt} = -e\mathcal{E}$$

integration gives


$$\mathbf{v}(t) = \frac{-e\mathcal{E}t}{m_e}$$

and if τ is the average time between collisions then the average drift speed is
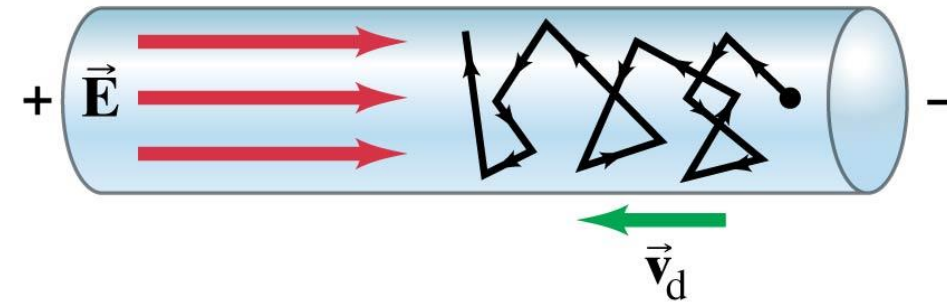
$$\bar{\mathbf{v}} = \frac{-e\mathcal{E}\tau}{m_e}$$



Drude theory: electrical conductivity

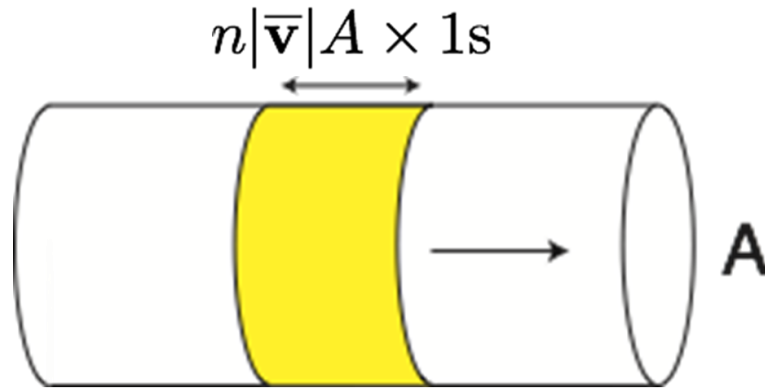

number of electrons passing in unit time

$$n|\bar{\mathbf{v}}|A$$

current of negatively charged electrons

$$-en|\bar{\mathbf{v}}|A$$

current density

$$\mathbf{j} = n\bar{\mathbf{v}}(-e)$$

and with $\bar{\mathbf{v}} = \frac{-e\boldsymbol{\mathcal{E}}\tau}{m_e}$ we get

Ohm's law

$$\mathbf{j} = \frac{ne^2\tau}{m_e}\boldsymbol{\mathcal{E}}$$

Drude theory: electrical conductivity



Ohm's law

$$\mathbf{j} = \frac{ne^2\tau}{m_e}\boldsymbol{\mathcal{E}}$$

$$\mathbf{j} = \sigma\boldsymbol{\mathcal{E}} = \frac{\boldsymbol{\mathcal{E}}}{\rho}$$

and we can define
the conductivity

$$\sigma = \frac{ne^2\tau}{m_e} = n\mu e$$

and the
resistivity

$$\rho = \frac{m_e}{ne^2\tau}$$

and the
mobility

$$\mu = \frac{e\tau}{m_e}$$

$$|\mathbf{v}| = \mu|\boldsymbol{\mathcal{E}}|$$

Resistor




- Resistance: A measure of difficulty to flow electrons through a circuit element
- Can be measured using Ohm's Law

$$V \propto I$$

or

$$V = RI$$

Unit of resistance: Ohm (Ω)

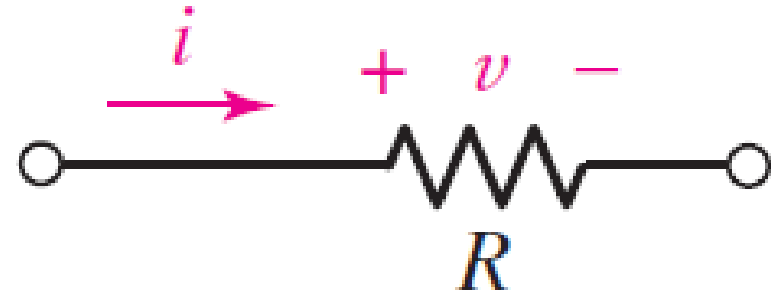

Resistor



- Relation with power:

$$P = VI = I^2 R = \frac{V^2}{R}$$

EXAMPLE 2.3

The $560\ \Omega$ resistor shown in Fig. 2.24*b* is connected to a circuit which causes a current of 42.4 mA to flow through it. Calculate the voltage across the resistor and the power it is dissipating.

Ans: 23.7 V, 1.003/5/7 W

Resistor



- Resistivity: Resistance of per unit length per unit area of an uniform conductor

$$R = \frac{\rho L}{A}$$

- Conductance:

$$G = \frac{1}{R} = \frac{I}{V}$$

Power relation with conductance:

$$P = \frac{I^2}{G} = V^2 G$$



Example




EXAMPLE 2.4

A dc power link is to be made between two islands separated by a distance of 24 miles. The operating voltage is 500 kV and the system capacity is 600 MW. Calculate the maximum dc current flow, and estimate the resistivity of the cable, assuming a diameter of 2.5 cm and a solid (not stranded) wire.

Ans: 1200 A, $R = 417 \text{ Ohm}$, $\text{area} = 4.9 \text{ cm}^2$, $\text{length} = 3.9 \times 10^6 \text{ cm}$, $\rho = 520 \text{ m}\Omega \cdot \text{cm}$

Non-ideal Voltage Source

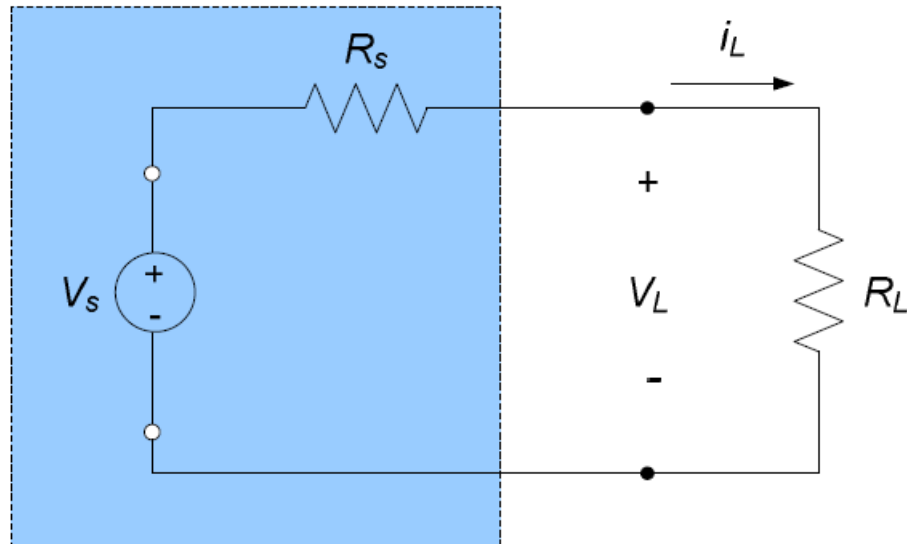


- Modelled as an ideal voltage source and internal resistance
- Implication:
 - When a load draws large current, supply voltage decreases and the converse
- Does not provide infinite power
- Note: Ideal voltage source means a source with zero internal resistance

Non-ideal current source



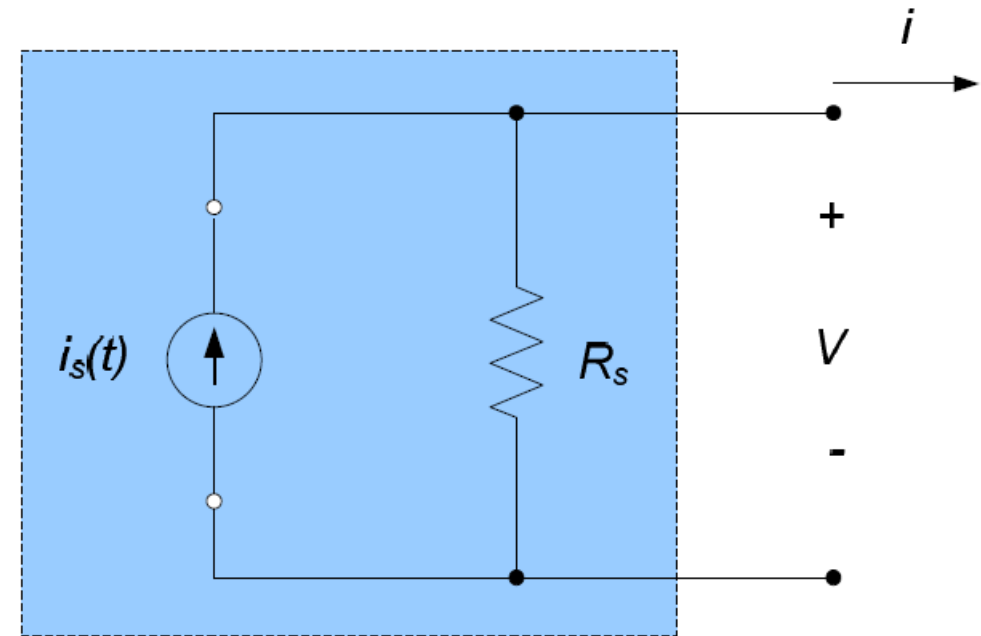- Modelled as an ideal current source and internal resistance in parallel
- Implication:
 - Higher terminal voltage results in lower supply current
- Note: Ideal current source means a source with infinite internal resistance






Nodes and loops



- **Node**: A point at which two or more circuit elements have a common connection
- **Loop**: If a set of nodes and elements are traversed in such a way that *no node is encountered more than once, then the set of nodes and elements are called a path*. If the start and end point of a path is the same node, then it is called a loop.




Node

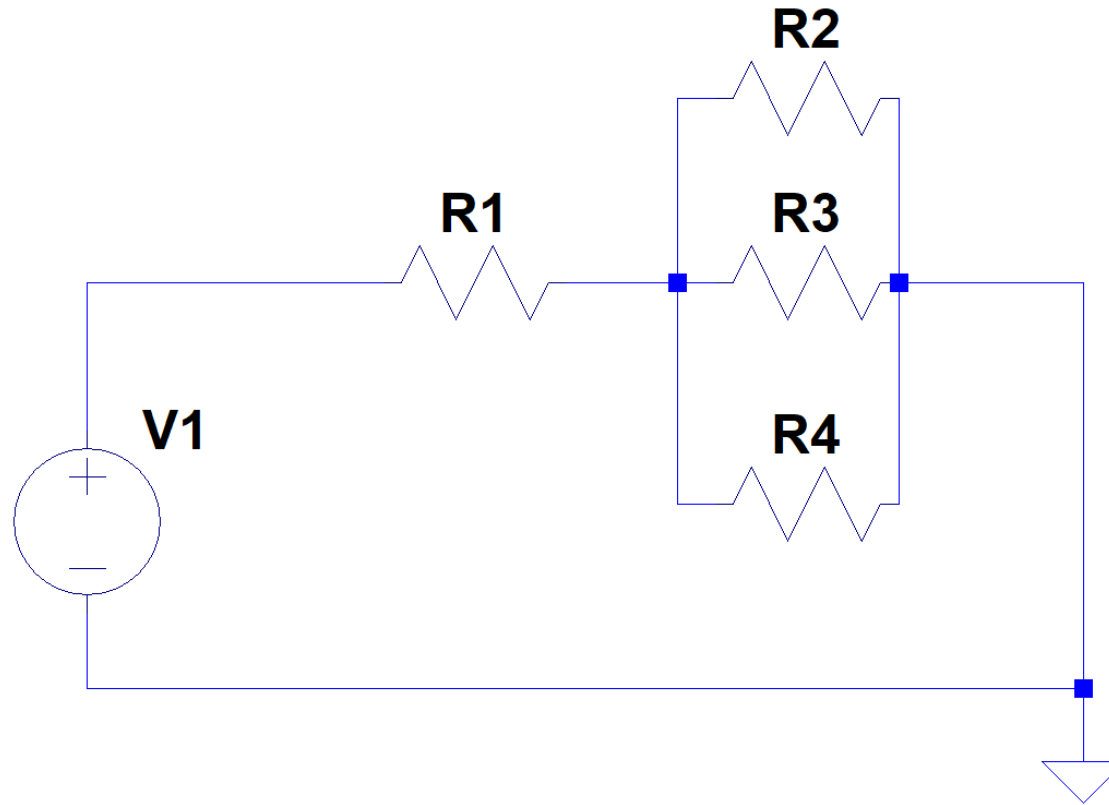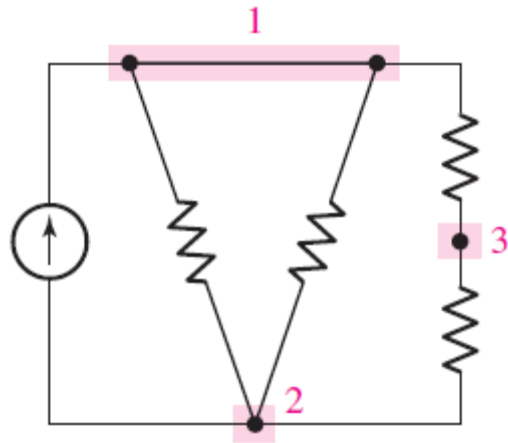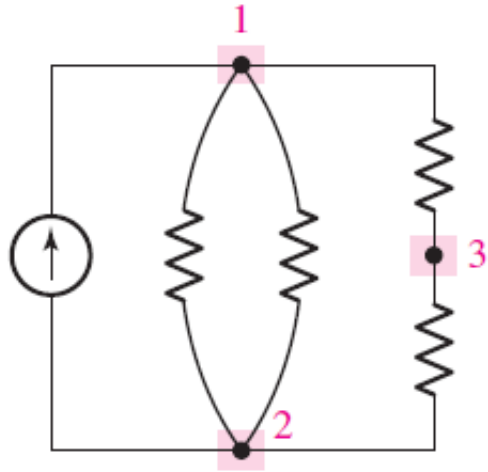

How many nodes are there in the above circuit?

Loop

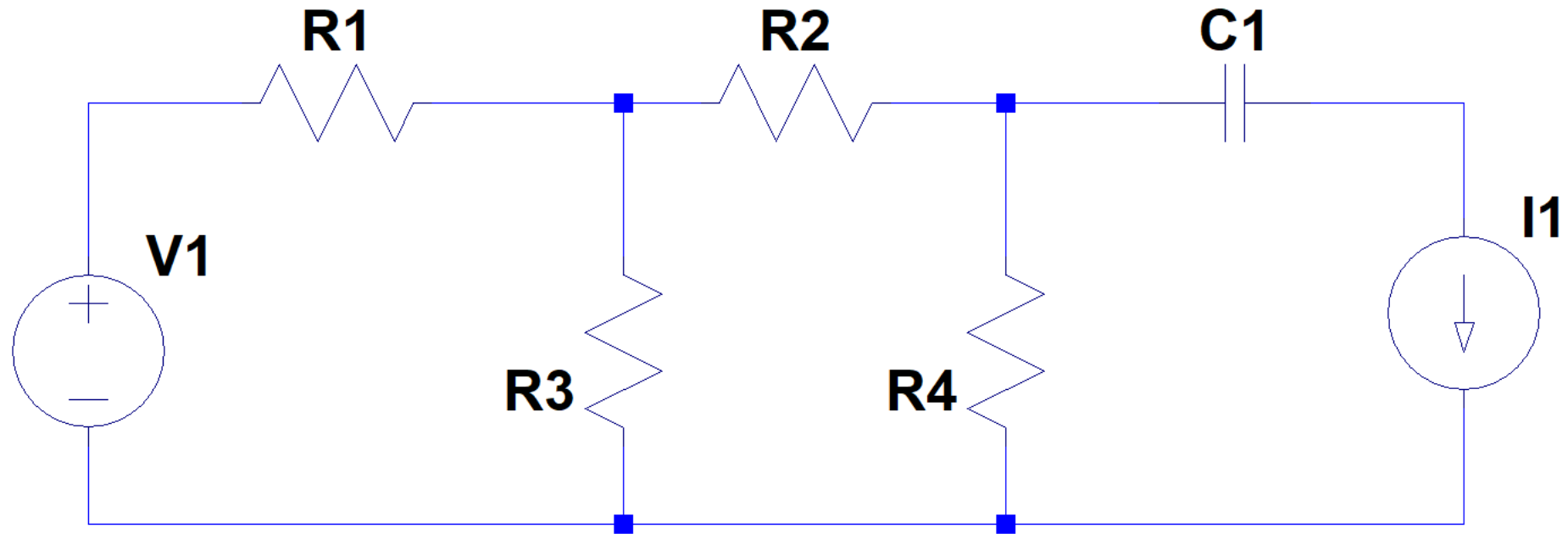

Kirchhoff's Laws



- Proposed by Gustav Kirchhoff [keerkh-hawf]
- Kirchhoff's Current Law (KCL): tells us the relationship of currents at a node
- Kirchhoff's Voltage Law (KVL): Tells us the relationship of voltages in a loop




Kirchhoff's Current Law




- The algebraic sum of the currents entering any node is zero
- Implication: current entering a node is equal to the current exiting the node
- Conservation of charge implies KCL

$$\sum_{n=1}^N i_n = 0$$

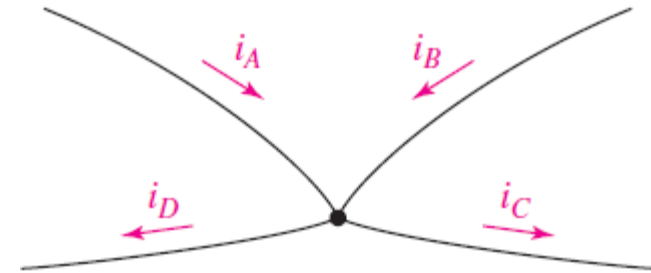

- **Current entering +ve, exiting -ve**

Example 1

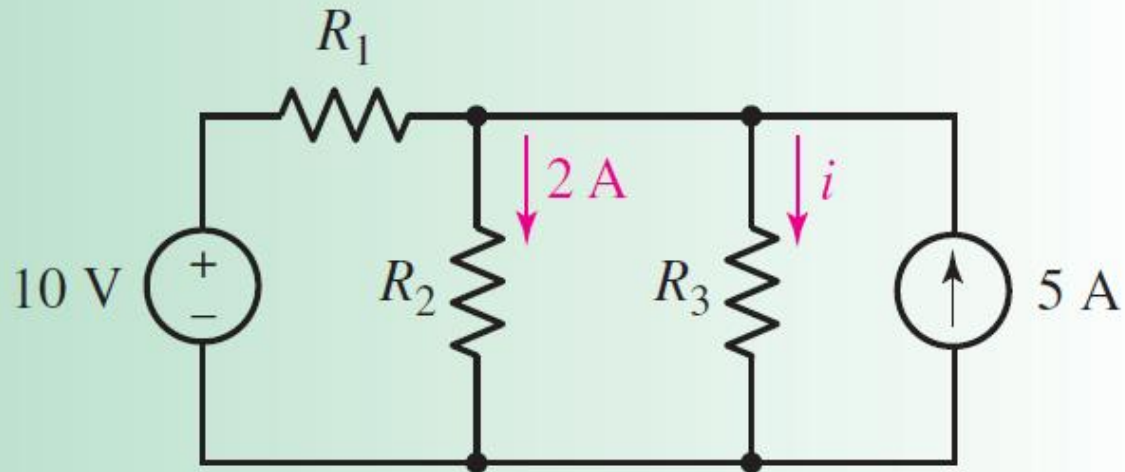

For the circuit in the Fig, compute the current through resistor R_3 if it is known that the voltage source supplies a current of 3 A.

Ans: 6 A

► **Identify the goal of the problem.**

The current through resistor R_3 , labeled as i on the circuit diagram.

► **Collect the known information.**

The node at the top of R_3 is connected to four branches.

Two of these currents are clearly labeled: 2 A flows out of the node into R_2 , and 5 A flows into the node from the current source. We are told the current out of the 10 V source is 3 A.

► **Devise a plan.**

If we label the current through R_1 (Fig. 3.3b), we may write a KCL equation at the top node of resistors R_2 and R_3 .

► **Construct an appropriate set of equations.**

Summing the currents flowing into the node:

$$i_{R_1} - 2 - i + 5 = 0$$




The currents flowing into this node are shown in the expanded diagram of Fig. 3.3c for clarity.

► **Determine if additional information is required.**

We have one equation but two unknowns, which means we need to obtain an additional equation. At this point, the fact that we know the 10 V source is supplying 3 A comes in handy: KCL shows us that this is also the current i_{R_1} .

► **Attempt a solution.**

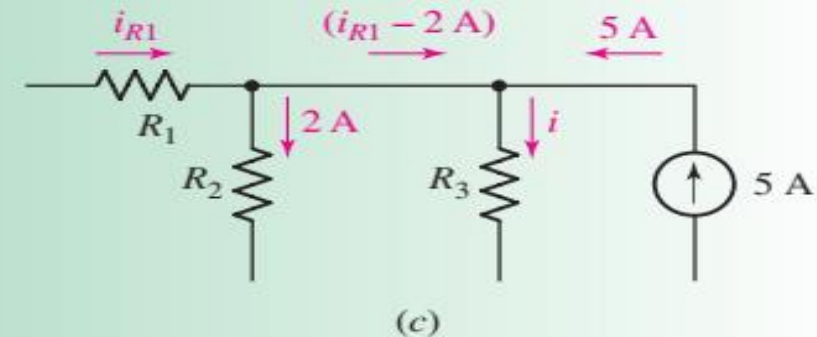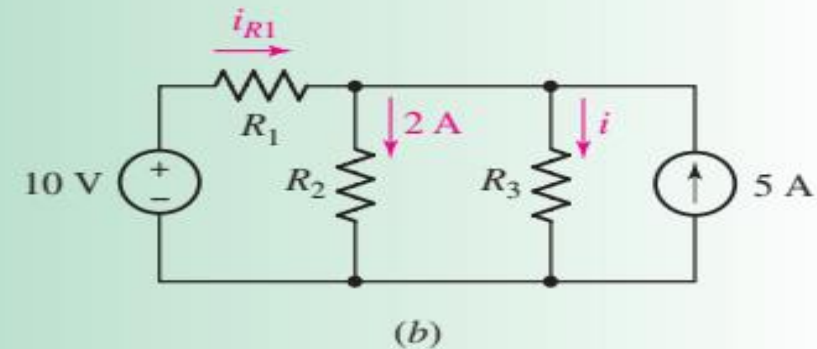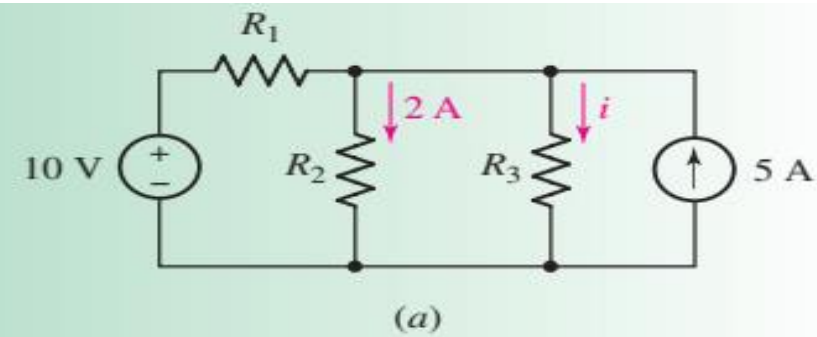Substituting, we find that $i = 3 - 2 + 5 = 6$ A.




■ **FIGURE 3.3** (a) Simple circuit for which the current through resistor R_3 is desired. (b) The current through resistor R_1 is labeled so that a KCL equation can be written. (c) The currents into the top node of R_3 are redrawn for clarity.

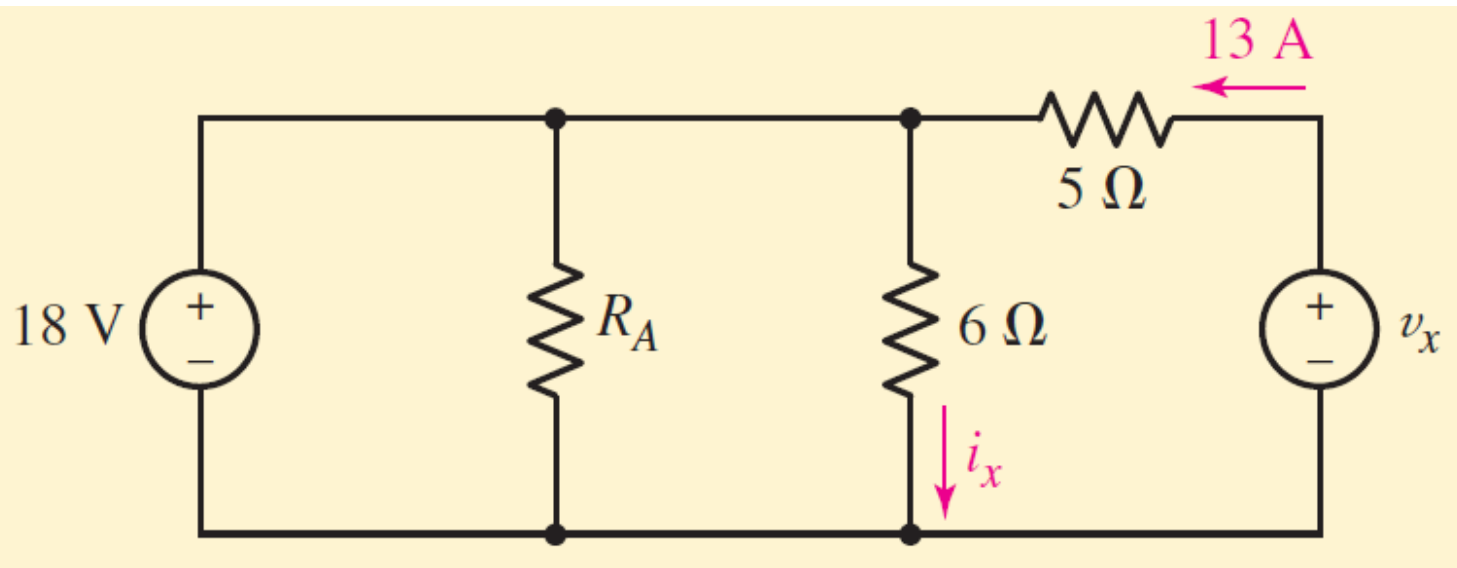Example 2




If $i_x = 3$ A and the 18 V source delivers 8 A of current, what is the value of R_A ?



Ans: 1 ohm

Example 2 solution

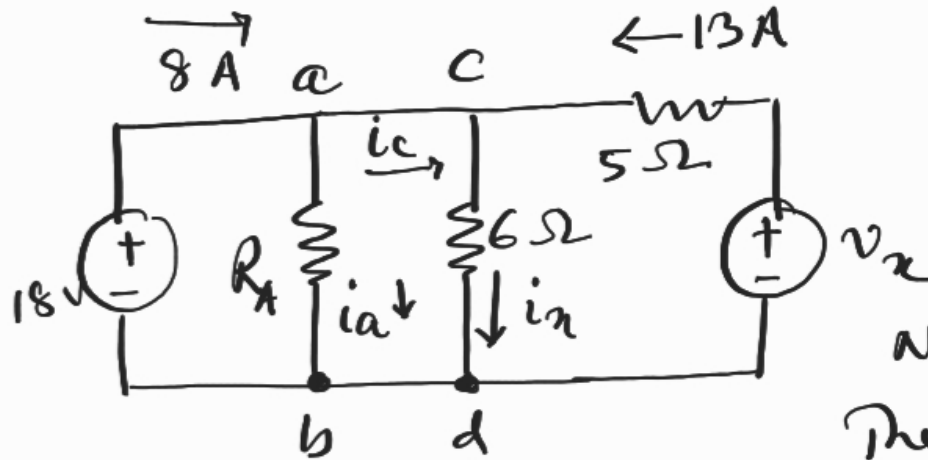

given $i_x = 3A$

voltage at $ab = 18V$

Now if we use KCL at a

Then we can write

$$8 = i_a + i_c$$

$$\therefore i_c = 8 - i_a$$

Now current at c ;

$$i_c + 13 = i_x$$

$$\Rightarrow 8 - i_a + 13 = 3 \Rightarrow i_a = 18$$

Using Ohm's law, $V_{ab} = R_A \cdot i_a \therefore R_A = \frac{18V}{18A} = 1\Omega$

Kirchhoff's Voltage Law




- The algebraic sum of the voltages around any closed path is zero

$$\sum_{n=1}^N v_n = 0$$

- Convention: sign should be –ve if a –ve side of an element is encountered



Kirchhoff's Voltage Law

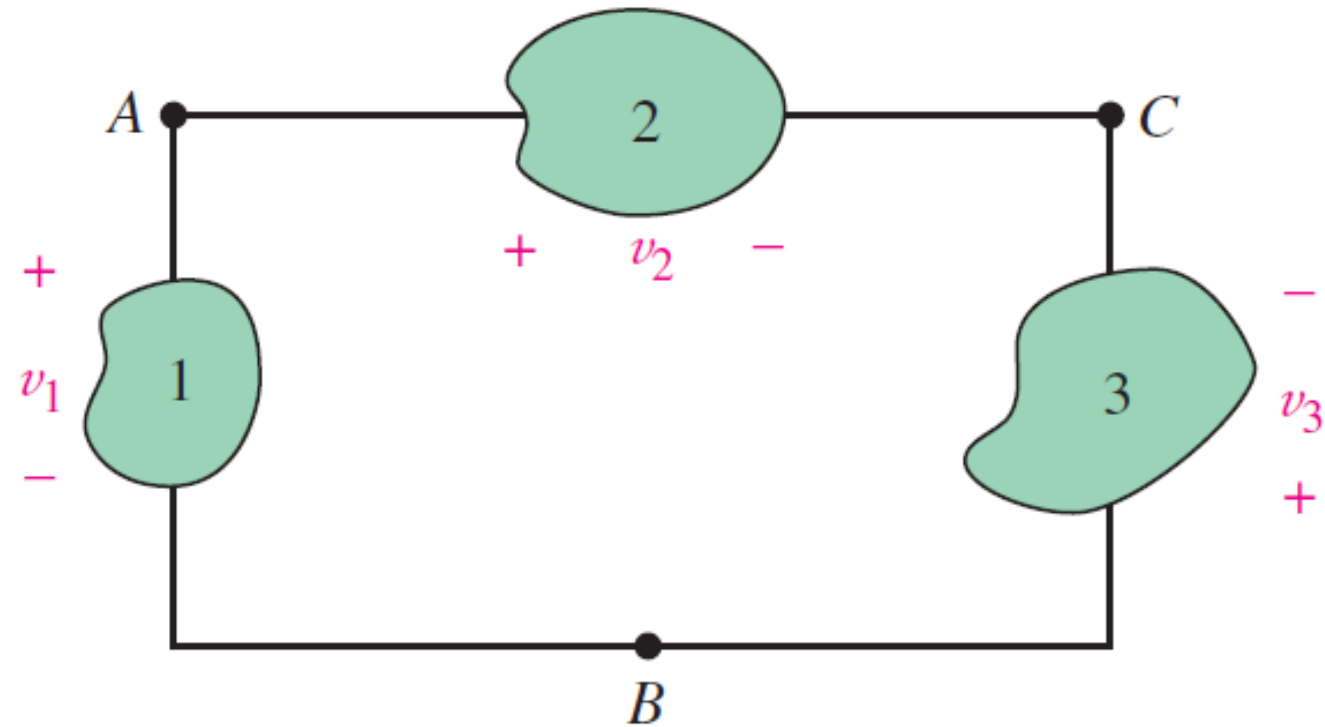


Example 3



In the circuit, find v_x and i_x .

Ans: 12V ,120 mA

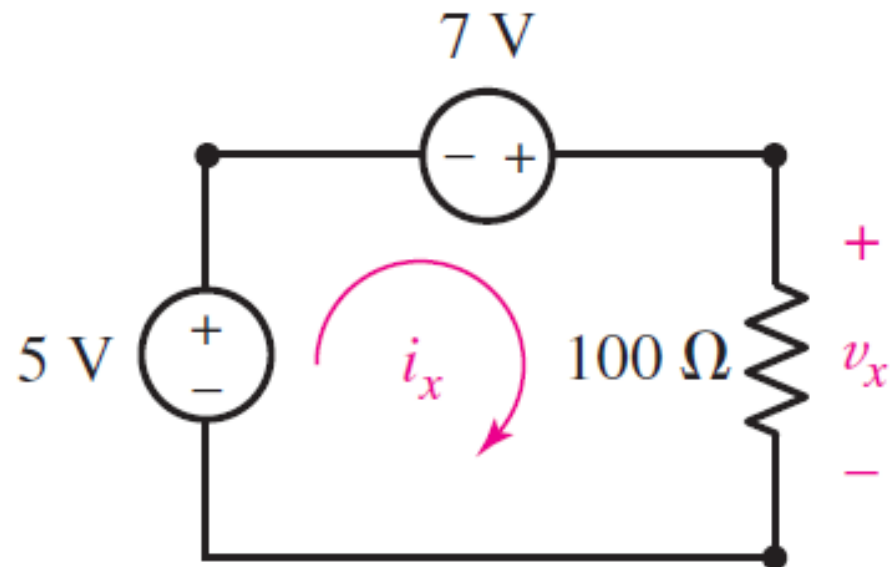

Example 3 solution



We know the voltage across two of the three elements in the circuit. Thus, KVL can be applied immediately to obtain v_x .

Beginning with the bottom node of the 5 V source, we apply KVL clockwise around the loop:


$$-5 - 7 + v_x = 0$$

so $v_x = 12$ V.


KCL applies to this circuit, but only tells us that the same current (i_x) flows through all three elements. We now know the voltage across the $100\ \Omega$ resistor, however.

Invoking Ohm's law,

$$i_x = \frac{v_x}{100} = \frac{12}{100} \text{ A} = 120 \text{ mA}$$

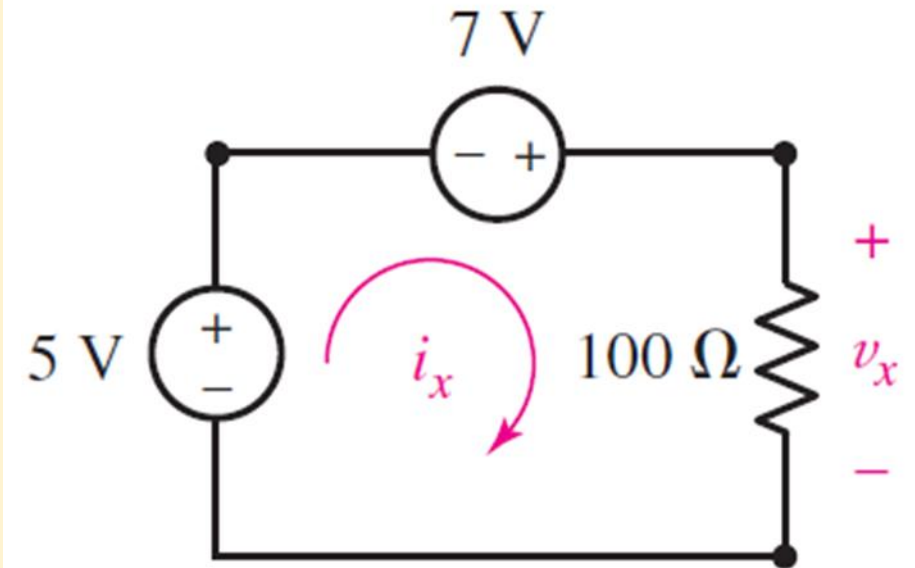

Example 4

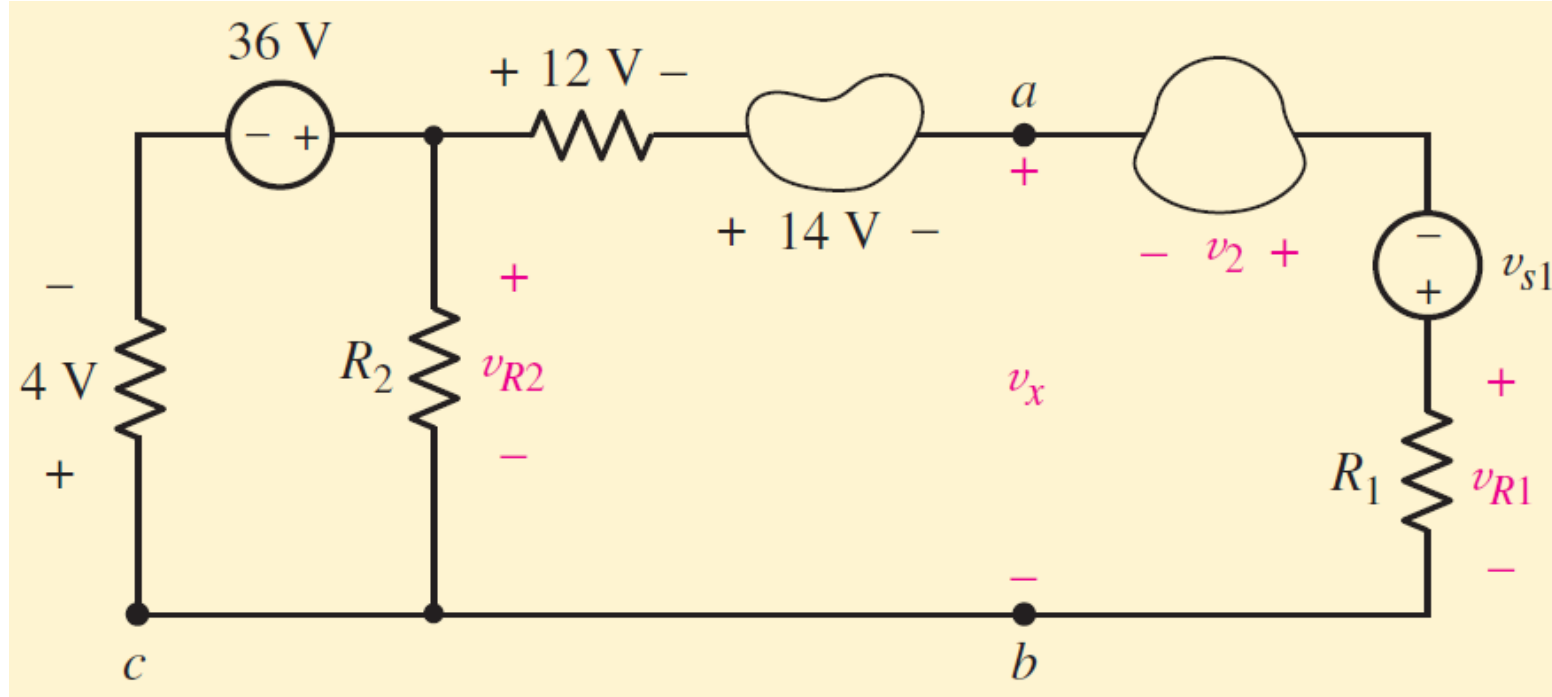

Find v_{R2} (the voltage across R_2) and the voltage labeled v_x .

Ans: 32 V, 6 V

Example 4 solution



The best approach for finding v_{R2} is to look for a loop to which we can apply KVL. There are several options, but the leftmost loop offers a straightforward route, as two of the voltages are clearly specified. Thus, we find v_{R2} by writing a KVL equation around the loop on the left, starting at point c :

$$4 - 36 + v_{R2} = 0$$

which leads to $v_{R2} = 32$ V.

To find v_x , we might think of this as the (algebraic) sum of the voltages across the three elements on the right. However, since we do not have values for these quantities, such an approach would not lead to a numerical answer. Instead, we apply KVL beginning at point c , moving up and across the top to a , through v_x to b , and through the conducting lead to the starting point:

$$+4 - 36 + 12 + 14 + v_x = 0$$


so that

$$v_x = 6 \text{ V}$$


An alternative approach: Knowing v_{R2} , we might have taken the shortcut through R_2 :

$$-32 + 12 + 14 + v_x = 0$$

yielding $v_x = 6$ V once again.

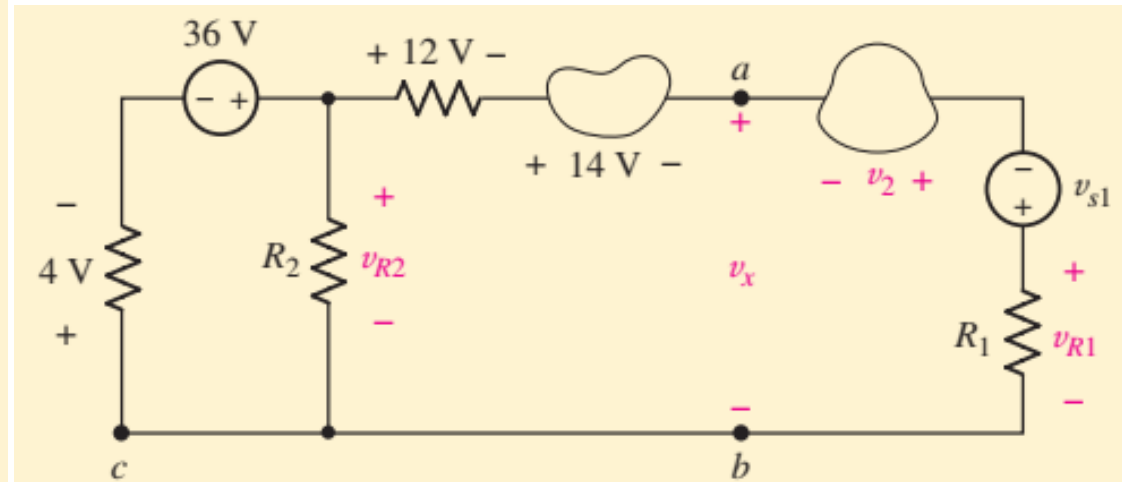



Example 5

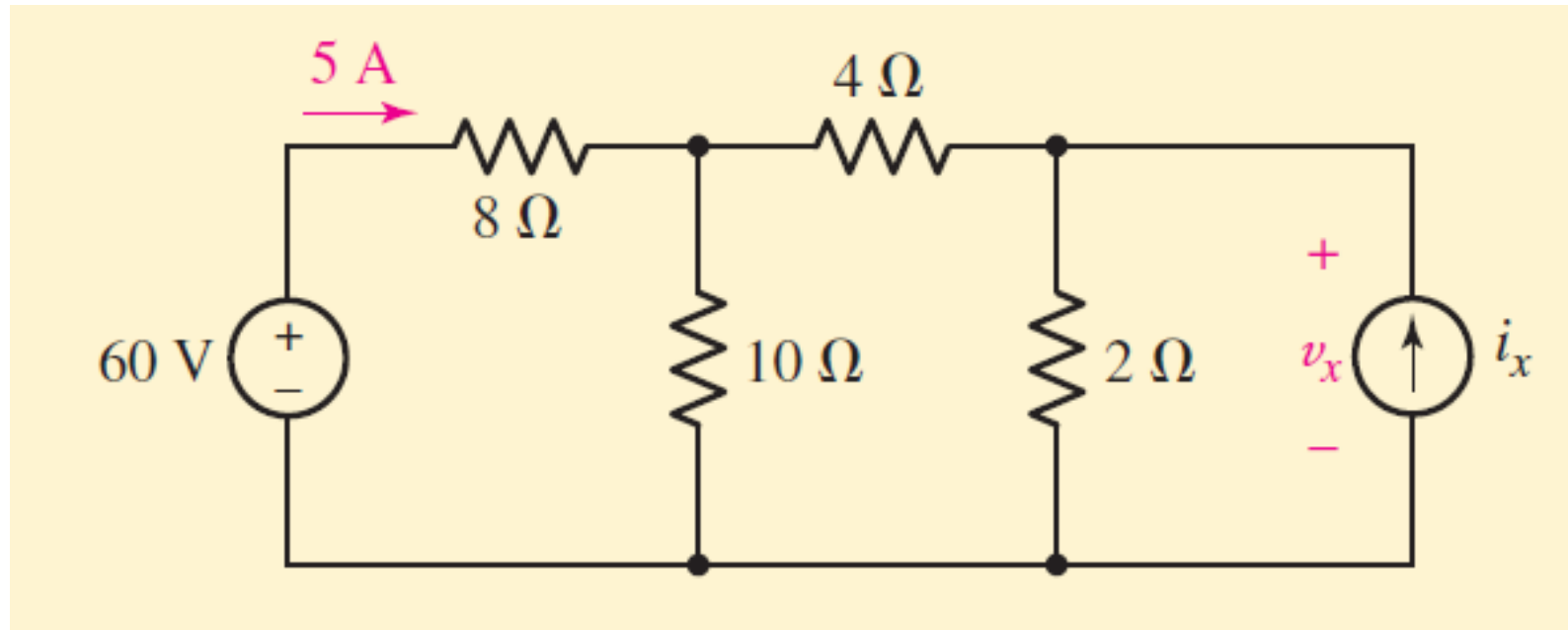

Determine v_x

Ans: 8V

Example 5 solution

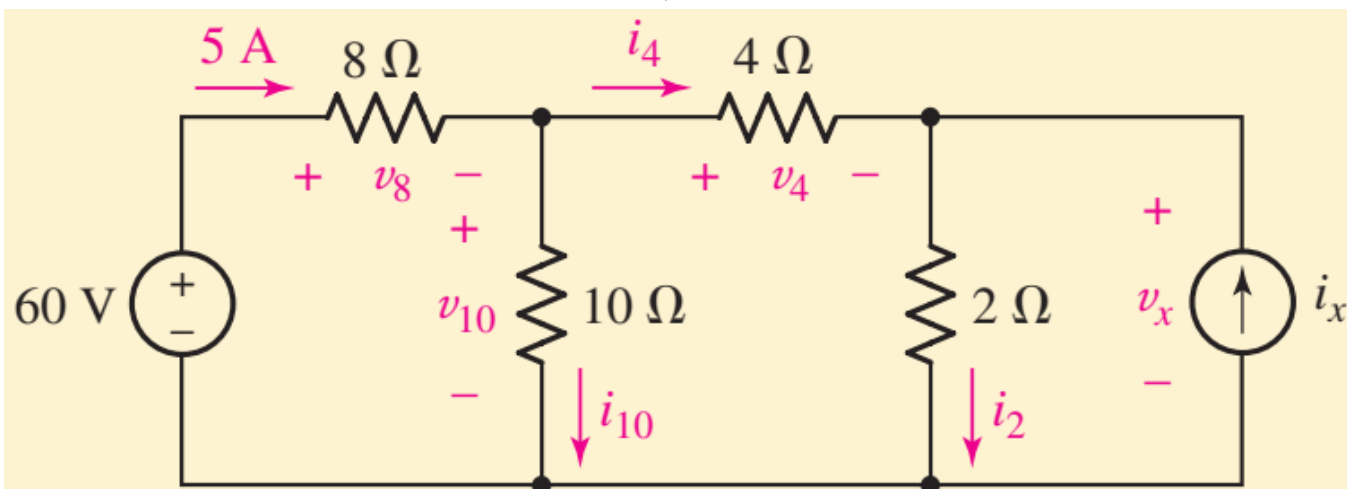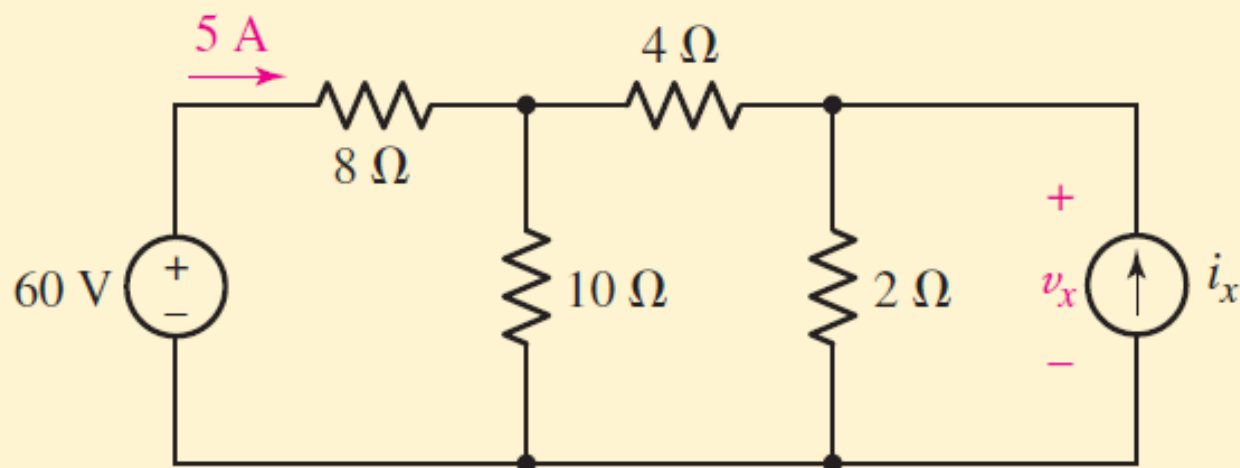

We begin by labeling voltages and currents on the rest of the elements in the circuit (Fig. 3.10b). Note that v_x appears across the $2\ \Omega$ resistor and the source i_x as well.

If we can obtain the current through the $2\ \Omega$ resistor, Ohm's law will yield v_x . Writing the appropriate KCL equation, we see that

$$i_2 = i_4 + i_x$$

Unfortunately, we do not have values for any of these three quantities. Our solution has (temporarily) stalled.

Since we were given the current flowing from the 60 V source, perhaps we should consider starting from that side of the circuit. Instead of finding v_x using i_2 , it might be possible to find v_x directly using KVL. We can write the following KVL equations:

$$-60 + v_8 + v_{10} = 0$$

and

$$-v_{10} + v_4 + v_x = 0 \quad [5]$$

This is progress: we now have two equations in four unknowns, an improvement over one equation in which *all* terms were unknown. In fact, we know that $v_8 = 40\text{ V}$ through Ohm's law, as we were told that 5 A flows through the $8\ \Omega$ resistor. Thus, $v_{10} = 0 + 60 - 40 = 20\text{ V}$, so Eq. [5] reduces to

$$v_x = 20 - v_4$$

If we can determine v_4 , the problem is solved.

The best route to finding a numerical value for the voltage v_4 in this case is to employ Ohm's law, which requires a value for i_4 . From KCL, we see that

$$i_4 = 5 - i_{10} = 5 - \frac{v_{10}}{10} = 5 - \frac{20}{10} = 3$$

so that $v_4 = (4)(3) = 12\text{ V}$ and hence $v_x = 20 - 12 = 8\text{ V}$.

Reference



- Hayt and Kemmerly, Chapter 3




Series and parallel circuits



Series circuit

$$v_1 = (R_1 + R_2 + R_3)i$$

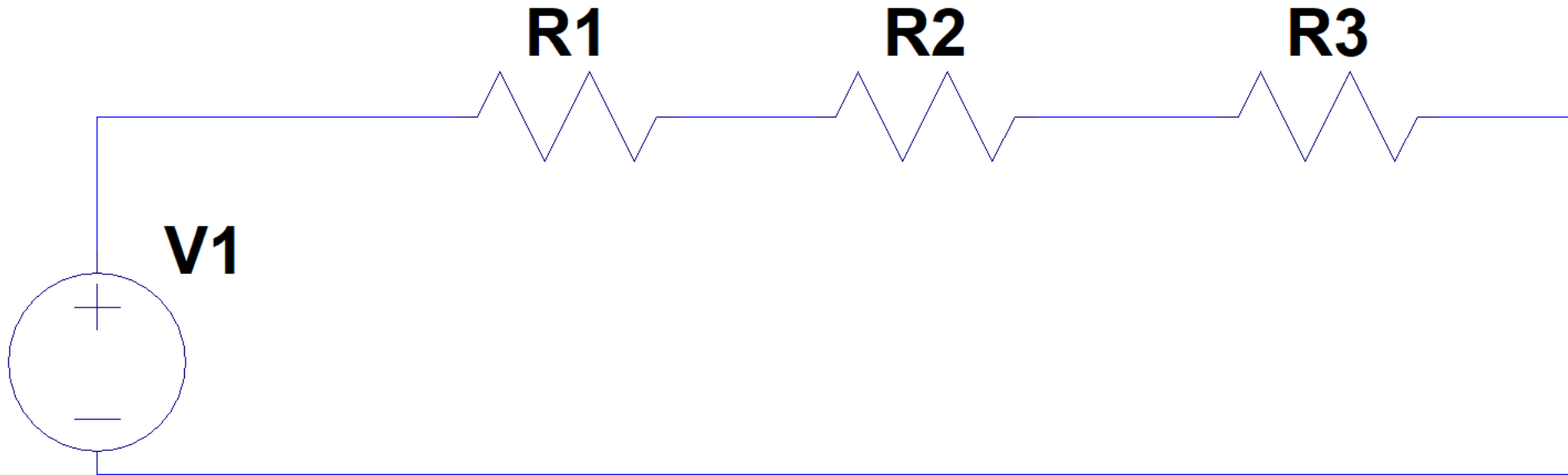


Series and parallel circuits



Parallel circuit

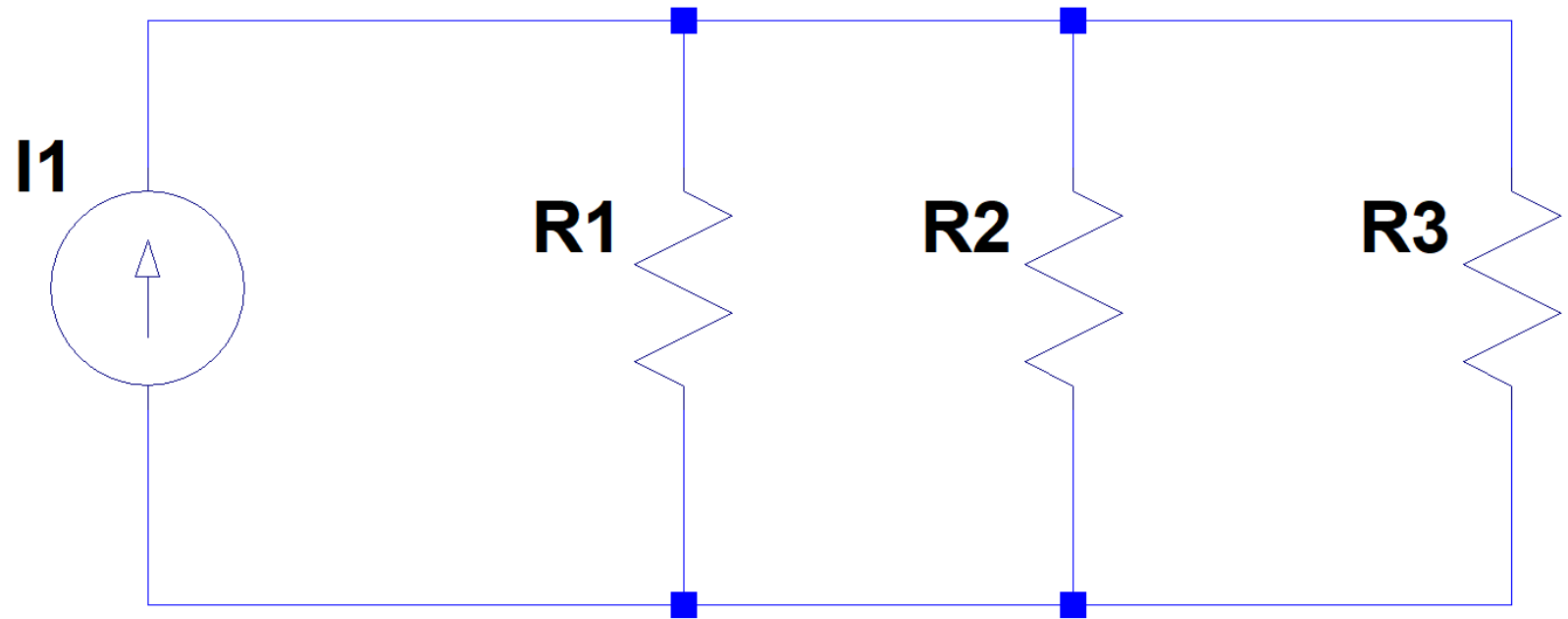
$$i_1 = \frac{v}{R_1} + \frac{v}{R_2} + \frac{v}{R_3}$$



Single loop circuit




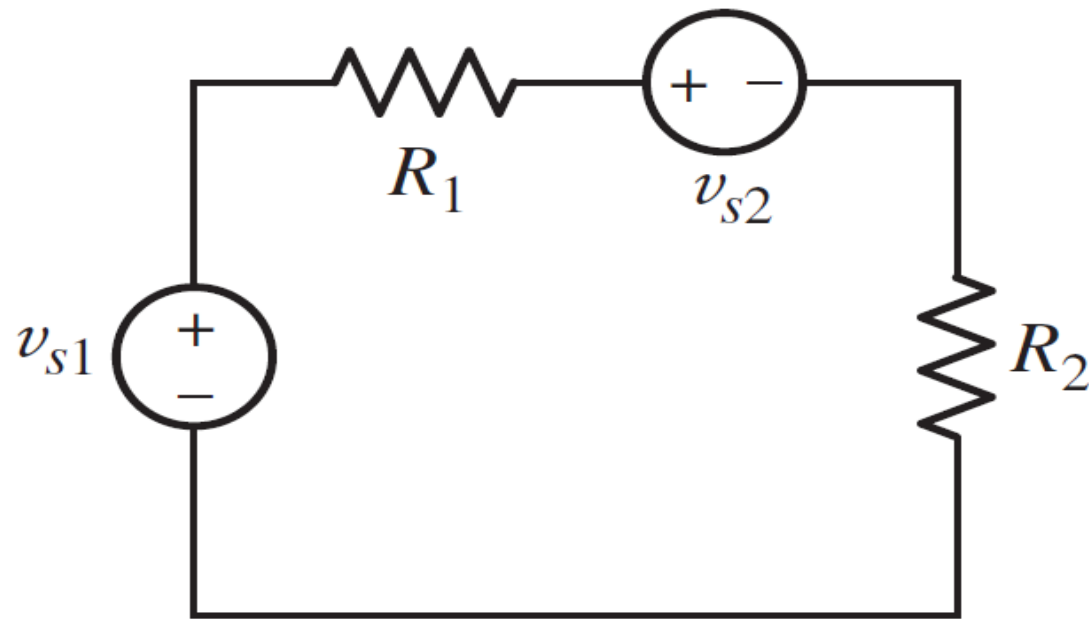We seek the current *through* each element, the voltage *across* each element, and the power *absorbed* by each element



Current through the circuit
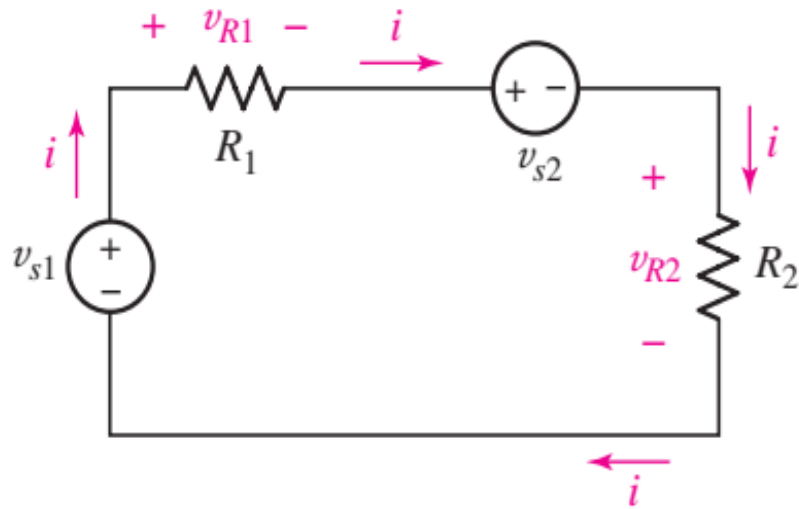
$$i = \frac{v_{s1} - v_{s2}}{R_1 + R_2}$$



$$-v_{s1} + v_{R1} + v_{s2} + v_{R2} = 0$$

We then apply Ohm's law to the resistive elements:

$$v_{R1} = R_1 i \quad \text{and} \quad v_{R2} = R_2 i$$

Substituting into Eq. [6] yields

$$-v_{s1} + R_1 i + v_{s2} + R_2 i = 0$$

Since i is the only unknown, we find that

$$i = \frac{v_{s1} - v_{s2}}{R_1 + R_2}$$

The voltage or power associated with any element may now be obtained by applying $v = Ri$, $p = vi$, or $p = i^2 R$.