 





# Basic Functions Using Multiplexers:

$$f(w_2, w_1, w_0) = \overline{w_2} \cdot w_0 + w_1 \cdot \overline{w_0}$$


$w_2 \backslash w_1 w_0$	00	01	11	10
0	0	1	1	1
1	0	0	0	1



$w_2 \backslash w_1$	0	1
0	$w_0$	1
1	0	$\overline{w_0}$

 


$w_2 \backslash w_1 w_0$	00	01	11	10
0	$w_0 + w_1$			
1	$w_1 \cdot \overline{w_0}$			

 

Alternative:


$w_1 w_0 \backslash w_2$	0	1
00	0	$\overline{w_2}$
01	$\overline{w_2}$	$\overline{w_2}$
11	0	1
10	0	1

 

$w_0 \backslash w_1$	0	1
0	$w_1$	$\overline{w_2}$
1	$\overline{w_2}$	$\overline{w_2}$

 
## Boolean Functions Using Multiplexers:

- $f(w, x, y, z) = \sum m(1, 4, 5, 7, 9, 10, 12, 13)$  using 4:1 MUX and 2:1 MUX only


 
# Boolean Circuits Using Multiplexers (HW)


- $f(w, x, y, z) = \sum m(1, 4, 5, 7, 9, 12, 13)$  using 8:1 MUX and logic gates only
- Design 1-bit full adder using 4:1 multiplexers
- Design a 2-input XNOR gate using 4:1 multiplexer
- Design a 2-input XNOR gate using 2:1 multiplexers




# 3:8 Decoder with Enable Using 2:4 Decoder: ← 2 of these

Control  $\bar{w}_2 = E_n \bar{w}_2$   $y_2 = E_n w_2$  for a comb<sup>n</sup> of  $w$ 's corresponding  $y \rightarrow 1$  sub. is dec. equivalent of  $w_1 w_0$

$E_n$	$w_2$	$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$
1	0	0	0	1	0	0	0	0	0	0	0
1	0	0	1	0	1	0	0	0	0	0	0
1	0	1	0	0	0	1	0	0	0	0	0
1	0	1	1	0	0	0	1	0	0	0	0
1	1	0	0	0	0	0	0	1	0	0	0
1	1	0	1	0	0	0	0	0	1	0	0
1	1	1	0	0	0	0	0	0	0	1	0
1	1	1	1	0	0	0	0	0	0	0	1
0	$\phi$	$\phi$	$\phi$	0	0	0	0	0	0	0	0

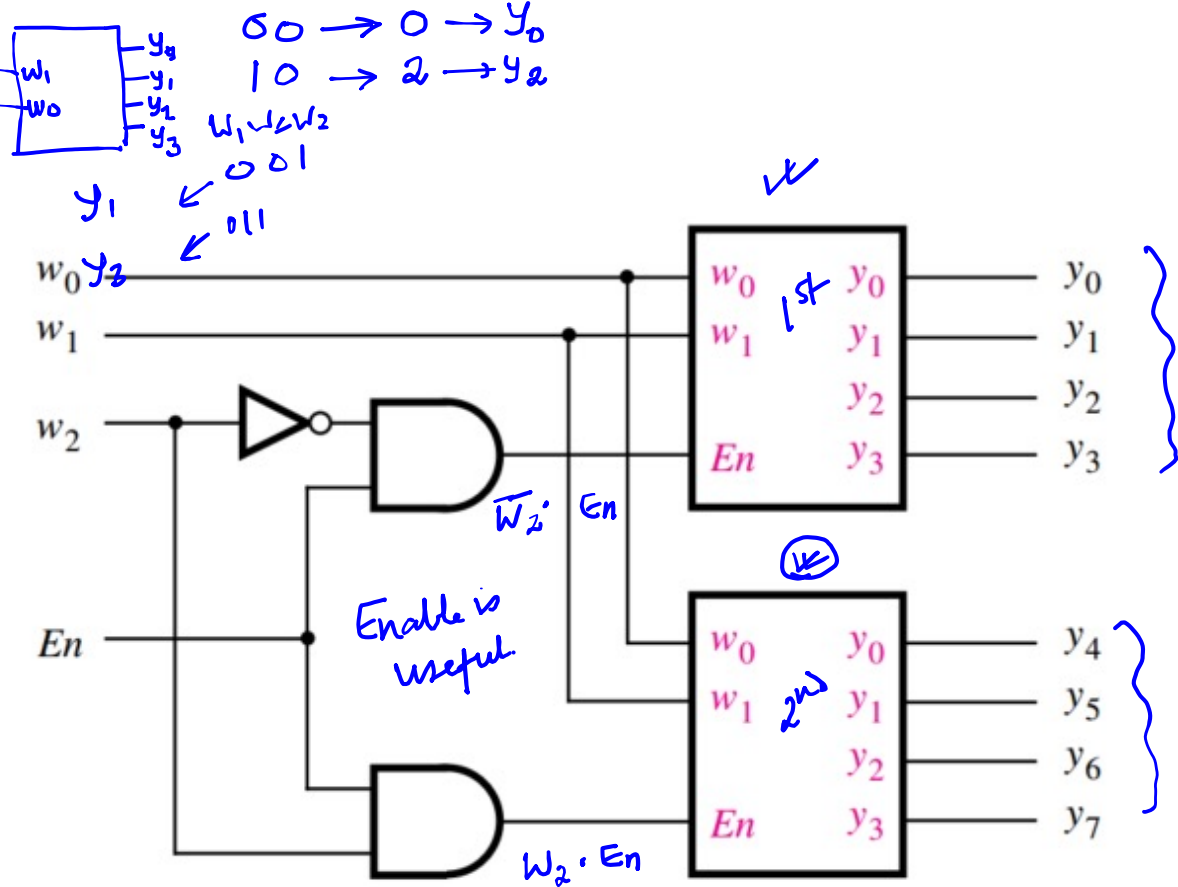
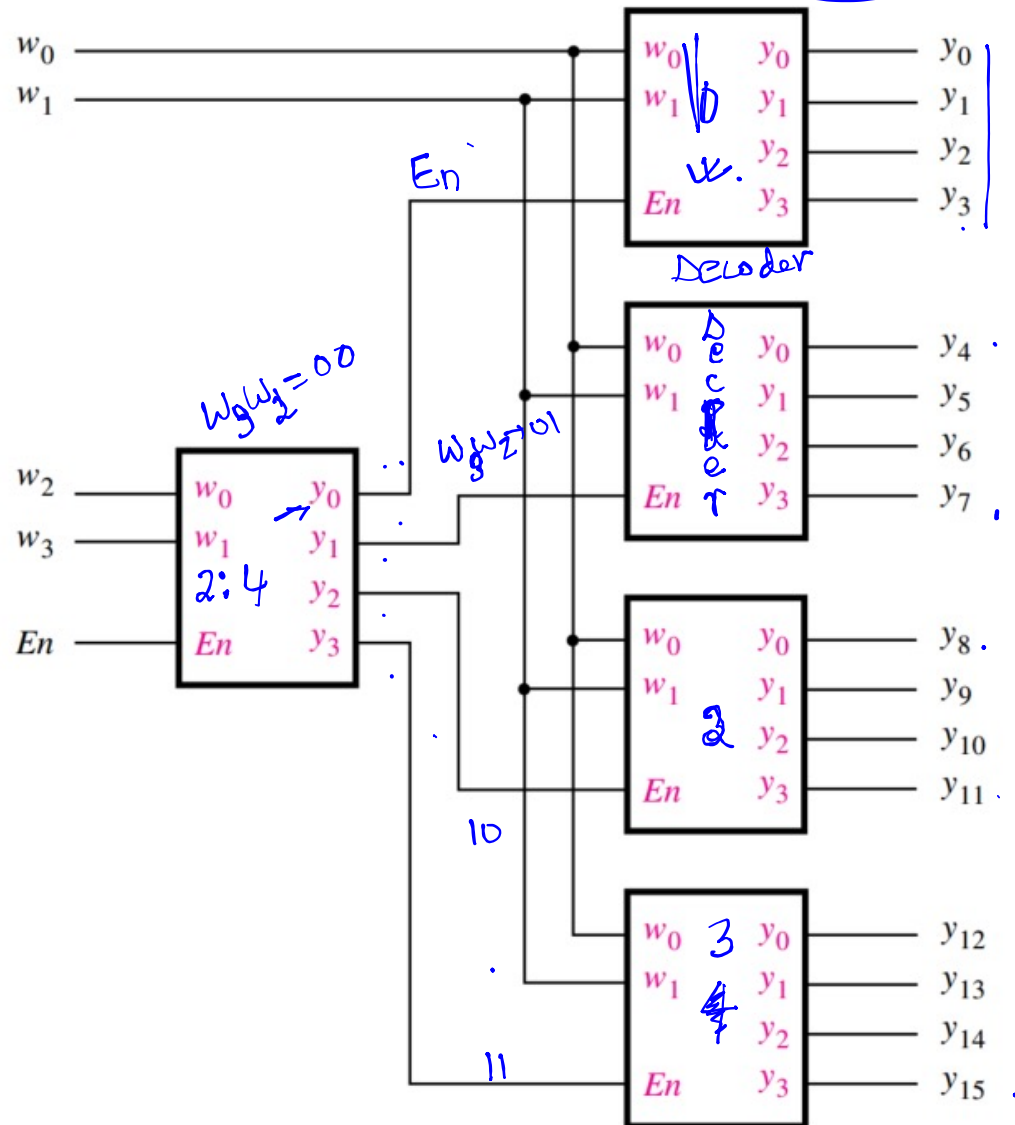
## 4:16 Decoder using 2:4 Decoders with Enable:



each output  
is a min term  
active high

Homework: 4:16 Decoder using  
3:8 Decoder with Enable.

common  
 $w_3, w_2, w_1, w_0$

using Decoder to  
realize a 1?

obvious  
active low

only one of the  
output zero  
max terms.



## Points to note while Realizing Logic Functions with Decoders:


- A function,  $f$ , with a long list of minterms requires an OR gate with large number of inputs. A  $n$ -variable function with  $k$  minterms can be expressed in its complemented form with  $(2^n - k)$  minterms.   
 $f \rightarrow$  short list of minterms.   
 $2^n - 11$  input OR 

1	1	1	1
1	1	1	1
1	1	1	1
1	1	1	1

 $2^n$  minterms close to  $2^n$
- If the number of minterms in a function with  $n$ -variables is greater than  $2^{n-1}$  terms, then  $\bar{f}$  can be expressed with fewer minterms. In such a case it is more advantageous to use NOR gate to sum the minterms of  $\bar{f}$ . The output of the NOR gate will be  $f$ .   
 $2^{n-1}$
- If the Decoder was made with NAND gates with Active Low Enable and Active Low Output, the external gates used must be NAND gates to get the SOP form instead of the OR gate. A two-level NAND gate circuit implements the SOP function and is equivalent to a two-level AND-OR circuit.   
Active High

 
## Logic Realization with Decoders:

$$f(A, B, C) = \sum m(0, 1, 3, 4, 6, 7)$$



Choosing minterms for  $f$
 
$$\bar{f}(A, B, C) = \sum m(\underline{2}, \underline{5})$$




Choosing minterms for  $\bar{f}$



## Logic Realization with Decoders:


- $f(A, B) = \sum m(2,3)$  || 2 different ways.

 The Decoder is always Enabled when output is to be used.



$En$	$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	$\phi$	$\phi$	0	0	0	0


Active High Output.

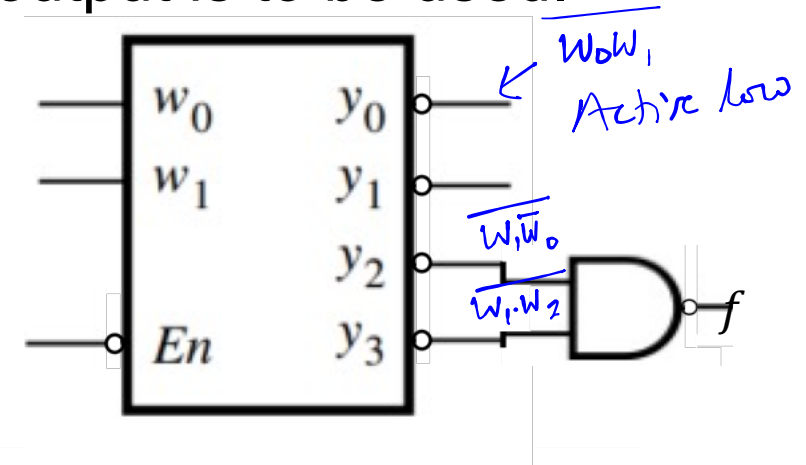

$En$	$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
1	$\phi$	$\phi$	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

Active Low Output.


# 4:1 Mux using Decoder:

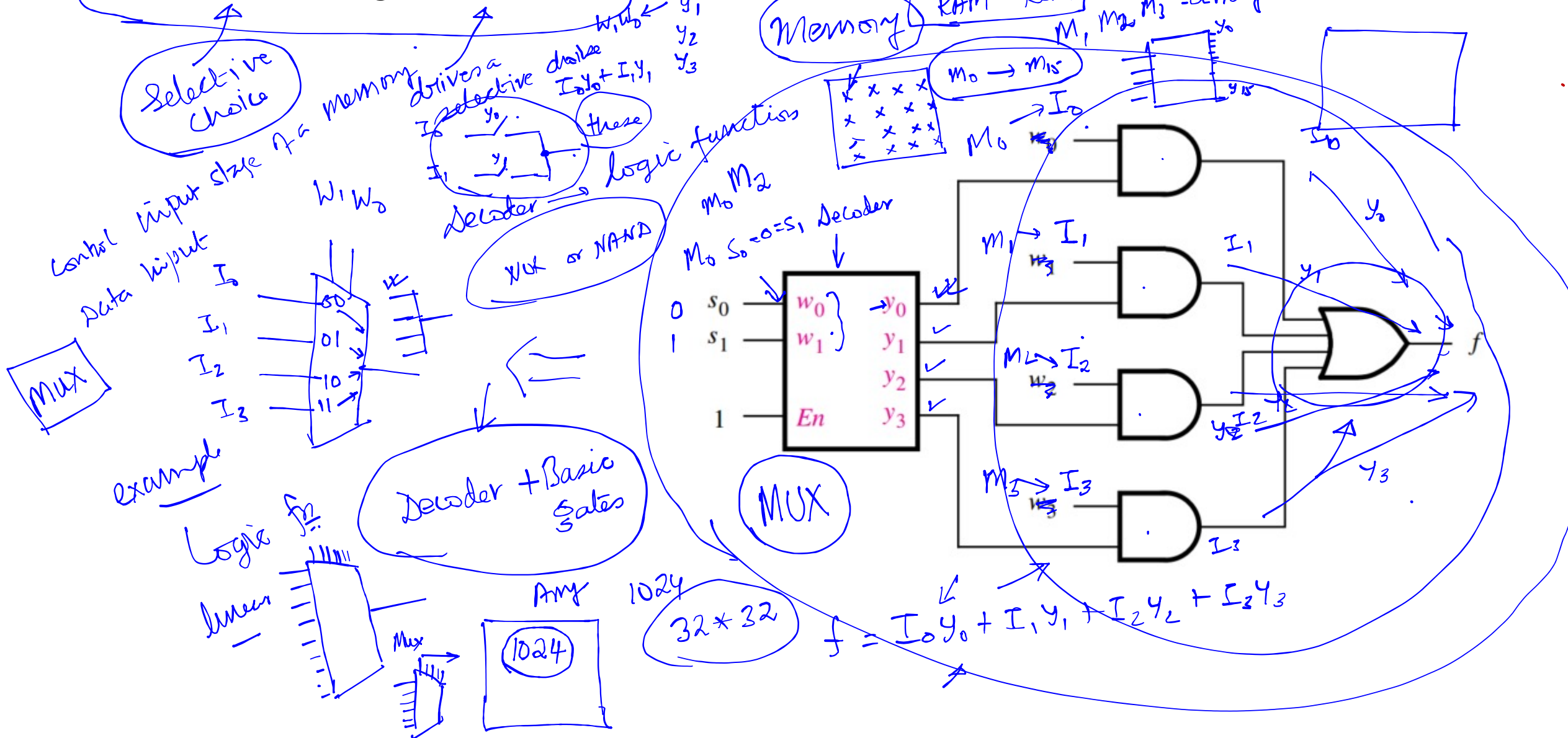

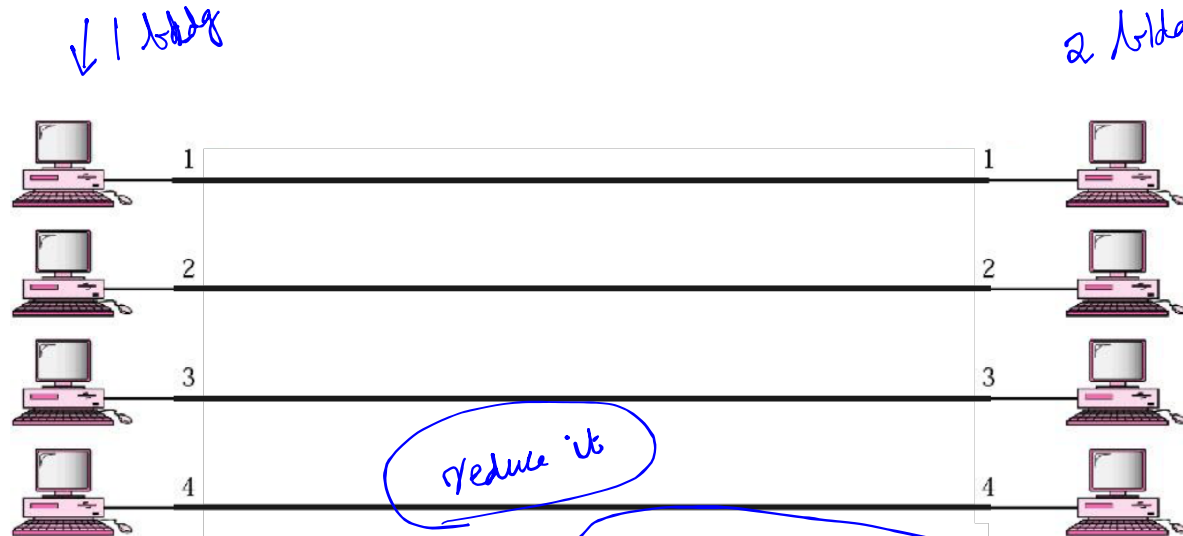
## Demultiplexers:

*Multiplexer*

A demultiplexer (also known as a demux or data distributor) is defined as a circuit that can distribute or deliver multiple outputs from a single input. The demultiplexer's output lines are 'n' in number, the select line number is 'm' and  $n = 2^m$ . The control signal or select input code decides the output line to which the input is to be transmitted.




This requires 4 wires/lines

 

This requires 1 MUX, 1 wire and 1 DMUX

# Demultiplexers:

 

Truth Table

$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

$$y_0 = \overline{w_1} \cdot \overline{w_0} \cdot I$$

$$y_1 = \overline{w_1} \cdot w_0 \cdot I$$


$$y_2 = w_1 \cdot \overline{w_0} \cdot I$$

$$y_3 = w_1 \cdot w_0 \cdot I$$

Decoder with Enable.

$$I = E_n$$
 
## Realizing Demultiplexer using a Decoder:





$$y_0 = \overline{w_1} \cdot \overline{w_0} \cdot E_n$$

$$y_1 = \overline{w_1} \cdot w_0 \cdot E_n$$

$$y_2 = w_1 \cdot \overline{w_0} \cdot E_n$$

$$y_3 = w_1 \cdot w_0 \cdot E_n$$

 
 


$$y_0 = \overline{w_1} \cdot \overline{w_0} \cdot I$$

$$y_1 = \overline{w_1} \cdot w_0 \cdot I$$

$$y_2 = w_1 \cdot \overline{w_0} \cdot I$$

$$y_3 = w_1 \cdot w_0 \cdot I$$

  

$$y_0 = \overline{w_1} \cdot \overline{w_0} \cdot I$$

$$y_1 = \overline{w_1} \cdot w_0 \cdot I$$

$$y_2 = w_1 \cdot \overline{w_0} \cdot I$$

$$y_3 = w_1 \cdot w_0 \cdot I$$

# HW

- Design full subtractor using 3:8 decoder
- Design full subtractor using 1:8 demultiplexer
- BCD to 7-segment decoder