
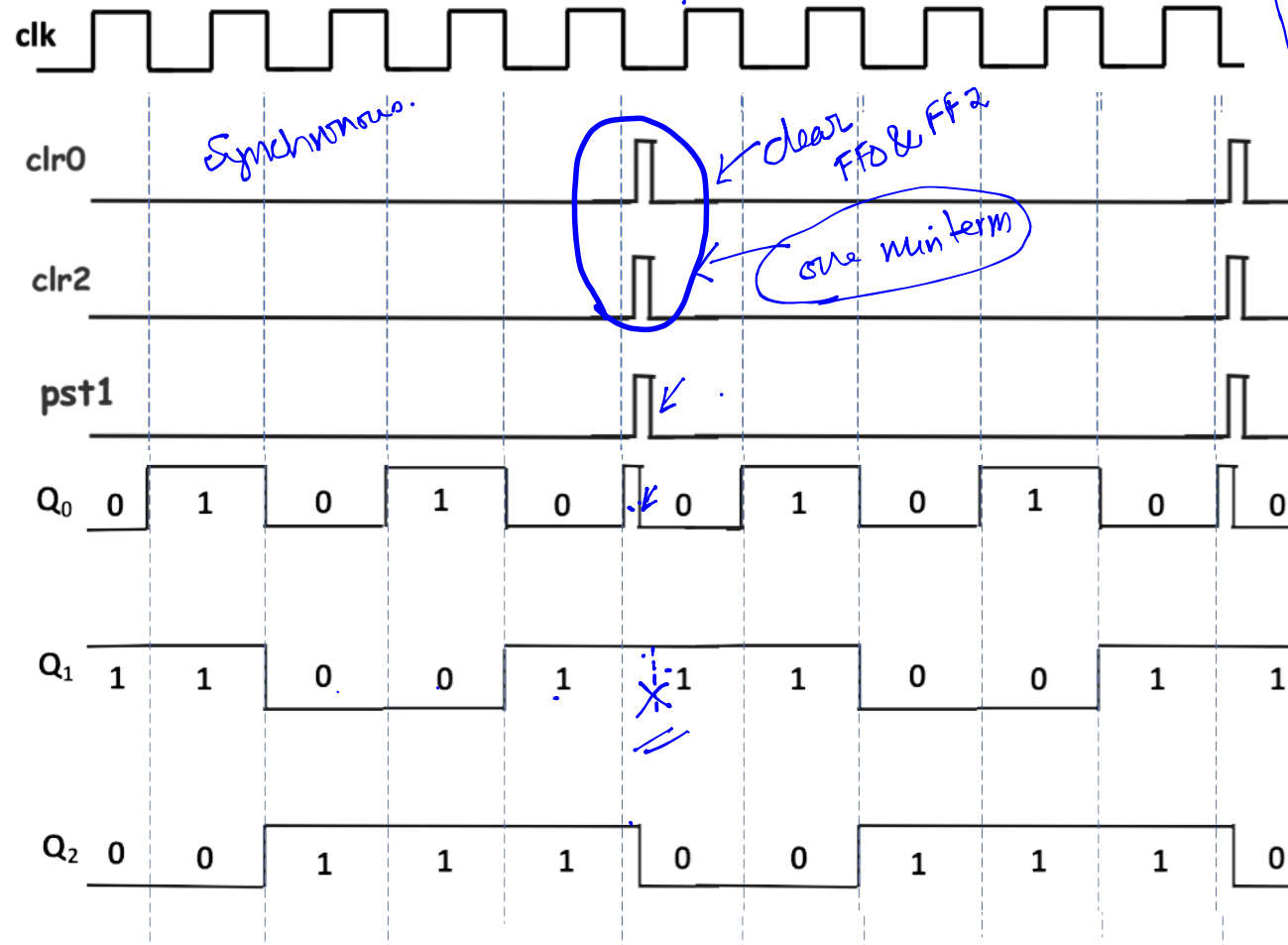


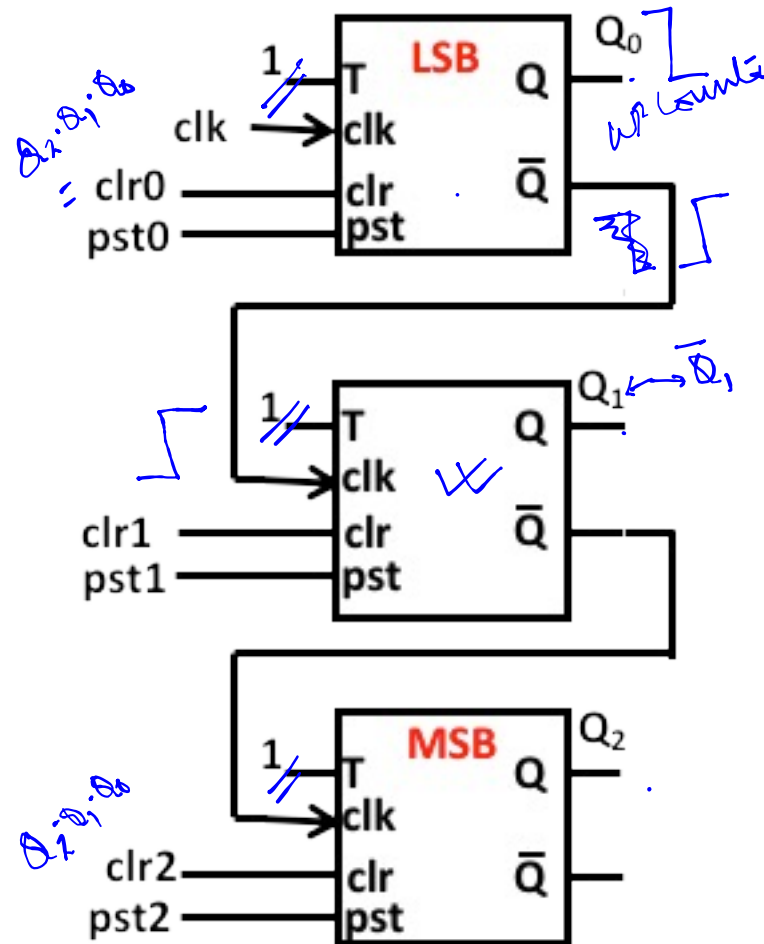


# Binary Counter with Clear and Preset:

- Counter: 2-→3-→4-→5-→ 6-→2-→3-→4-→5-→ 6-→2-----




$$clr_0 = clr_2 = pst_1 = Q_2 \cdot Q_1 \cdot Q_0 ; \quad clr_1 = pst_0 = pst_2 = 0$$


 
# Synchronous Modulo-6 UP Counter using T-FF:




## Frequency Division by 3:

 

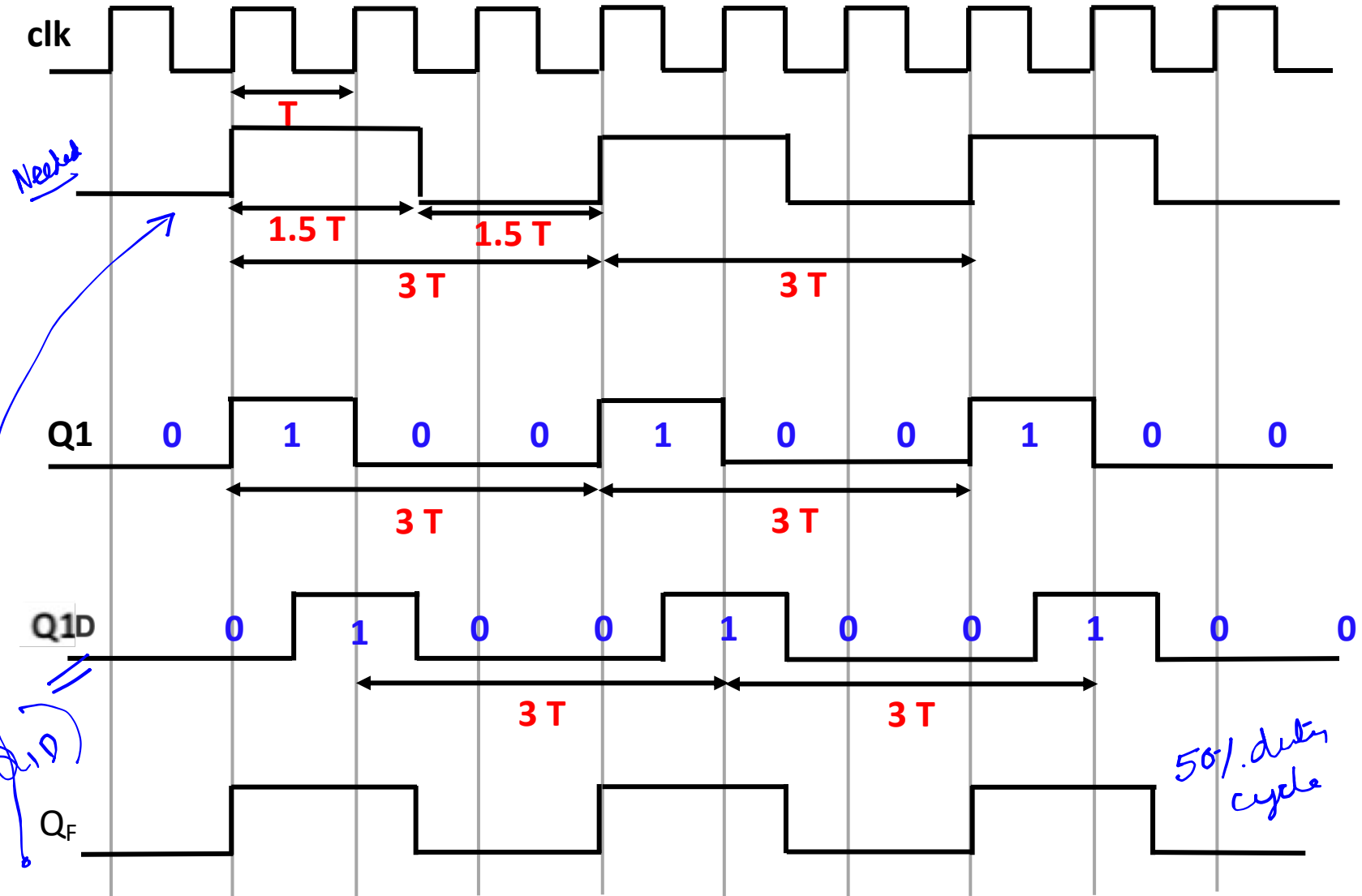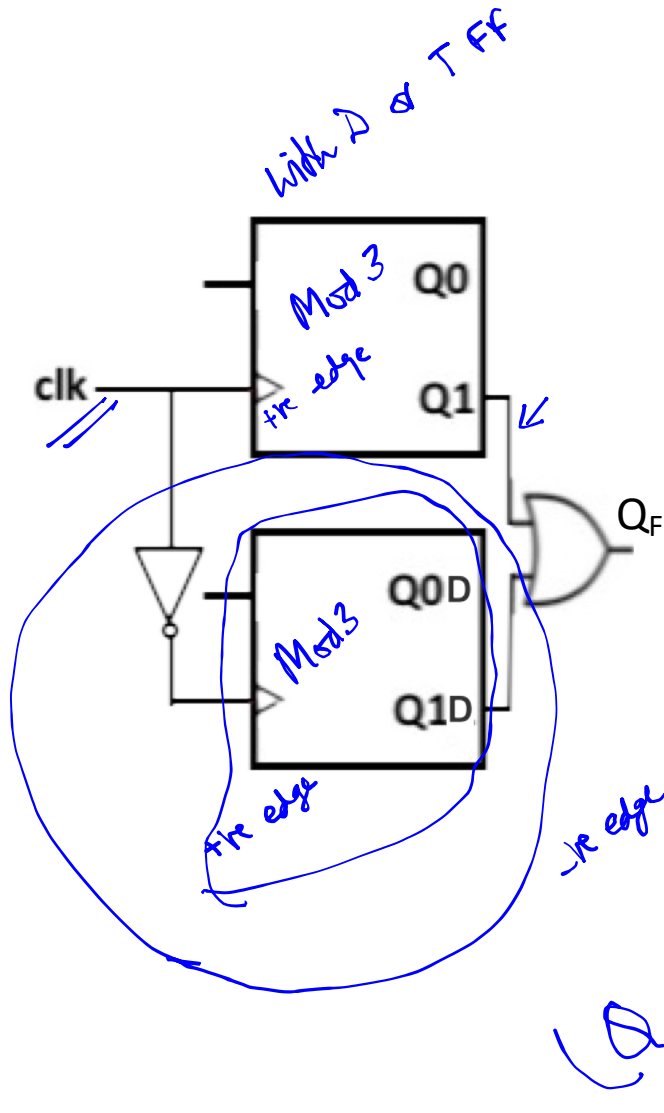
# Frequency Division by 3 with Duty Cycle 50%: Alternative


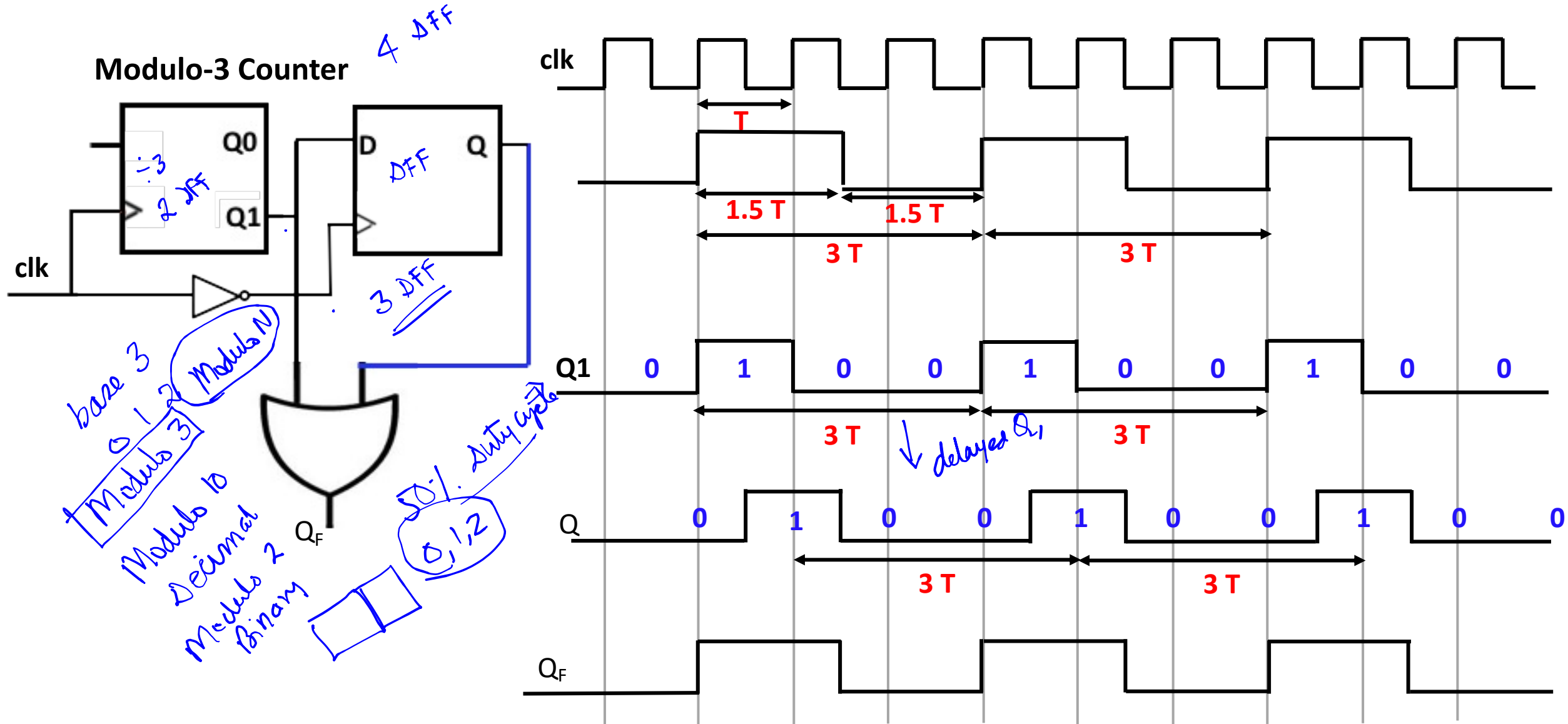
# Frequency Division by 3 with Duty Cycle 50%:




# Frequency and Phase:

 


These two clocks have same frequency, but the phase difference is 45 degree.

Phase shift  $+45^\circ$

2.5

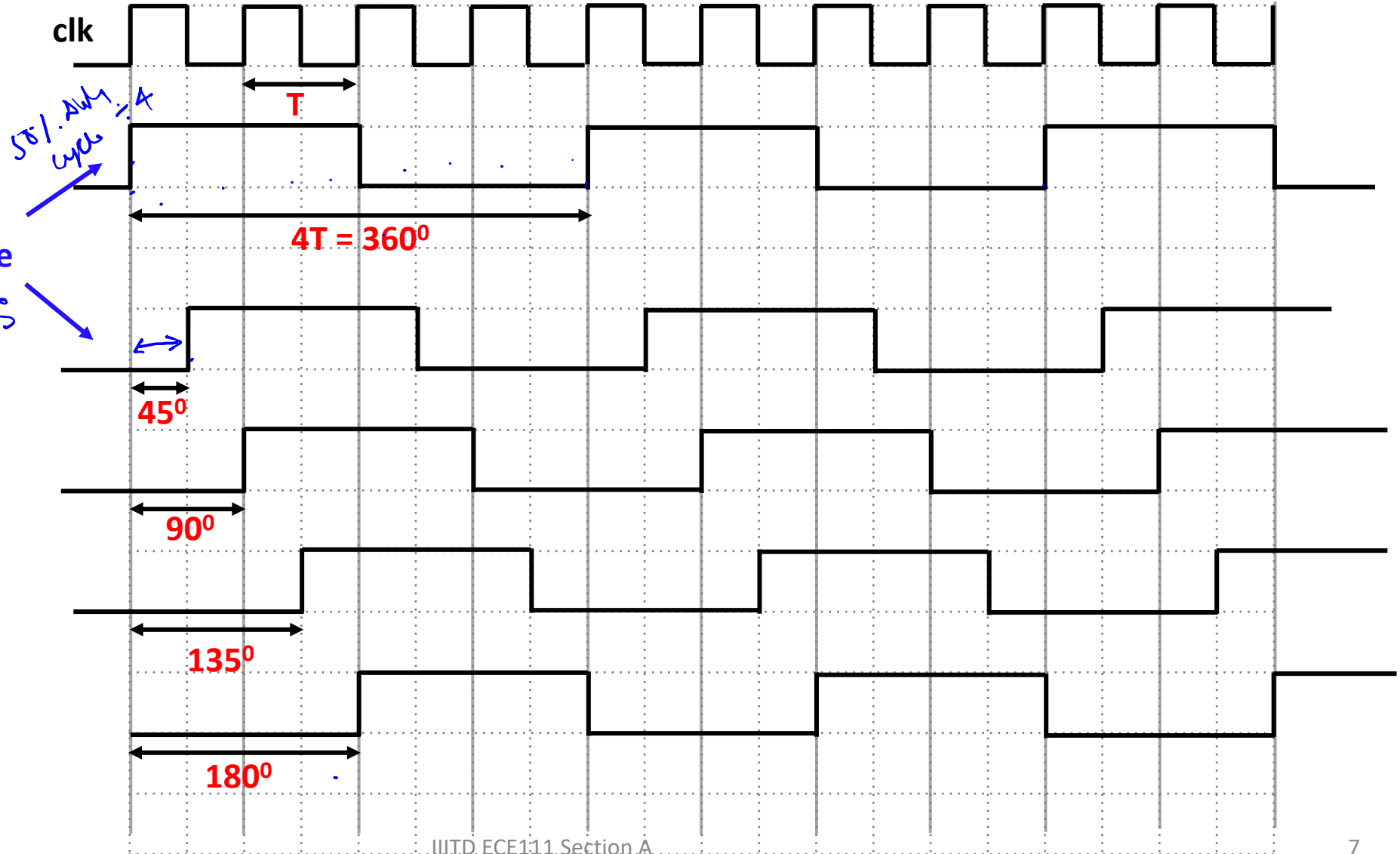


# Frequency and Phase:

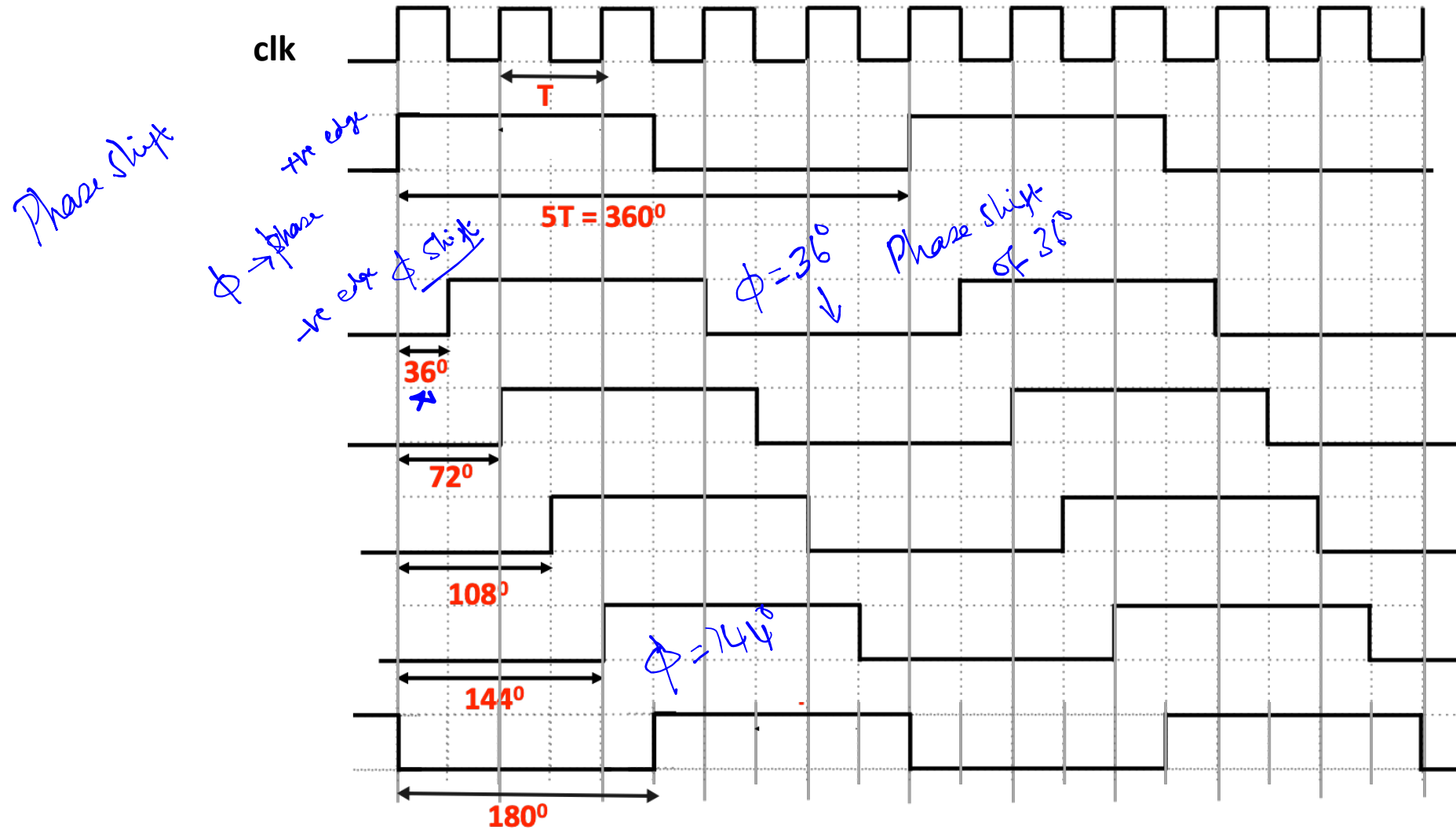




## Frequency, Phase and Duty Cycle:

$Q_1$	$Q_0$
0	0
0	1
1	0
1	1

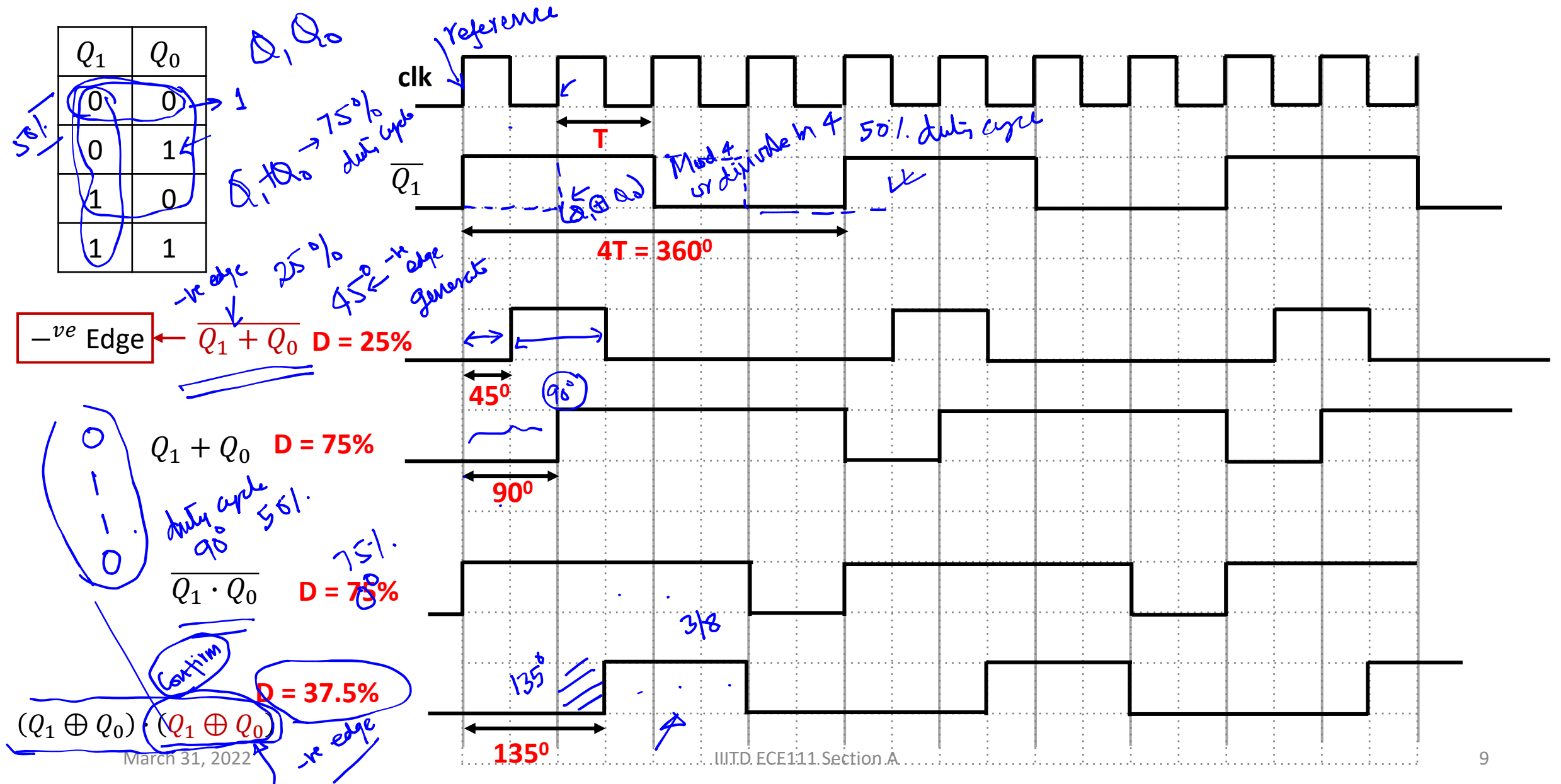


# Frequency Division by 5:

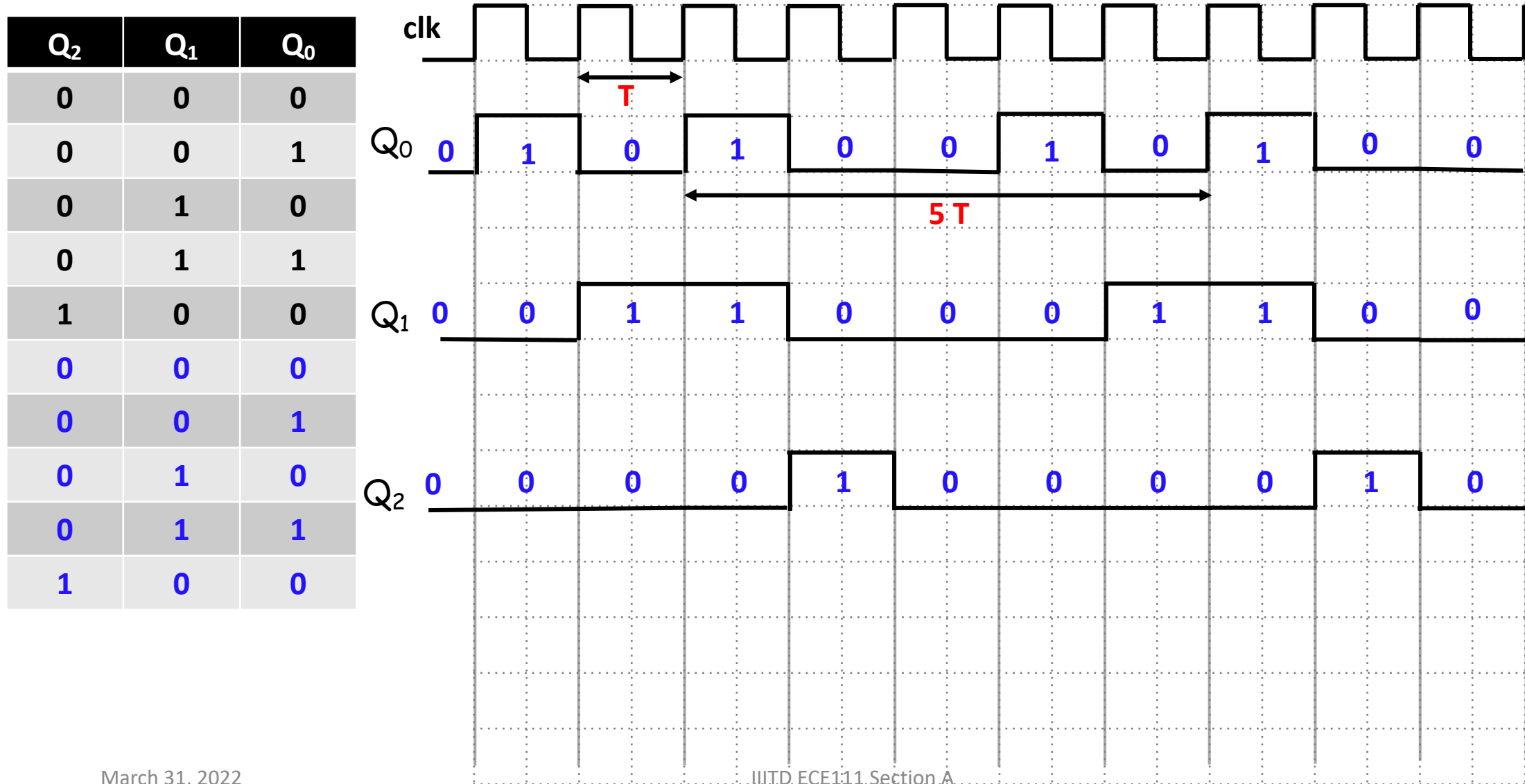


## Frequency Division by 5 with 50% duty cycle:

$Q_2$	$Q_1$	$Q_0$
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0

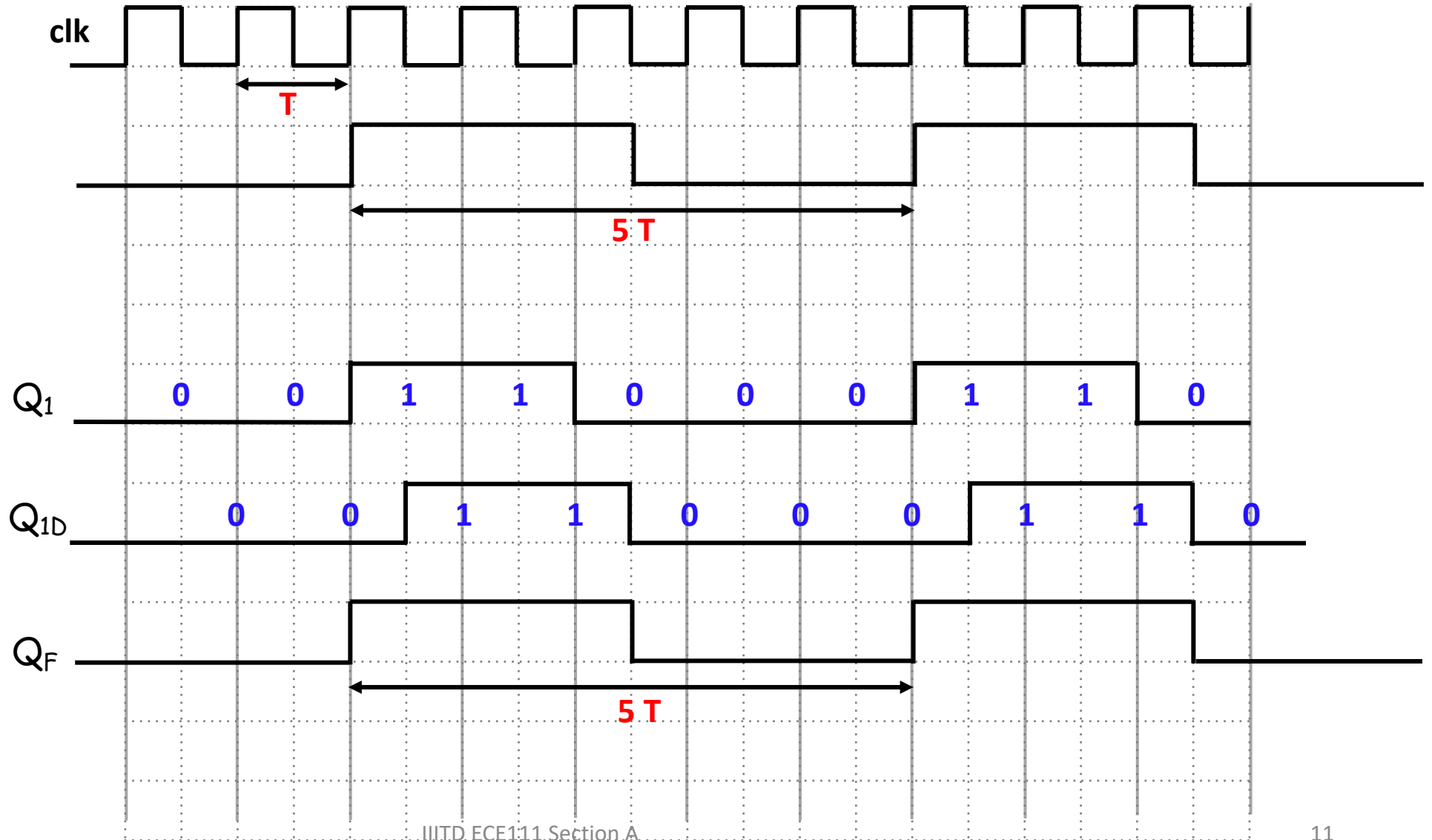

# Frequency Division by 5:

 

$Q_2$	$Q_1$	$Q_0$
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0


- Desired Duty cycle: 20% -> Use  $Q_2$
- Desired Duty cycle: 40% -> Use  $Q_1$
- Desired Duty cycle: 60% -> Use  $Q_1 + Q_2$
- Desired Duty cycle: 50% -> Use  $Q_1$  from +ve edge triggered DFF ORed with  $Q_1$  from -ve edge triggered D-FF
- Desired Duty cycle: 30% -> Use  $Q_2$  from +ve edge triggered DFF ORed with  $Q_2$  from -ve edge triggered D-FF
- Desired Duty cycle: 80% -> Use  $Q_2 + Q_1 + Q_0$

Mod 5 counter  
100% / 5 = 20%


- Minimum Duty cycle: 20% with resolution of 10%
- Phase resolution:  $360/21 = 36$  degree
 
## Frequency Division by 3 (HW):

Realize these  
wave forms  
identifying Duty cycle  
&  $\phi$



## Frequency Division by 3 (HW):

 

# Homework

- Design the circuit which divides the input clock by 7 or 9 or 11, you can use the same approach.

# Characteristics Equation of Various Flip Flops:

Device Type	Characteristic Equation
S-R Latch	$Q_n = S + \bar{R}Q_{n-1}$
D Latch	$Q_n = D$
Edge-Triggered D flip-flop	$Q_n = D$
D flip-flop with enable	$Q_n = En \cdot D + Q_{n-1}$
Master Slave S-R flip-flop	$Q_n = S + \bar{R}Q_{n-1}$
Master Slave J-K flip-flop	$Q_n = J \cdot \overline{Q_{n-1}} + \bar{K}Q_{n-1}$
Edge Triggered J-K flip-flop	$Q_n = J \cdot \overline{Q_{n-1}} + \bar{K}Q_{n-1}$
T flip-flop	$Q_n = \overline{Q_{n-1}}$
T flip-flop with enable	$Q_n = En \cdot \overline{Q_{n-1}} + \bar{E}nQ_{n-1}$

Next week  
class on  
Monday & Wednesday  
8:30 to 10:00  
Free on Thursday

I will be  
available  
on the link  
for office hour  
on Thursday  
on class time